



$$i' = \frac{1}{L}(u - Ri - u_c) \quad (1)$$

$$u'_c = \frac{1}{C}i \quad (2)$$

We derive u'_c from equation [2] and we obtain

$$u''_c = \frac{1}{C}i' \quad (3)$$

then we replace variable i' from [1] into [3] and we get

$$u''_c = \frac{1}{C} \frac{1}{L}(u - Ri - u_c). \quad (4)$$

Repeatedly, we substitute variable i from [2] into equation [4]

$$u''_c = \frac{1}{C} \frac{1}{L}(u - RCu'_c - u_c) \quad (5)$$

and we modify it into form

$$LCu''_c + RCu'_c + u_c = u. \quad (6)$$

We set concrete numerical values

$$L = 10^{-2}H, C = 10^{-6}F, R = 200\Omega, u = \sin(1000)t$$

$$L \cdot C = 10^{-8}$$

$$R \cdot C = 2 \cdot 10^{-4}$$

Firstly, we replace variables in equation [6]

$$10^{-8}u''_c + 2 \cdot 10^{-4}u'_c + u_c = \sin(1000)t \quad (7)$$

which give us characteristic equation

$$10^{-8}\lambda^2 + 2 \cdot 10^{-4}\lambda + 1 = 0$$

$$\lambda_{1,2} = \frac{-2 \cdot 10^{-4} \pm \sqrt{4 \cdot 10^{-8} - 4 \cdot 10^{-8}}}{2 \cdot 10^{-8}}$$

$$\lambda_{1,2} = \frac{-2 \cdot 10^{-4} \pm 0}{2 \cdot 10^{-8}}$$

with the double root

$$\lambda_{1,2} = -10^4. \quad (8)$$

Homogeneous solution for **double root** is given by

$$u_{CH} = e^{-10^4 t}(C_1 t + C_2). \quad (9)$$

The right-hand side of double root solution will be expressed by

$$u_{cp} = A \sin(1000)t + B \cos(1000)t \quad (10)$$

and before replacement we derive variable u_{cp} to u'_{cp} a u''_{cp} using equation [10]

$$u'_{cp} = A1000 \cos(1000)t - B1000 \sin(1000)t \quad (11)$$

$$u''_{cp} = -A10^6 \sin(1000)t - B \cdot 10^6 \cos(1000)t \quad (12)$$

Now we substitute equations [10], [11] and [12] into [7] and we obtain

$$10^{-8}[-A \cdot 10^6 \cdot \sin(1000)t - B \cdot 10^6 \cdot \cos(1000)t] + 2 \cdot 10^{-4}[1000A \cdot \cos(1000)t - 1000B \cdot \sin(1000)t] + A \cdot \sin(1000)t + B \cdot \cos(1000)t = \sin(1000)t \quad (13)$$

We compare coefficients on left-hand and right-hand side of equation [13] and we get system of two linear equations

$$10^{-8}(-A) \cdot 10^6 - 2 \cdot 10^{-4} \cdot 1000B + A = 1$$

$$10^{-8}(-B) \cdot 10^6 + 2 \cdot 10^{-4} \cdot 1000A + B = 0$$

and we calculate

$$\begin{aligned} 0,99A - 0,2B &= 1 \\ 0,2A + 0,99B &= 0 \end{aligned}$$

$$\begin{aligned} A &= -4,95B \\ 0,99(-4,95)B - 0,2B &= 1 \\ -5,1005B &= 1 \end{aligned}$$

$$\begin{aligned} B &\doteq -0,19605921 \\ A &\doteq 0,97049309 \end{aligned}$$

General solution is given by

$$u_c = u_{ch} + u_{cp}$$

which in our case is

$$u_c = e^{-10^4 t} (C_1 \cdot t + C_2) + 0,97049309 \sin(1000)t - 0,196059209 \cos(1000)t \quad (14)$$

Initial values are set to zero.

$$u_c(0) = 0 \quad i(0) = 0 \quad \implies \quad u'_c(0) = 0$$

By substituting condition $u_c(0) = 0$ into [14] we calculate

$$C_2 = 0,196059209 \quad (15)$$

and before using substitution $u'_c(0) = 0$ we derive equation [14]

$$\begin{aligned} u'_c &= (-10^4) \cdot e^{-10^4 t} (C_1 \cdot t + C_2) + e^{-10^4 t} \cdot C_1 + \\ &\quad + 0,97049309 \cdot 1000 \cos(1000)t + 0,196059209 \cdot 1000 \sin(1000)t \end{aligned}$$

$$u'_c = (-10^4) \cdot e^{-10^4 t} (C_1 \cdot t + C_2) + e^{-10^4 t} \cdot C_1 + 970,49309 \cos(1000)t + 196,059209 \sin(1000)t \quad (16)$$

Now we substitute $u'_c(0) = 0$ into [16]

$$0 = -10^4 C_2 + C_1 + 970,49309$$

and we replace C_2 from equation [15]

$$\begin{aligned} 0 &= -10^4 \cdot 0,196059209 + C_1 + 970,49309 \\ C_1 &= 990,099002 \end{aligned} \quad (17)$$

Finally, we substitute [15] and [17] into [14] and the result is given by

$$\begin{aligned} \mathbf{u}_c &= \mathbf{e}^{-10^4 \mathbf{t}} (990,099002 \mathbf{t} + 0,196059209) + \\ &+ 0,97049309 \sin(1000)\mathbf{t} - 0,196059209 \cos(1000)\mathbf{t} \end{aligned} \quad (18)$$

For calculating variable i we modify equation [2] into

$$i = C \cdot u'_c \quad (19)$$

and the first we derive u_c from [18]

$$\begin{aligned} u'_c &= -10^4 e^{-10^4 t} (990,099002t + 0,196059209) + e^{-10^4 t} 990,099002 + \\ &+ 0,97049309 \cdot 1000 \cos(1000t) + 0,196059209 \cdot 1000 \sin(1000t) \end{aligned}$$

$$u'_c = e^{-10^4 t} (9900990,02 \cdot t - 2950,691029) + 196,059209 \sin(1000t) + 970,49309 \cos(1000t) \quad (20)$$

Then we substitute u'_c from [20] into [19] and the result is

$$\begin{aligned} i &= 10^{-6} [e^{-10^4 t} (9900990,02 \cdot t - 2950,691029) + \\ &+ 196,059209 \sin(1000t) + 970,49309 \cos(1000t)] \end{aligned}$$

$$\begin{aligned} \mathbf{i} &= \mathbf{e}^{-10^4 \mathbf{t}} (9,90099002 \mathbf{t} - 29,50691029 \cdot 10^{-4}) + \\ &+ 1,96059209 \cdot 10^{-4} \sin(1000\mathbf{t}) + 9,7049309 \cdot 10^{-4} \cos(1000\mathbf{t}) \end{aligned} \quad (21)$$