


# Prvky počítačů (IPRe)

**First lab**

Vysoké učení technické v Brně, Fakulta informačních technologií v Brně  
Božetěchova 2, 612 66 Brno

Lector: Petr Veigend (iveigend@fit.vutbr.cz)


Gabriela Nečasová  
Petr Veigend

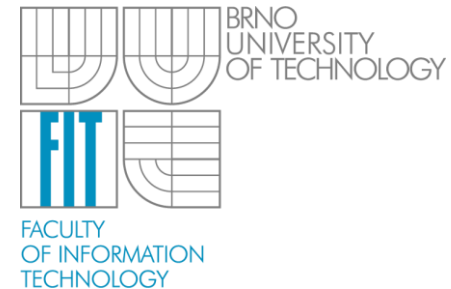

2014/2015

- Basic information, safety briefing
- Introduction to the lab kit, IPR metr software
- Simple measurements
- Solderless field circuits

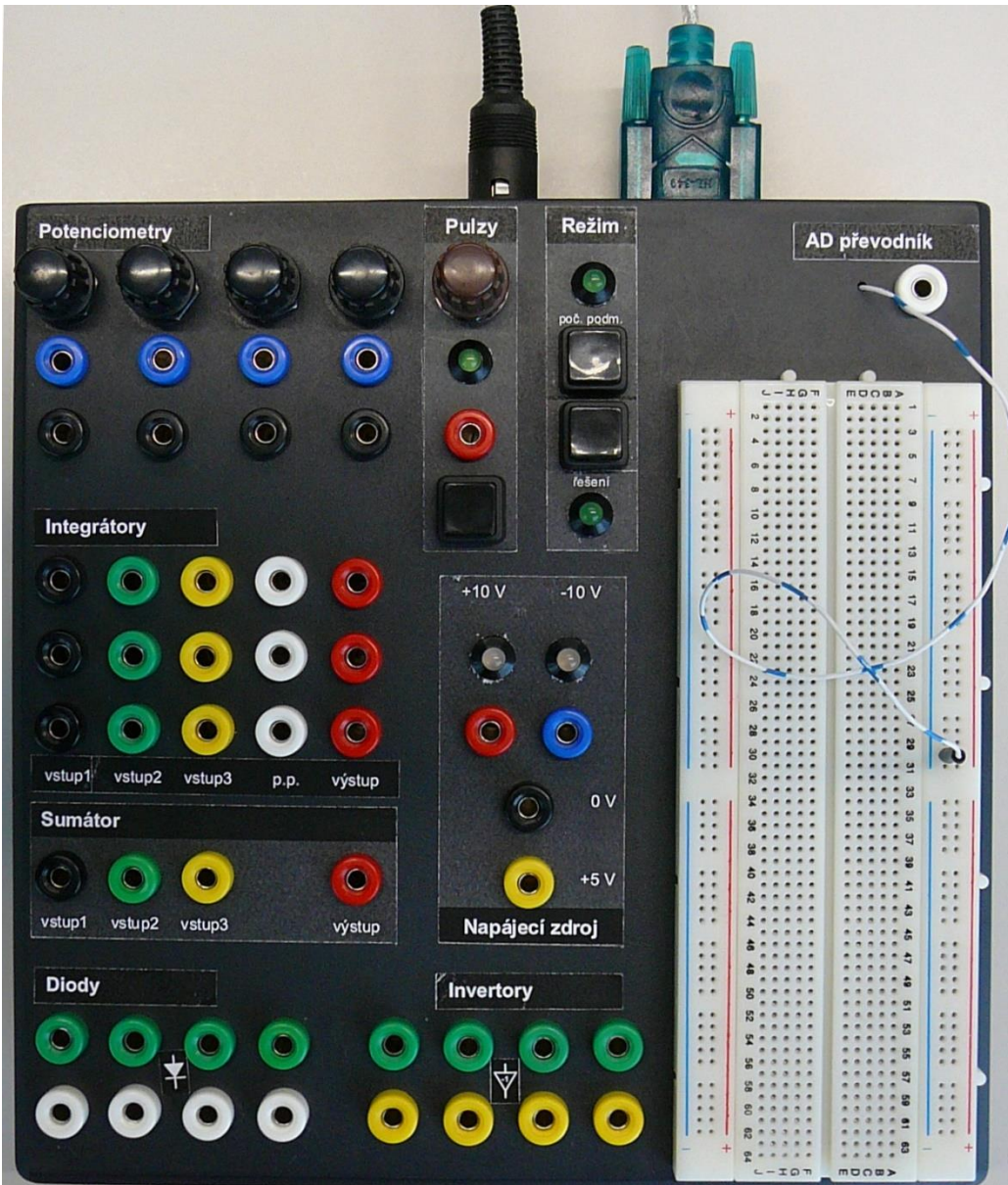
- Hi, my name is Petr
- You don't have to work alone, you can cooperate
  - **The important thing is to learn something new, understand something, etc.**
- Basically don't eat, drink, behave responsibly
- We are going to work with electricity and you all know that it can kill you


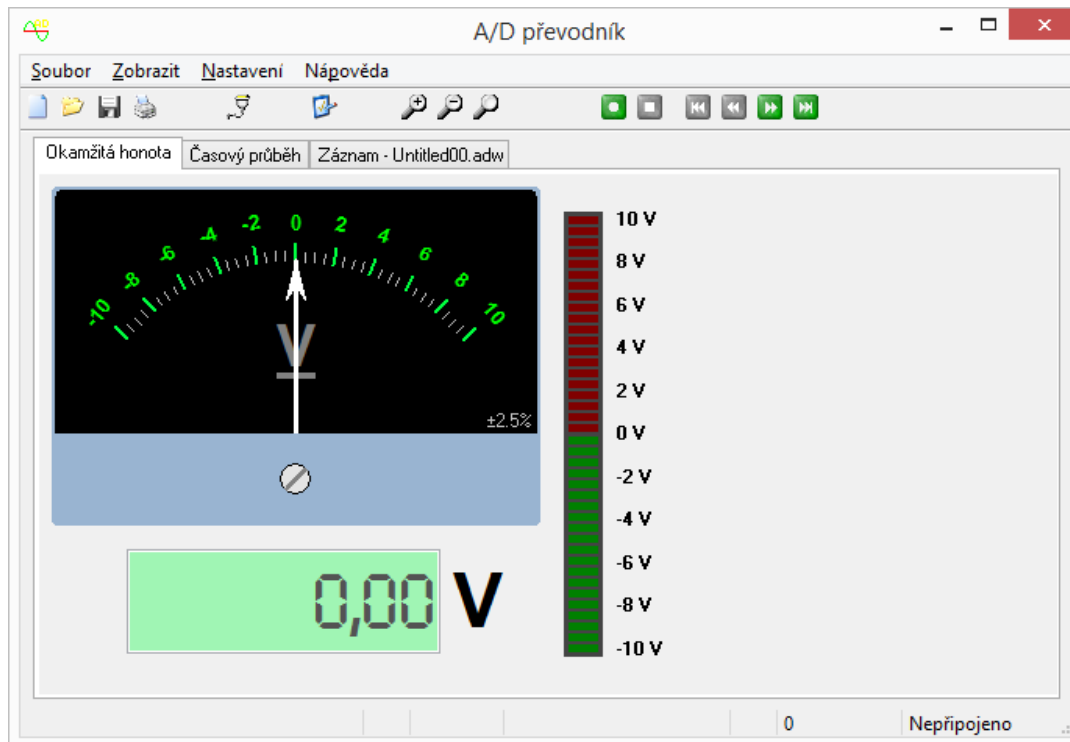
## Notice:

- The button that changes the mode of the operation of the kit (Režim)
- AD converter (převodník) input
- Voltage sources +10 V, 0 V, -10 V, +5 V (napájecí zdroj)
- Resistors with variable resistances (potentiometers)
- Integrators
- Adders (sumátor)
- Invertors
- Diodes
- **Solderless board**

- Displays the voltage on the input of AD converter



- Okamžitá hodnota – current value
- Časový průběh – value in time

- Download IPR Metr from
  - [http://www.fit.vutbr.cz/~strnadel/ipr/ipr\\_downloads.htm](http://www.fit.vutbr.cz/~strnadel/ipr/ipr_downloads.htm)
- Save it on your P drive and run it
  - Check, if it says **Připojeno** (**Connected** in English) in the lower hand corner
  - If it doesn't, check the connection settings
    - Nastavení → Vlastnosti → Nastavení portu
    - Port=COM3, BaudRate=9600, StopBits=1, DataBits=8, Parity=None, FlowControl=None
- **Note:** Switch your kit to the **Řešení** operation mode


- Using the IPR Metr check that the voltage source supplies the correct voltage.



- Using the IPR Metr check that the voltage source supplies the correct voltage.
- **Solution**
  - Voltage source (+10V, -10V, +5V) – AD converter




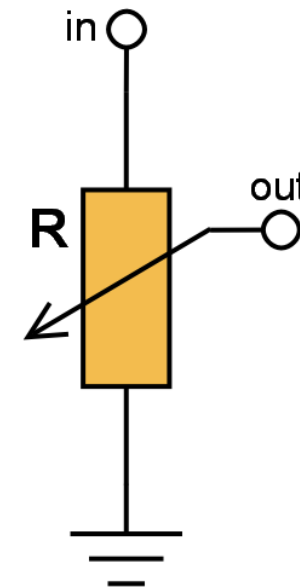- Choose one of the potentiometers
- Using the IPR metr check that you can control the value of the voltage in between 0 % to 100 % of the **input voltage** (by turning the knobs)




- Choose one of the potentiometers
- Using the IPR metr check that you can control the value of the voltage in between 0 % to 100 % of the **input voltage** (by turning the knobs)
- **Solution**
  - **Input of the potentiometer** – voltage source
  - **Output of the potentiometer** – AD převodník

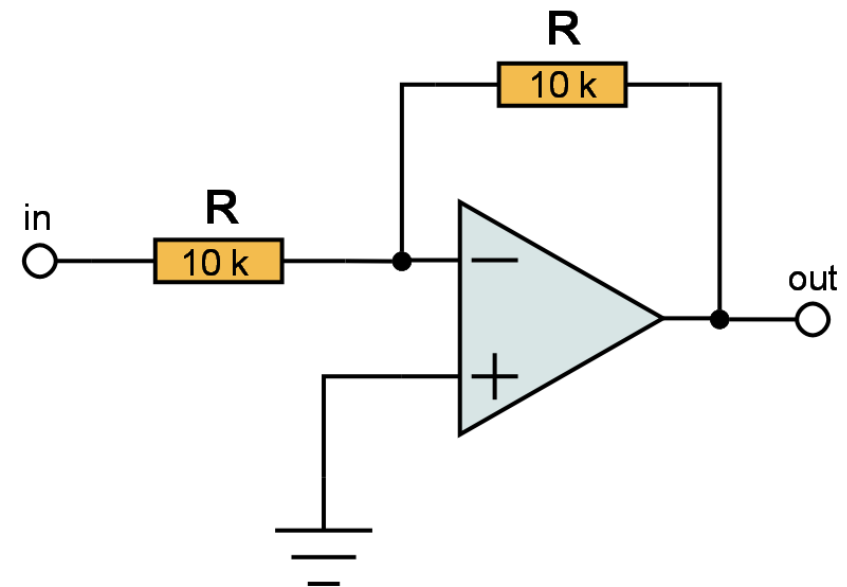- Check that the inverter can flip the polarity of the **input** voltage.



- Check that the inverter can flip the polarity of the **input** voltage.
- **Solution**
  - **Input** – voltage source
  - **Output** – AD convertor

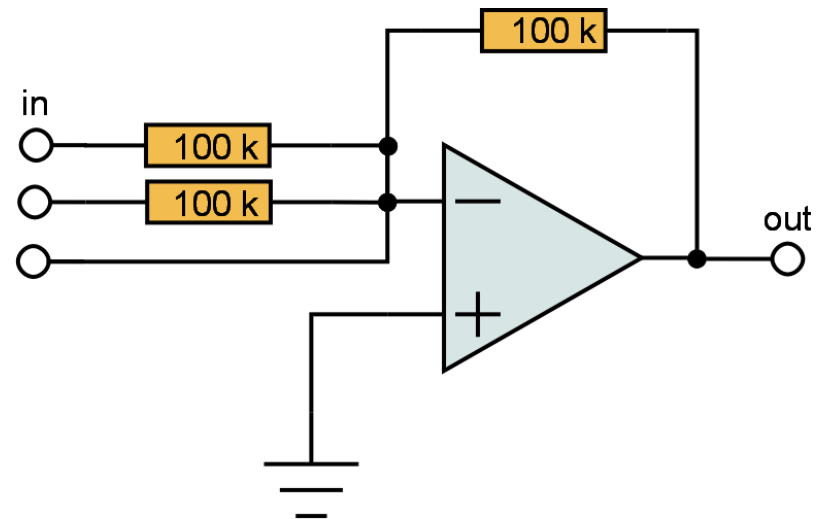- Check that the adder can add the voltages together
  - 3 inputs (**black, green, yellow**), invert polarity
  - **1 output**
- Note that one of the inputs is multiplied by infinity. Figure out which one and don't use it.




- Check that the adder can add the voltages together
  - 3 inputs (**black**, **green**, **yellow**), invert polarity
  - **1 output**
- Note that one of the inputs is multiplied by infinity. Figure out which one and don't use it.
- **Solution**
  - 1. input: -10V
  - 2. input: +5V
  - Output: AD convertor (you should get +5 V)

- Check the integrator

- 3 inputs (**black, green, yellow**)
- 1 initial condition (white)
- **1 output**
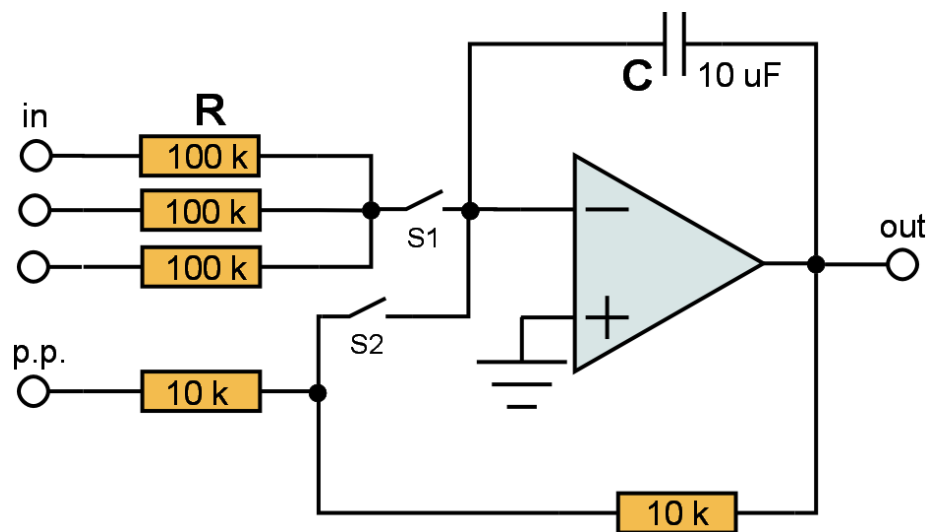
## Modes

- Initial condition (poč. podm.)
- Solution (řešení)





- Check the integrator
  - 3 inputs (**black**, **green**, **yellow**)
  - 1 initial condition (white)
  - **1 output**
- **Solution**
  - Input: -10V,
  - Initial condition (white socket): +5V,
  - Change mode to **poč. podm.**
  - Output: AD convertor
  - Switch to mode **řešení**
- Note that integral should calculate the area under the curve



- In this part the lab, we are going to work with the solderless field and multimeter to measure parameters of electrical circuits

**Change the settings before plugging in!!!!!!**

**DCV**  
direct current  
voltage



**DCA**  
direct current  
amperes



**$\Omega$  resistance**




**Measurements (U, I, R)**  
**Ground (GND, -)**



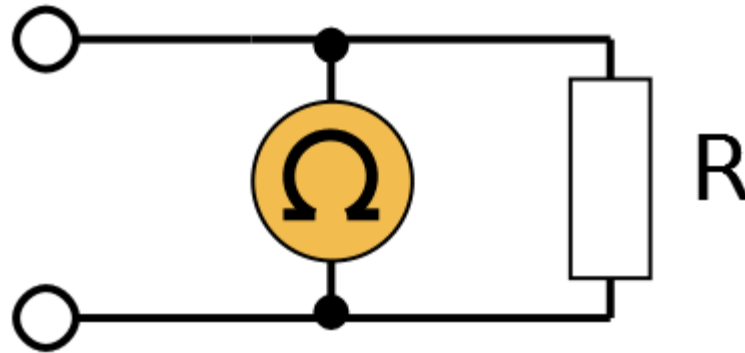- 1) Prepare a resistor and measure its **resistance (R)**
- 2) Then connect the provided circuit including the voltage
- 3) Measure **the current (I)** that is passing through the resistor
- 4) Measure the **voltage (U)** on the resistor

- Connect the resistor to the solderless board and measure its resistance




- **How to**


- Just connect the resistor to the different columns of the solderless field and connect multimeter in parallel (**same columns as the resistor**)
- Don't connect input voltage
- **Multimeter:** set  $\Omega$ , **20k**

- Example of the parallel connection


Schematic diagram

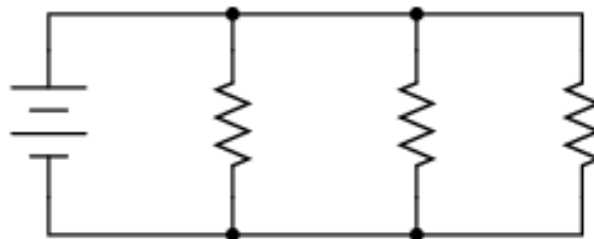

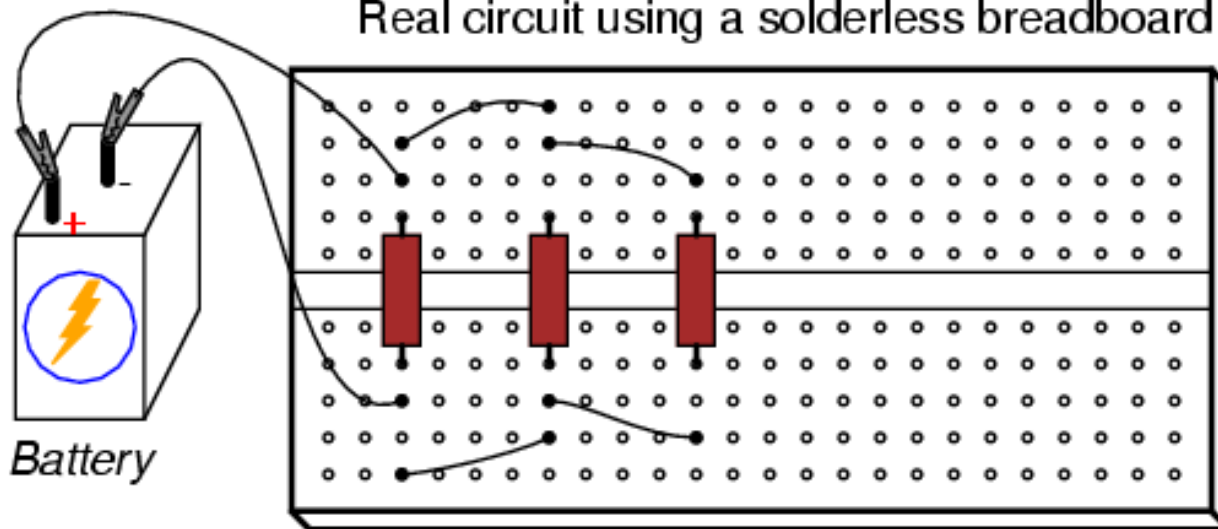
Real circuit using a solderless breadboard



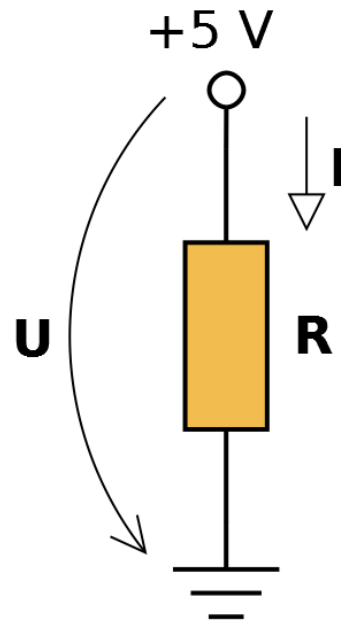- Connect this circuit in the solderless field



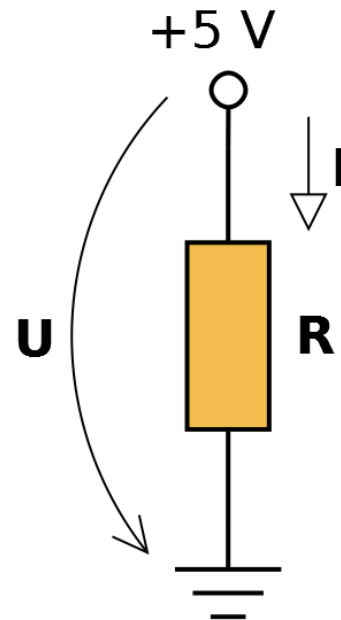
- Connect this circuit in the solderless field



- **How to**

- On the one terminal of R connect voltage of 5V (**red column**)
- On the second terminal of R connect 0V (**GND**)

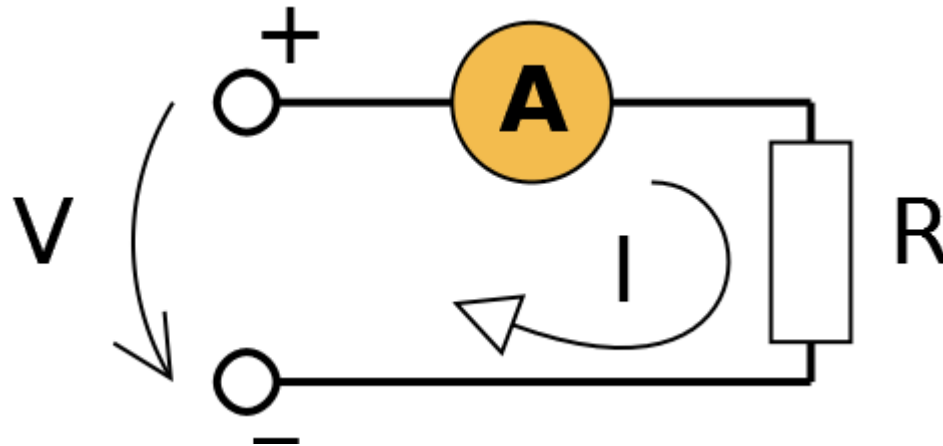
- Current has to be measured **in series**



- **How to**
  - **Multimeter: DCA, 200mA**, before plugging in



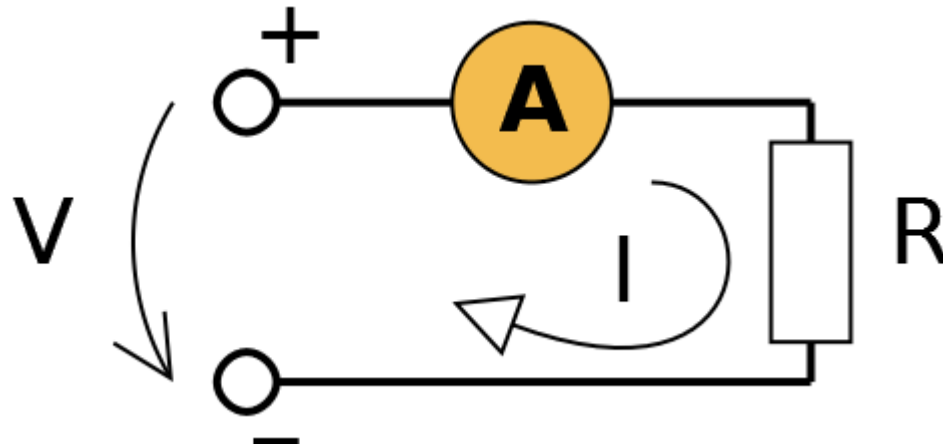
- Current has to be measured **in series**


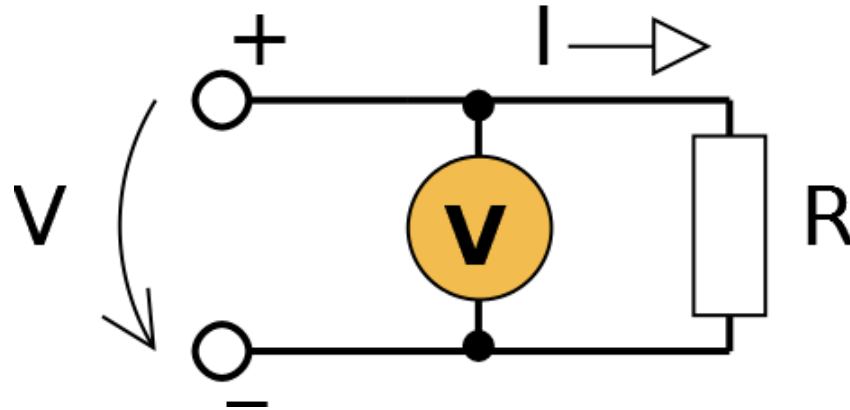
## • How to


- **Multimeter: DCA, 200mA**, before plugging in
- On one terminal of R connect voltage of 5V (same column)
- On the other terminal of R (same column) connect the current meter (multimeter, measurements cable), connect the GND cable to the 0V (**GND**)

- Voltage has to be measured **in parallel**



- **How to**
  - **Multimeter: DCV, 20V**, before plugging in

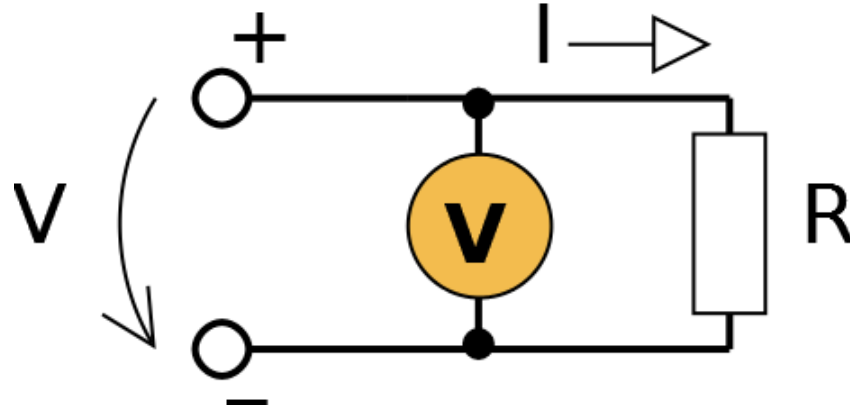- Voltage has to be measured **in parallel**



- **How to**

- **Multimeter: DCV, 20V**, before plugging in
- On the one terminal of R connect 5V
- On the second terminal, connect 0V
- Connect the measurement cable of the multimeter to the same column as the 5V
- Connect the GND cable of the multimeter to the column with the GND

- Connect the following circuit (one terminal is connected to 5V, other is disconnected)




- What is the voltage on the resistor?

- Connect the following circuit (one terminal is connected to 5V, other is disconnected)




- What is the voltage on the resistor?
- **Result**
  - There is no voltage drop on the resistor, so there is nothing to measure

- Connect the following circuit

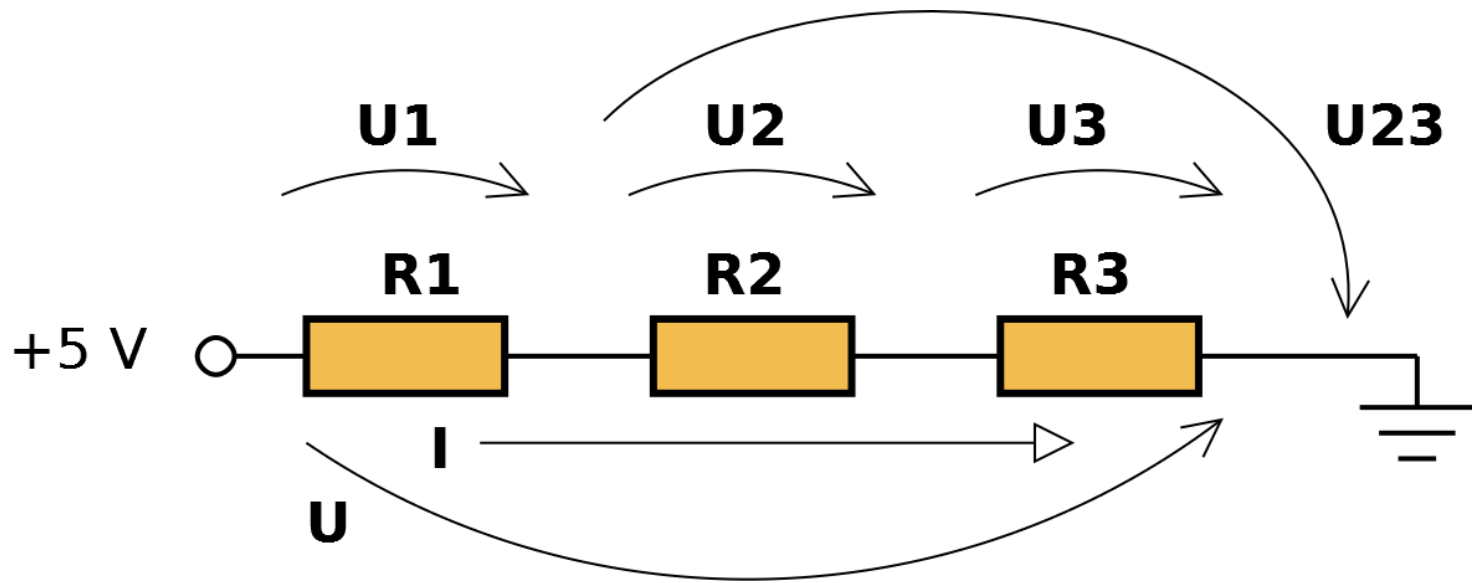

- Check the Ohm's Law, Kirchhoff's Law

- Check how you set your multimeters

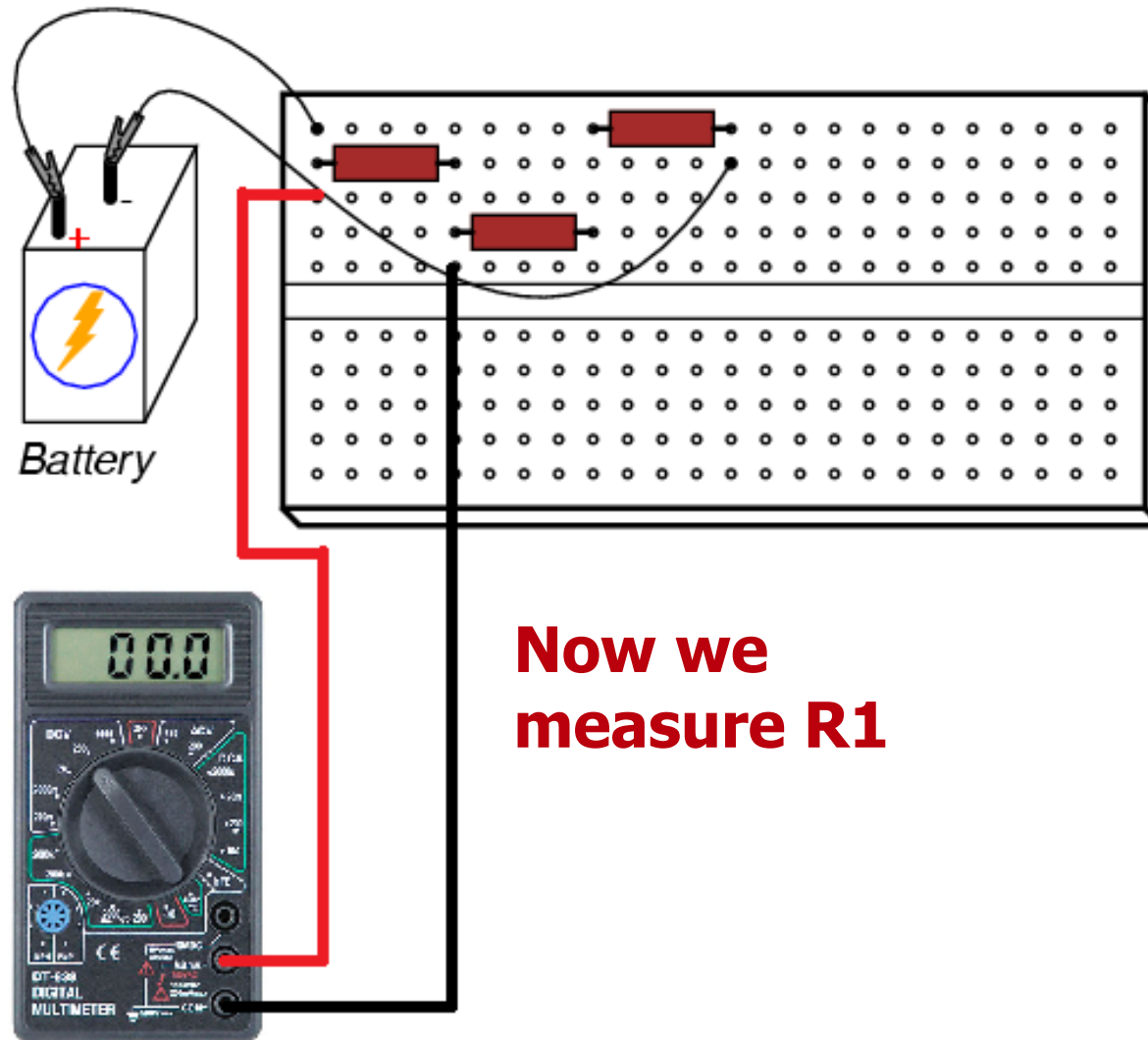

Thank you for your attention!