

IPRE ≡ HARDWARE OF GAMERS

AGAIN LABORATORIES

JIRI KUNOVSKY

(KUNOVSKY @ FIT. VUTBR. CZ)

- 1) LINEAR CIRCUITS (R, L, C
+ OPERATIONAL
AMPLIFIER)
- 2) NONLINEAR CIRCUITS (μ IC, TRANSISTOR
GATES (NAND, NOR)
REGISTERS (F-Flip)
PROCESSORS (ALU)
CONTROLLERS + MEMORIES)


OPERATIONAL AMPLIFIER


U_g ... INPUT VOLTAGE

U_o ... OUTPUT VOLTAGE

A .. GAIN

- (minus) \equiv INVERSE OF VOLTAGE

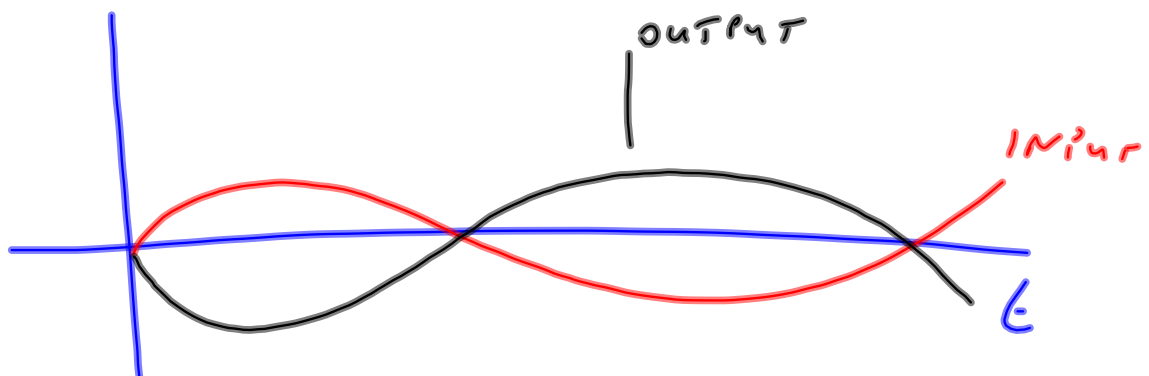

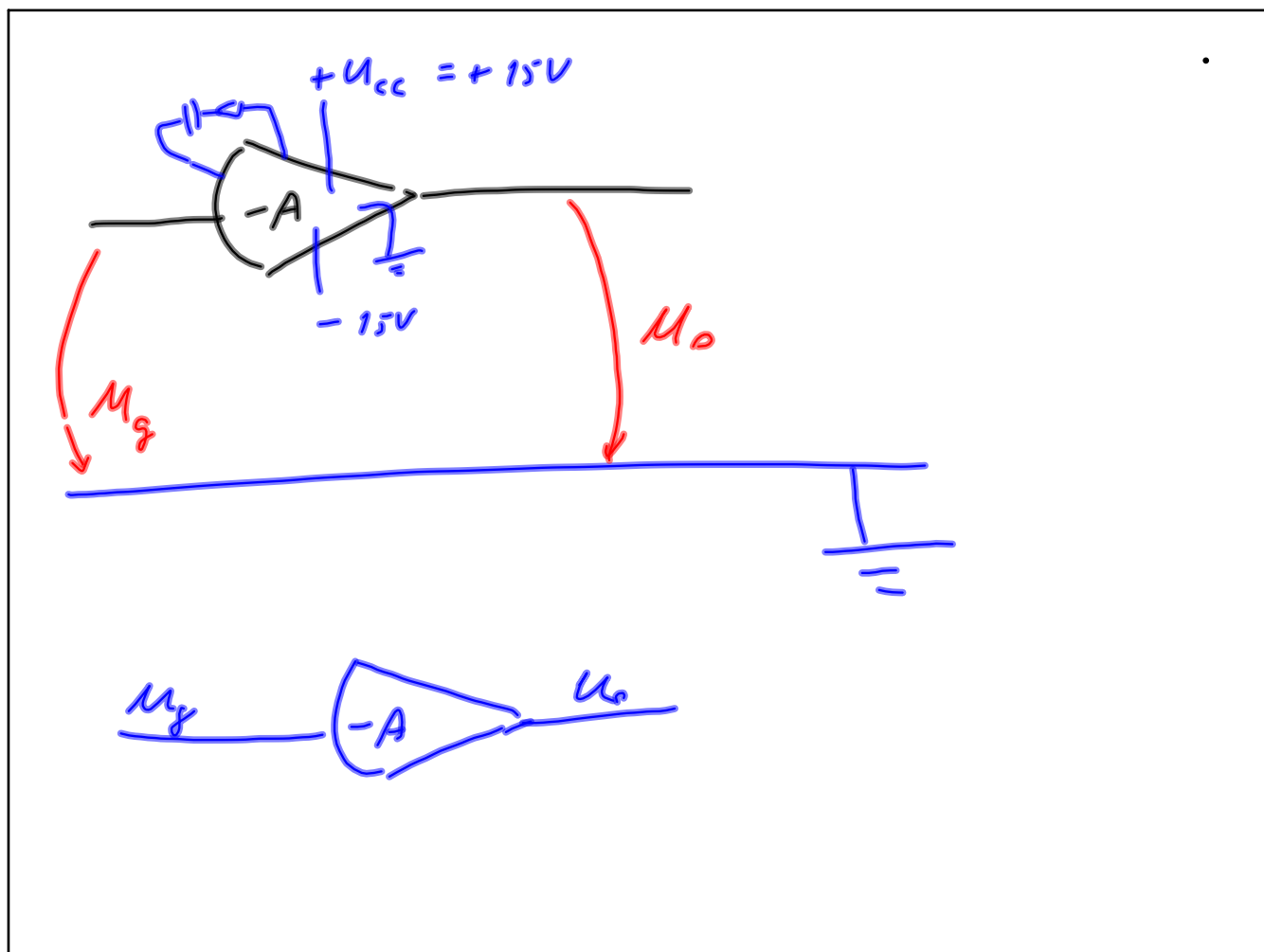


PROPERTIES OF OA

1) $A \rightarrow \infty$

2) R_{IN} (INPUT RESISTANCE) $\rightarrow \infty \Omega$

3) R_{OUT} (OUTPUT RESISTANCE) $\rightarrow 0 \Omega$

PRACTICAL EXAMPLES

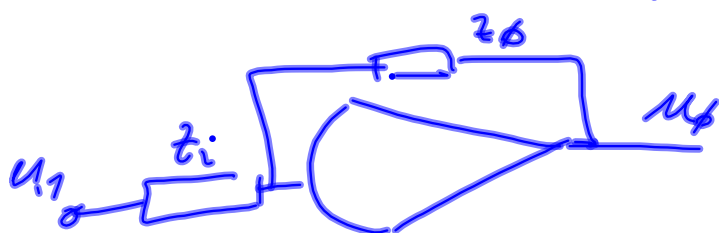

z_o ... FEEDBACK IMPEDANCE


z_i ... INPUT IMPEDANCE

$$u_o = f(u_i)$$

???

$$z_p = R_p \quad - \quad R_{\text{EIS}} \approx R$$
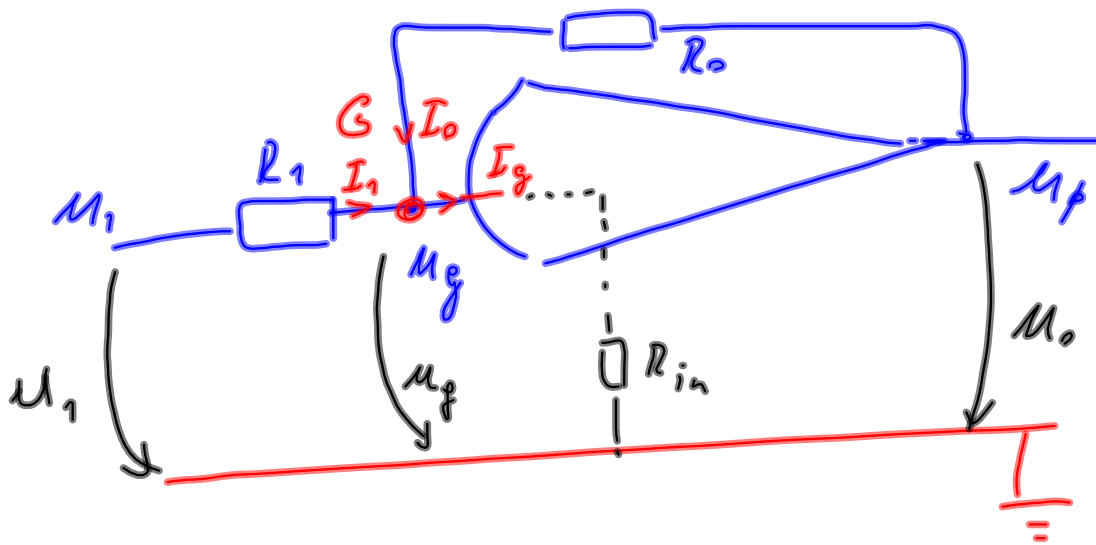
$$z_i = R_1 \quad \dots \quad - \quad - \quad -$$




$$I_1 + I_o = I_g$$

$$I_1 = \frac{U_1 - U_g}{R_1}$$

$$I_o = \frac{U_o - U_g}{R_o}$$

$$I_g = \frac{U_g}{R_{in}}$$
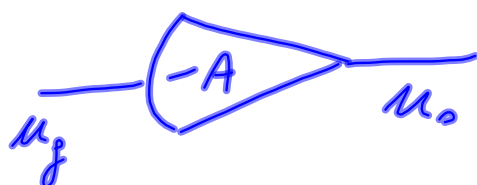
$$\frac{U_1 - U_g}{R_1} + \frac{U_o - U_g}{R_o} = \frac{U_g}{R_{in}}$$



$$U_o = -A \cdot U_g$$

$$U_g = \frac{U_o}{-A}$$

$$A \rightarrow \infty$$

$$U_g = 0$$

$$\left[\frac{u_1}{R_1} + \frac{u_o}{R_o} = 0 \right]$$

$$u_o = f(u_1)$$


$$u_o = -u_1 \frac{R_o}{R_1}$$

VERY OFTEN $R_o = R_1 = R$

$$\underline{\underline{u_o = -u_1 \cdot \frac{R_o}{R_1}}}$$

INVERSE OF SIGN


SYMBOL FOR INVERTOR.

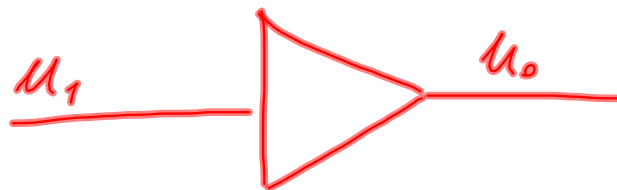

$$u_o = -u_1$$

$$u_o = -2 u_i \quad ??$$

$$\frac{R_o}{R_i} = 2$$

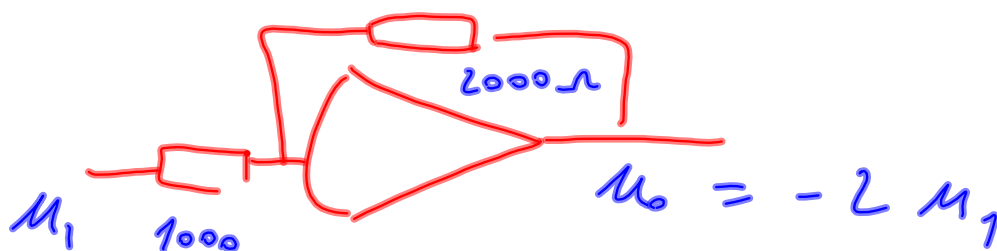

How to solve



$$U_0 = -0.231 U_1$$

$$\frac{R_0}{R_1}$$

$$R_1 = 1000 \Omega$$


$$R_0 = 231 \Omega$$

USING POTENTIALS

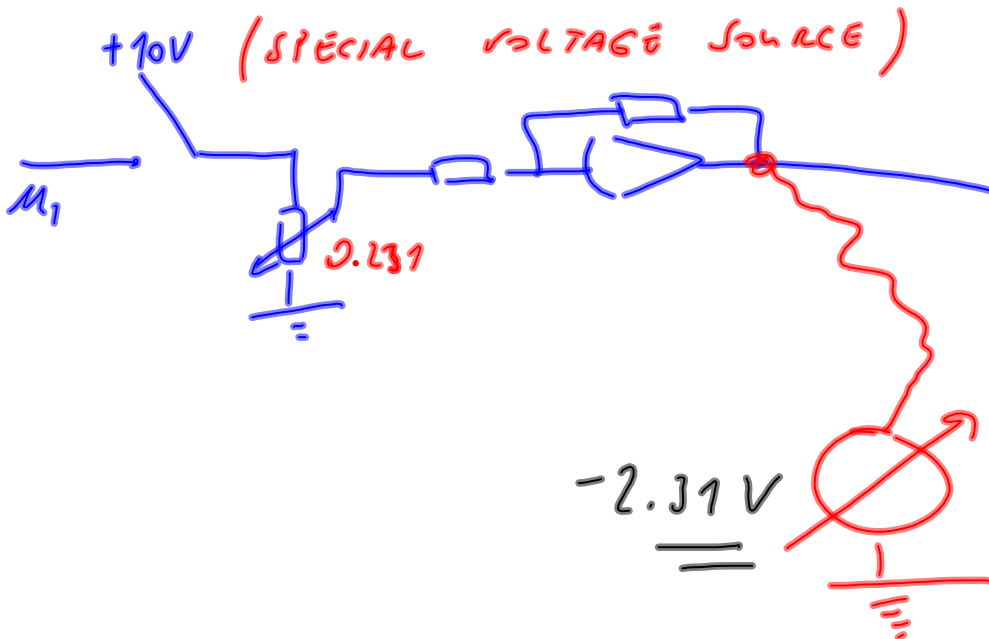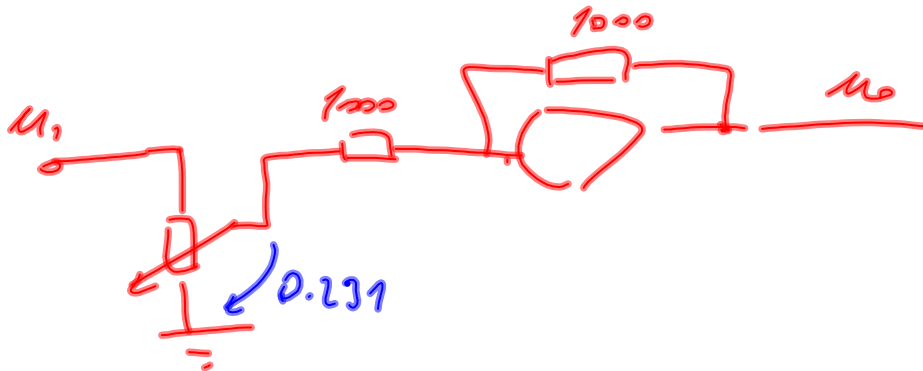

ALSO VOLTAGE SOURCE -10V


ΣΥΝΤΕΡ

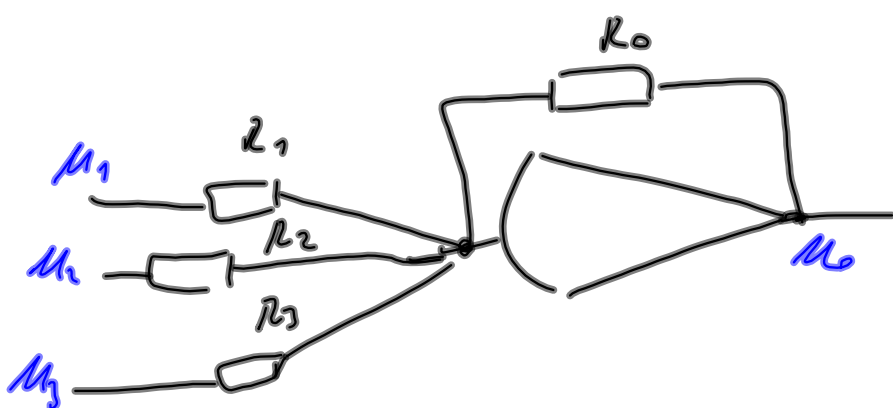


$$U_0 = -U_1 \frac{R_0}{R_1} - U_2 \frac{R_0}{R_2} - U_3 \frac{R_0}{R_3}$$

ΤΥΠ. ΑΛΛΓ

$$R_0 = R_1 = R_2 = R_3$$

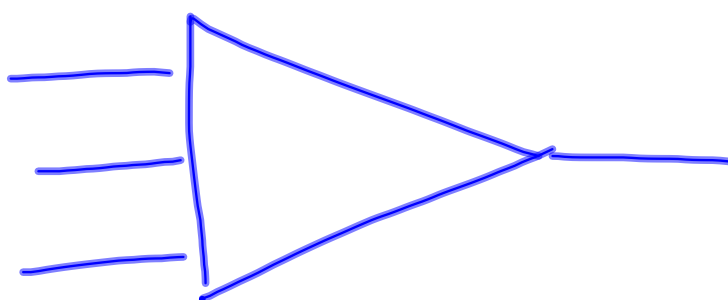

ALL EXAMPLES WERE
NOT TIME DEPENDENT

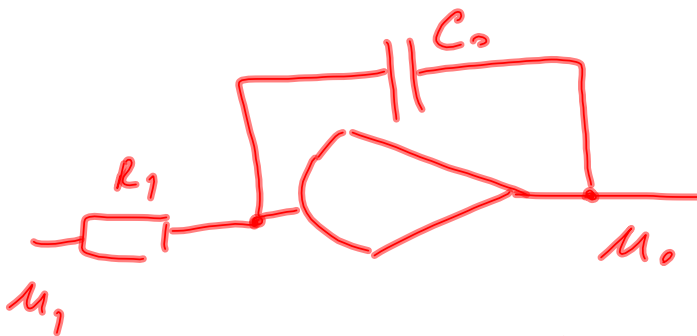


$$u_o(t) = -\frac{1}{R_1 C_0} \int u_1(t) dt + u_o(0)$$

AGAIN

$$\frac{1}{R_1 C_0} = 1 \quad \text{GAIN}$$


$$u_o(t) = -\int u_1(t) dt + u_o(0)$$

INITIAL
CONDITION

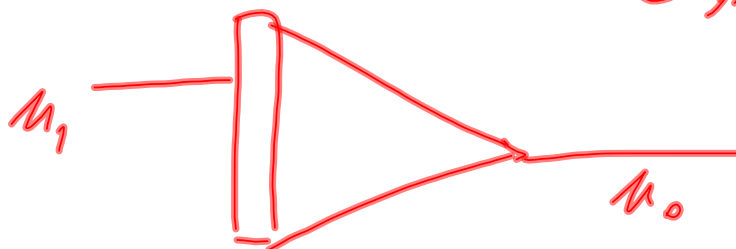

$$u_o = -\int u_1 dt + u_o$$
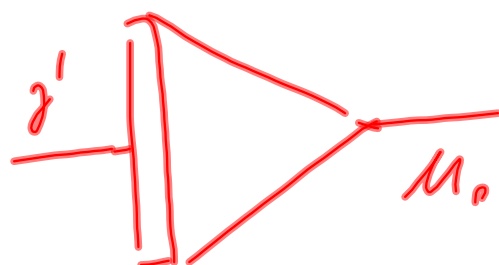
$$\boxed{\gamma' = \gamma \quad \gamma(0) = 1}$$






$$\boxed{u_o = \mathcal{D}}$$

$$\boxed{u_o = - \int \gamma' dt}$$

$$u_o = - \int \frac{d\gamma}{dt} dt$$

$$u_o = - \gamma$$

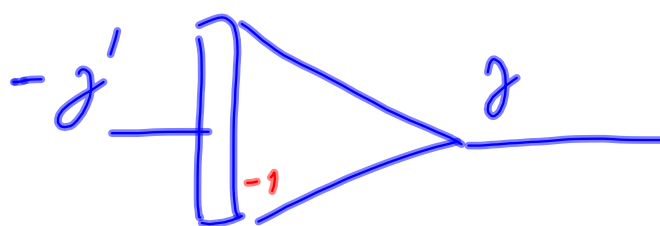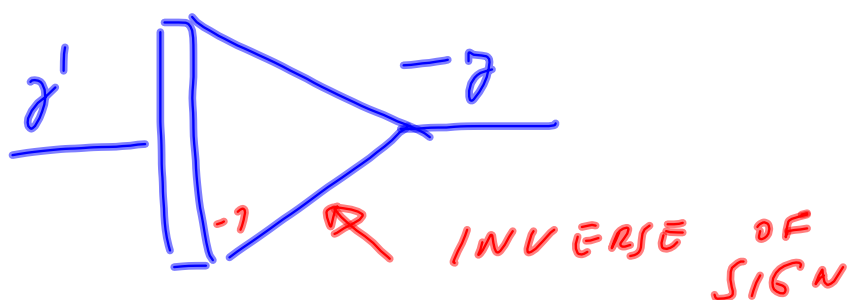

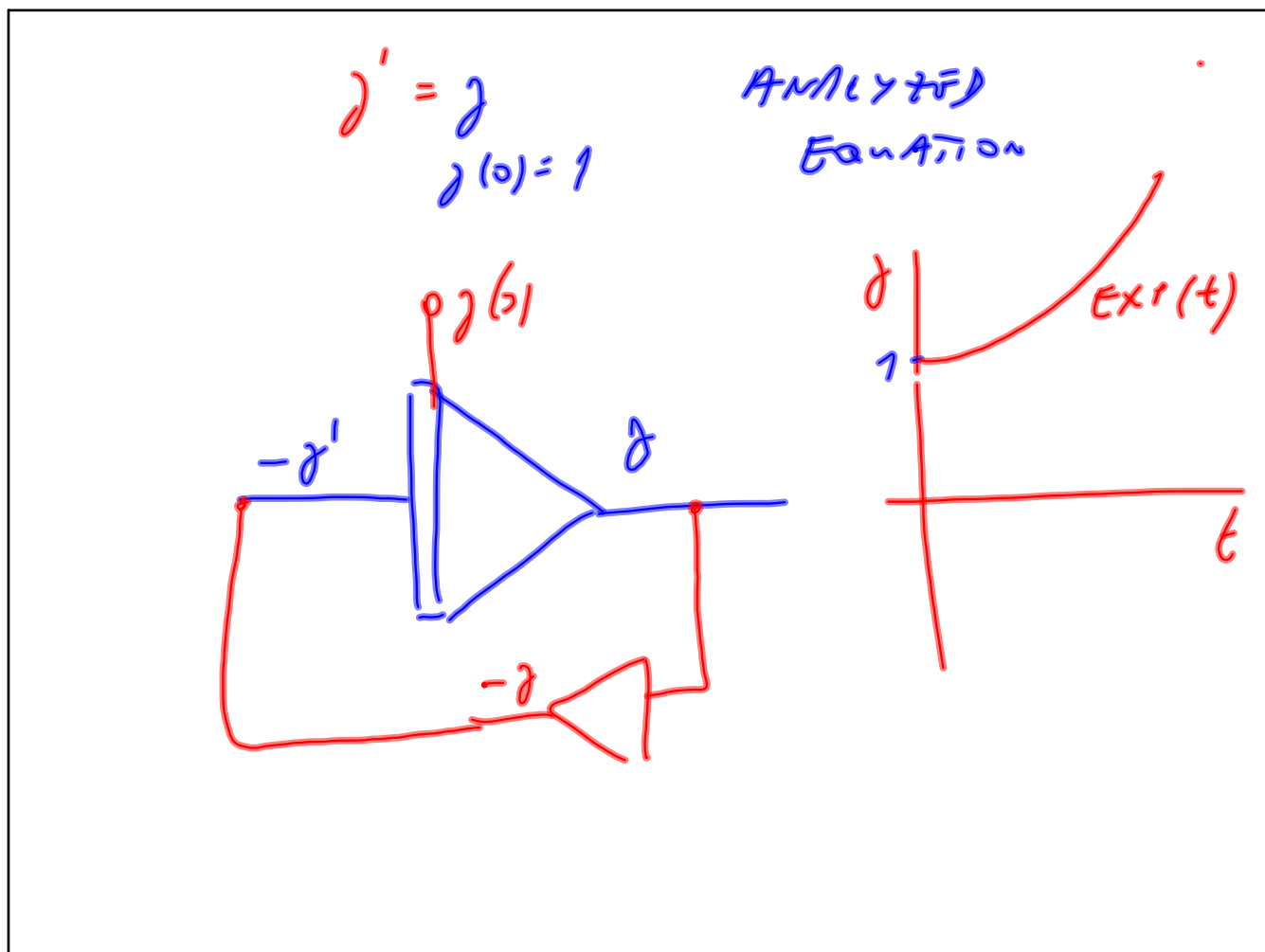

GENERATION OF FUNCTION

$$y = \sin t$$

$$y' = \cos t$$

$$v = \cos t$$

$$v' = -\sin t$$

$$\left[\begin{array}{l} y' = v \\ v' = -y \end{array} \right. \quad \left. \begin{array}{l} y(0) = 0 \\ v(0) = 1 \end{array} \right.$$

$$y = \sin t$$

