

Elektronika pro informační technologie (IEL)

First lab

Brno University of Technology, Faculty of Information Technology
Božetěchova 1/2, 612 66 Brno - Královo Pole
Petr Veigend, iveigend@fit.vutbr.cz




- Basic info
- What you need to know to not die here
- Introduction to the lab equipment
- Simple measurements (Ohms law, Kirchoffs law)

- Hi, my name is Petr
- You don't have to work alone, you can cooperate
 - **The important thing is to learn something new, understand something, etc.**
- Basically don't eat, drink, behave responsibly
- We are going to work with electricity and you all know that it harm you

LAB EQUIPMENT

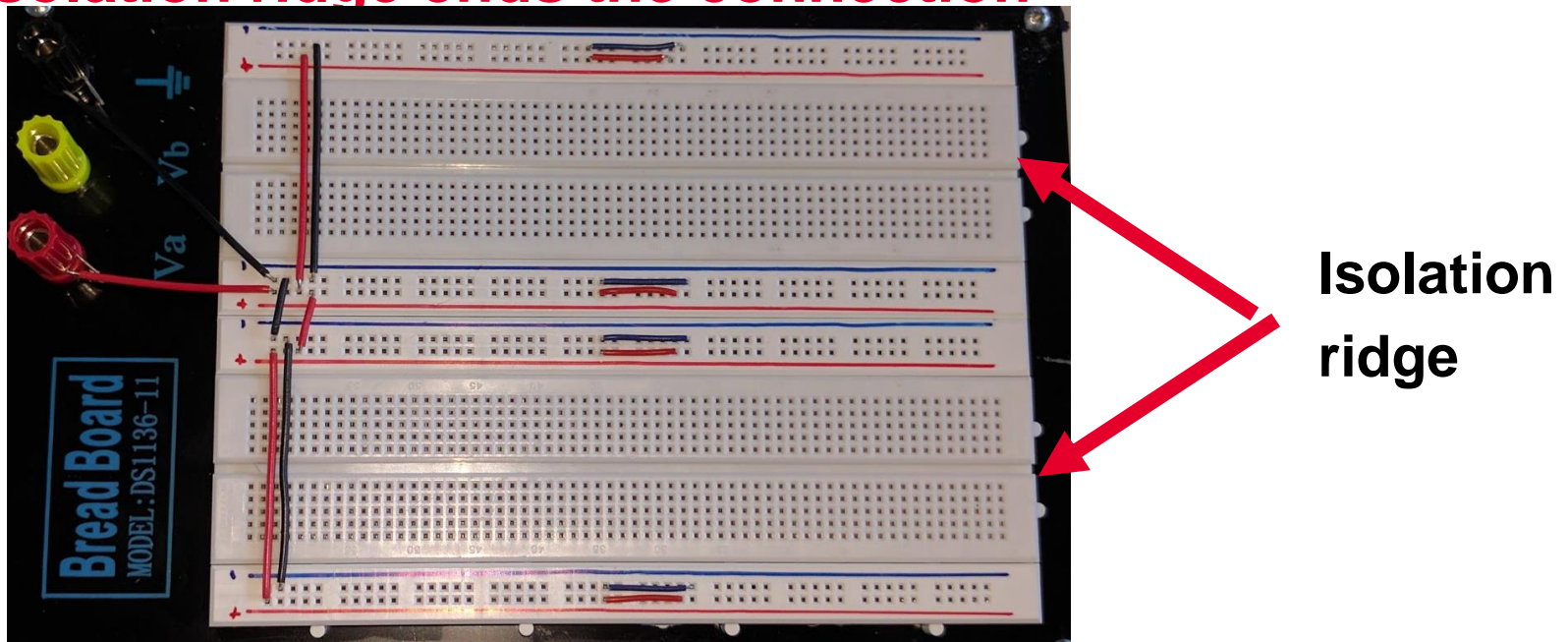- You will connect the parts using the solderless board and measure the voltages (or currents) using the multimeter
- Solderless board – **columns are conductively connected**
- **Isolation ridge ends the connection**



Set before the measurement



DCV
direct voltage

DCA
direct current

Ω
resistanc

Test wire

Ground (GND)

Measure (U, I, R)

- **Ohms Law**


$$U = R * I$$

- **U – voltage [V, Volt]**
- **R – resistance [Ω , Ohm]**
- **I – current [A, Ampér]**

• Kirchhoffs laws (KL)


- **1.st KL:** Algebraic sum of the currents in the node is equal to 0.

$$\sum_{k=1}^n I_k = 0$$

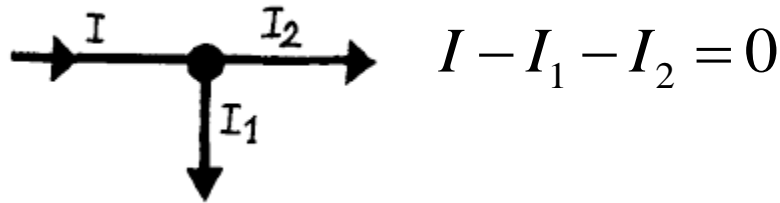

- **2. KZ:** Algebraic sum of the voltage in the closed loop is equal to 0.

$$\sum_{k=1}^n U_k = 0$$

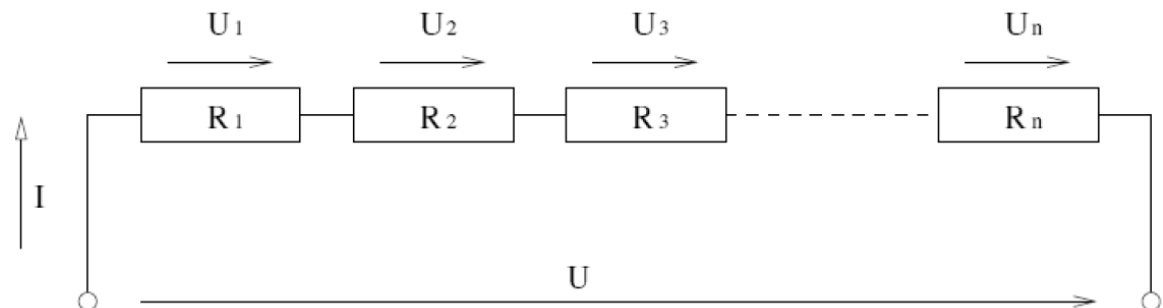

$$U_1 + U_2 + U_3 + \dots + U_n - U = 0$$

- Voltage divider (input voltage $U=5V$, 2 resistors R_1 , R_2)

Voltage on individual resistors (using Ohms Law)


$$U_{R1} = I \cdot R_1$$


$$U_{R2} = I \cdot R_2$$

Voltage (2.nd KL):

$$U - U_{R1} - U_{R2} = 0$$

$$U_{R1} + U_{R2} = U$$

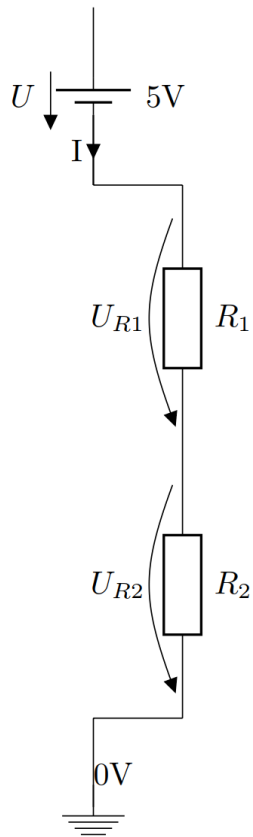

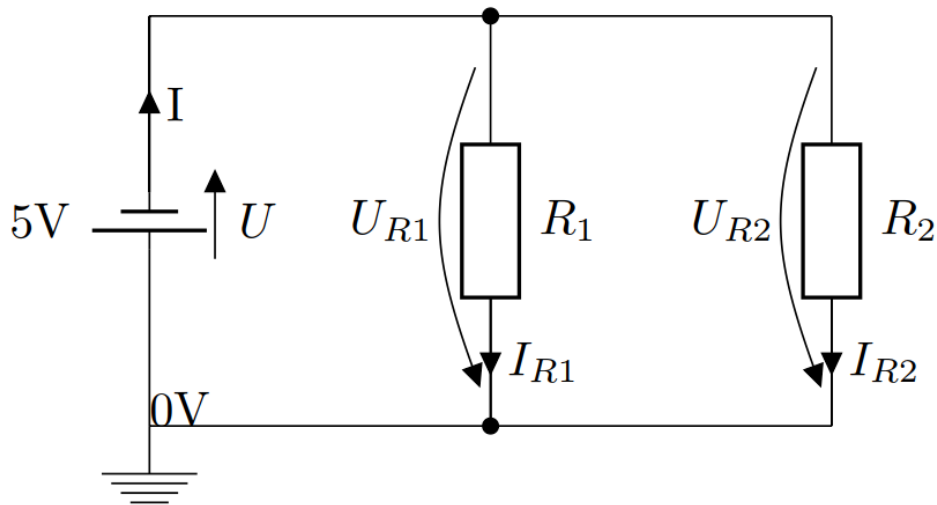

Current (1st. KL):

$$I - I_{R1} - I_{R2} = 0$$

$$I_{R1} + I_{R2} = I$$


Voltage (OL)

$$U_{R1} = I_{R1} \cdot R_1 \Rightarrow I_{R1} = \frac{U_{R1}}{R_1}$$


$$U_{R2} = I_{R2} \cdot R_2 \Rightarrow I_{R2} = \frac{U_{R2}}{R_2}$$

$$U_{R1} = U_{R2} = U$$

Measuring **voltage** (in parallel)

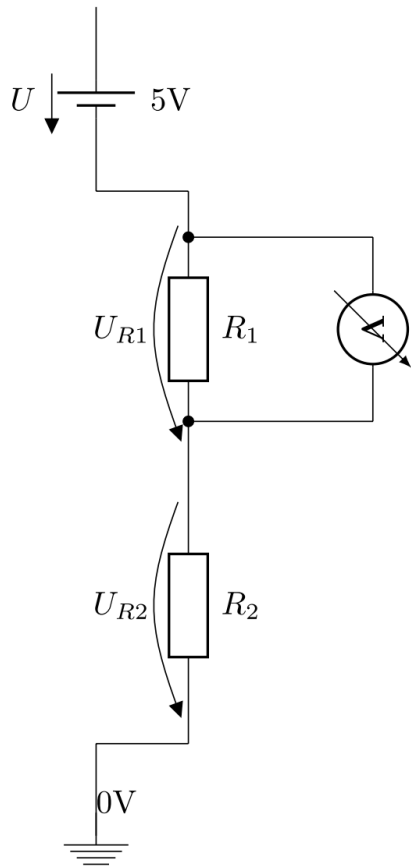


Measuring **current** (in series)

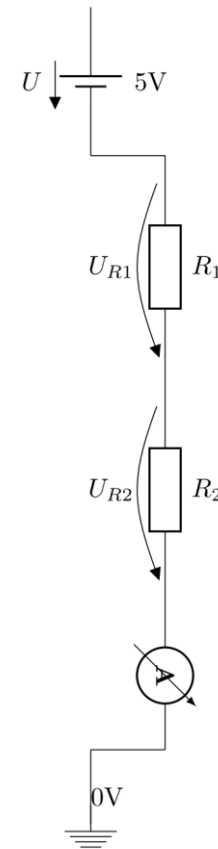

1ST EXPERIMENT


- Prepare a resistor, measure its **resistance (R)**
- Connect the following circuit, including the input voltage
- Measure the voltage (**U**) on the resistor
- Measure the current (**I**), that flows through the resistor

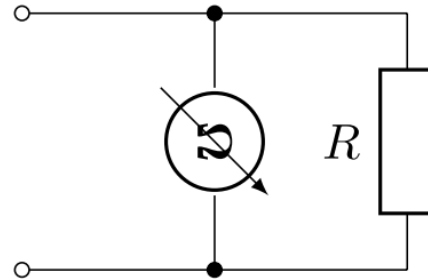- Connect the resistor into the solderless board and measure its resistance




- **Multimeter: Ω , 20k**
- Just connect the resistor to the different rows of the board and connect multimeter in **parallel**
 - 1st wire: $V\Omega mA \rightarrow$ resistor (same column)
 - 2nd wire COM \rightarrow resistor (same column)
- **Do not connect input voltage**

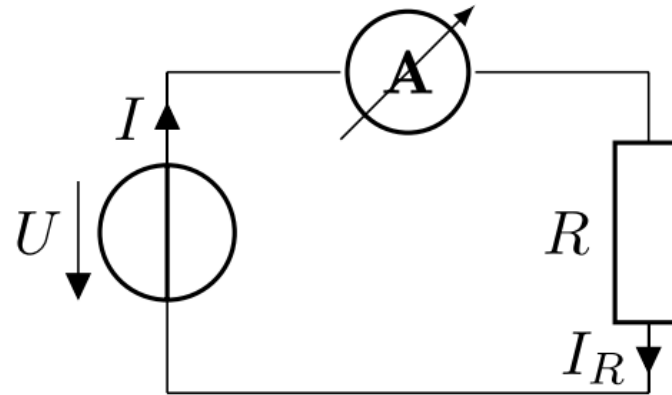- Connect the input voltage
- Connect the ampermeter into the circuit in the **series**



- **Measurement**
 - **Multimeter: A, 200mA**, set before connecting the input voltage
 - On one terminal of R : **5V, +**
 - On the second one: **0V, -**


- Connect the voltmeter in **parallel**

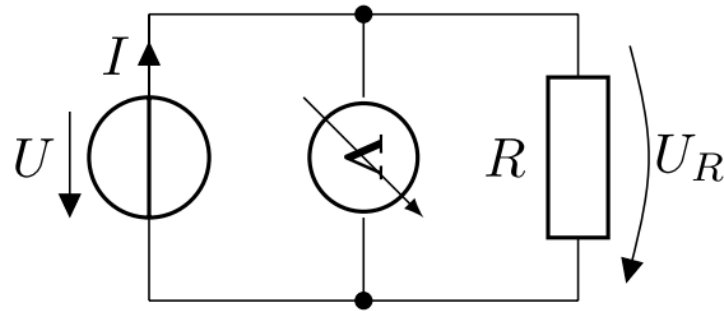

- **Measurement**

- **Multimeter: V, 20V**, set before connecting the input
- One terminal of R: **5V**
- Other terminal of R: **0V**
- **VΩmA**: same column as 5V
- **COM**: same column as **0V**


2ND EXPERIMENT

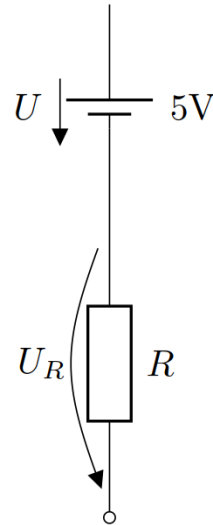


- **What is going to be the value of the voltage on the resistor? Why?**


3RD EXPERIMENT

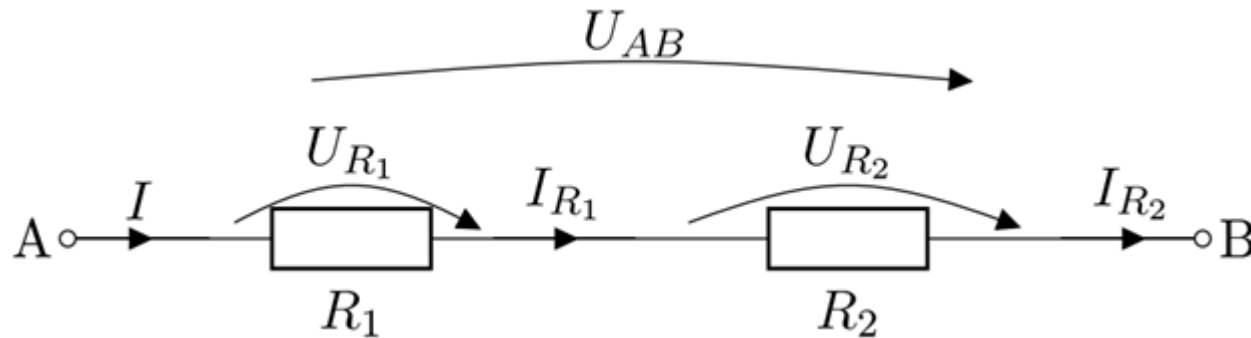- Connect the following circuit
 - Prepare two resistors (find out their resistances, if you don't know them already)
 - Connect the input voltage $U_{AB} = 5V$ and measure the voltages U_{R1} , U_{R2} and currents I_{R1} , I_{R2}



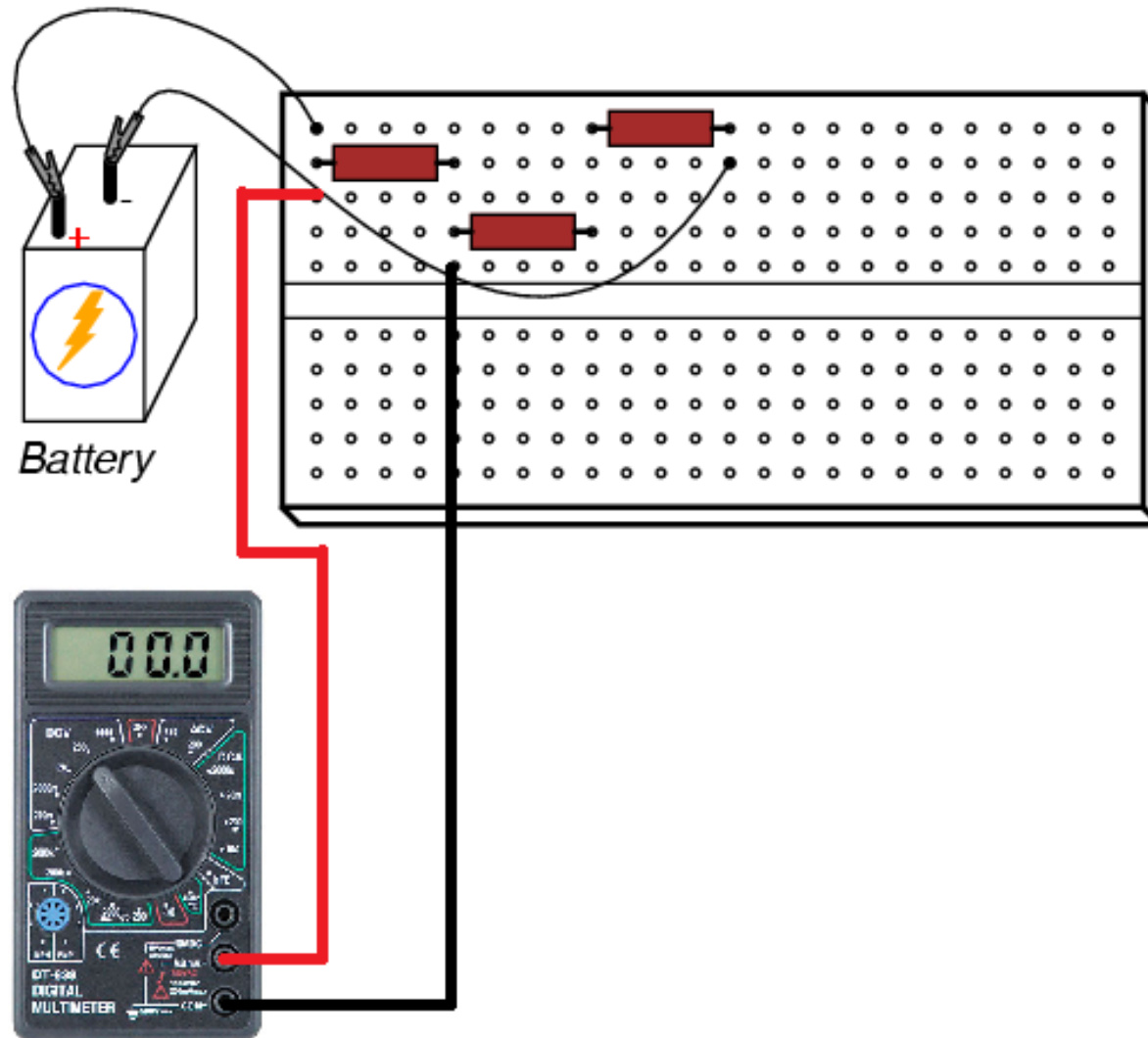

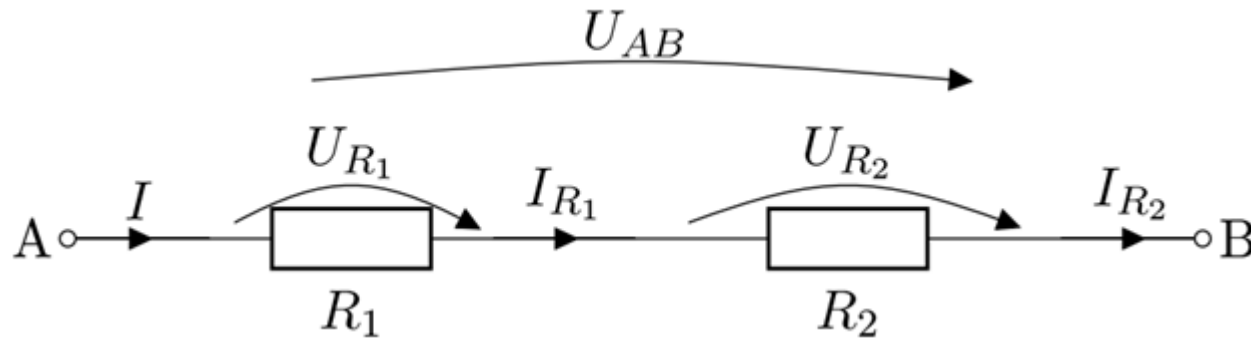- Connect the following circuit
 - Prepare two resistors (find out their resistances, if you don't know them already)
 - Connect the input voltage $U_{AB} = 5V$ and measure the voltages U_{R1} , U_{R2} and currents I_{R1} , I_{R2}



Thank you for your attention!