
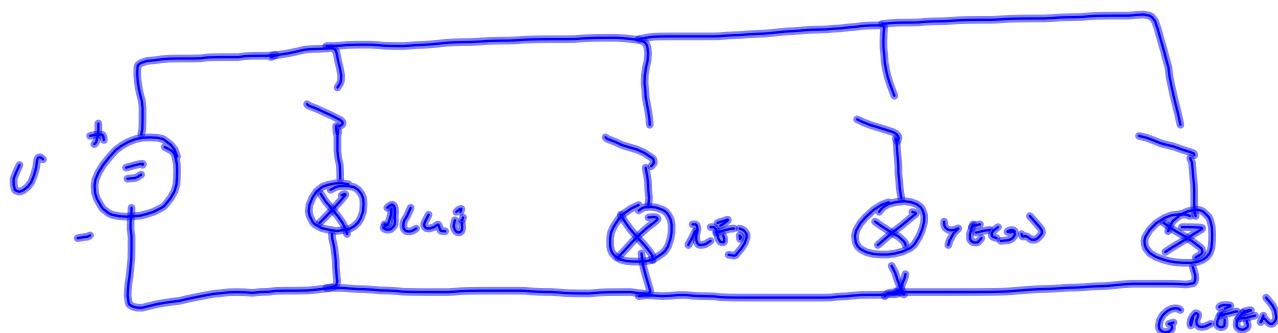




1ELE

JIRI KUNOVSKY

KUNOVSKY @ FIT.VUTBR.CZ

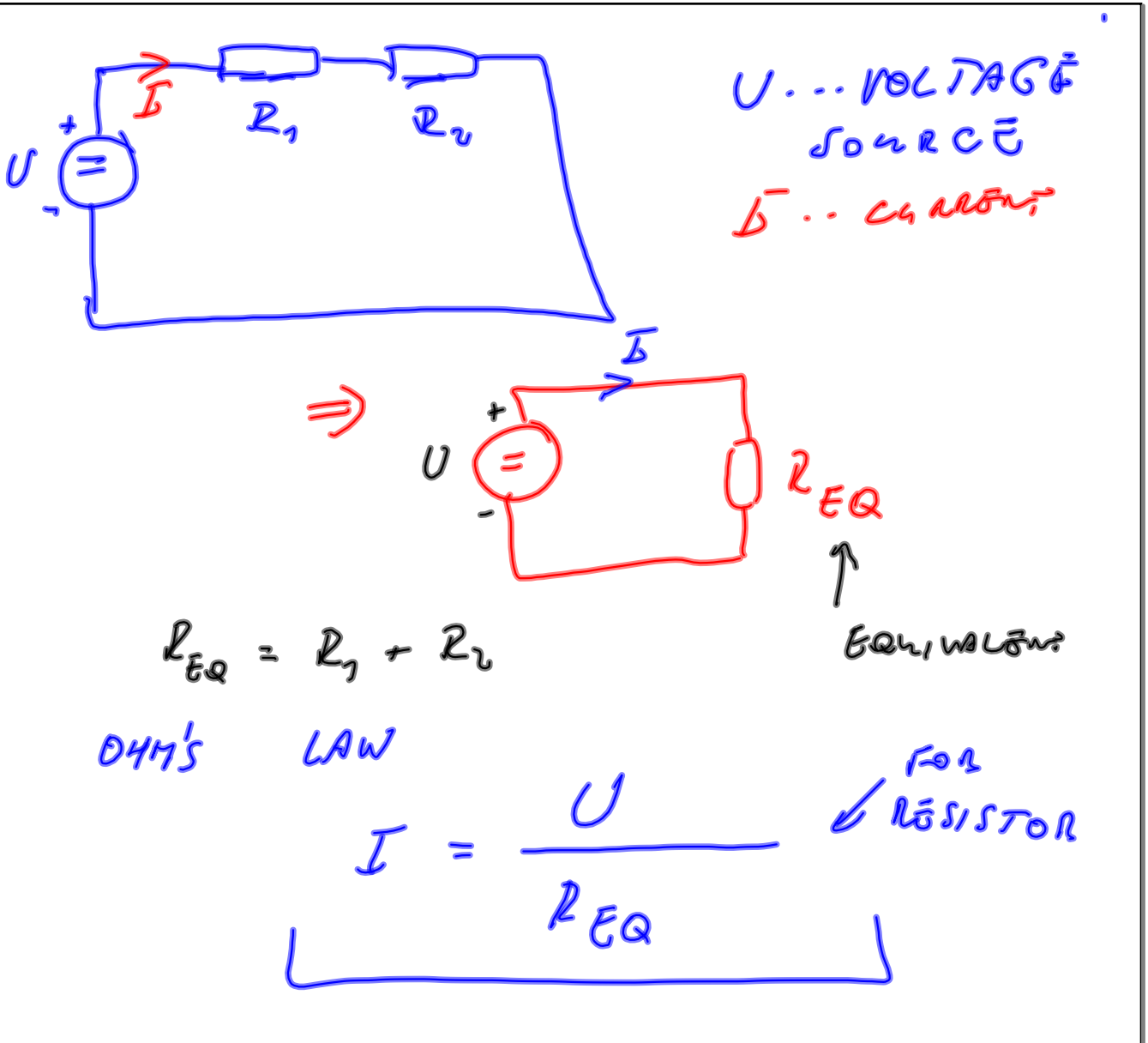



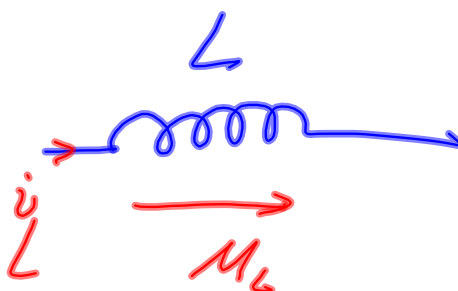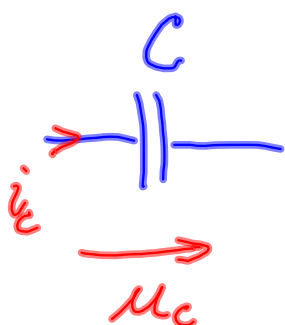



$$u_c = \frac{1}{C} i_c$$

$$i_L = \frac{1}{L} u_L$$


$$u_c = \frac{d u_c}{dt}$$

$$i_L = \frac{d i_L}{dt}$$

CIRCUIT WITH ONE SOURCE

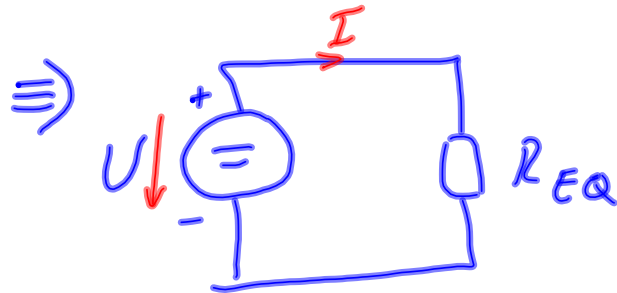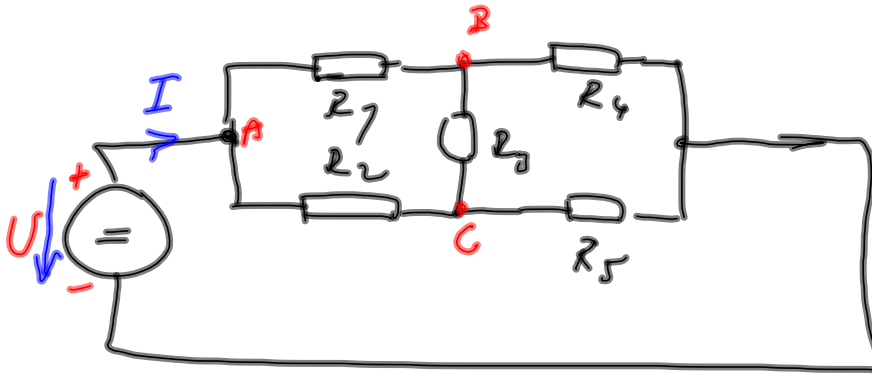

$$I = \frac{U}{R_{EQ}}$$

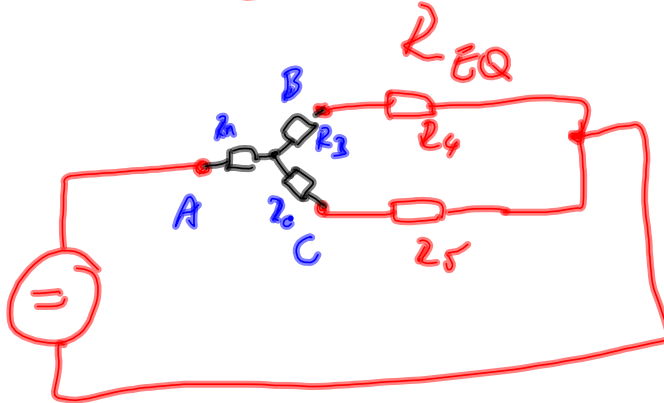


$$R_A = \frac{R_1 \cdot R_2}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_2 \cdot R_3}{R_1 + R_2 + R_3}$$


$$R_B = \frac{R_1 \cdot R_3}{R_1 + R_2 + R_3}$$

MORE VOLTAGE SOURCES

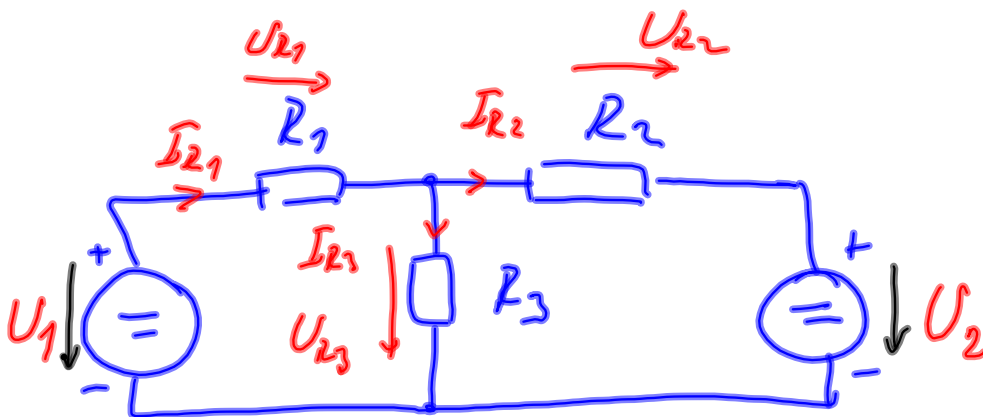

$$I_{R1}, I_{R2}, I_{R3} \equiv ??$$

$$U_{R1}, U_{R2}, U_{R3} \equiv ?$$

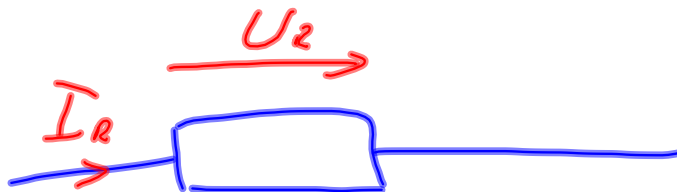

$U_{R1} = \bar{I}_A \cdot R_1$
 $U_{R3} = R_3 (\bar{I}_A - \bar{I}_B)$

$\bar{I}_A = ?$ $\bar{I}_B = ?$

II. KIRCHHOFF'S LAW
 $\Sigma \text{ VOLTAGES IN LOOP} = \emptyset$

Loop A: $U_{R1} + U_{R3} - U_1 = \emptyset$

$R_1 \cdot \bar{I}_A + R_3 (\bar{I}_A - \bar{I}_B) - U_1 = \emptyset$

Loop B
 $U_{R2} + U_2 - U_{R3} = \emptyset$

$R_2 \bar{I}_B + U_2 - R_3 (\bar{I}_A - \bar{I}_B) = \emptyset$


TWO EQUATIONS FOR TWO UNKNOWN
 $\Rightarrow \underline{\bar{I}_A}, \underline{\bar{I}_B}$

FINAL QUESTION
 $\bar{I}_{R1}, \bar{I}_{R2}, \bar{I}_{R3} = ?$

$\bar{I}_{R1} = \bar{I}_A$
 $\bar{I}_{R2} = \bar{I}_B$
 $\bar{I}_{R3} = \bar{I}_A - \bar{I}_B$

NOJĚ RŮTNOJ


$$U_A = ?$$

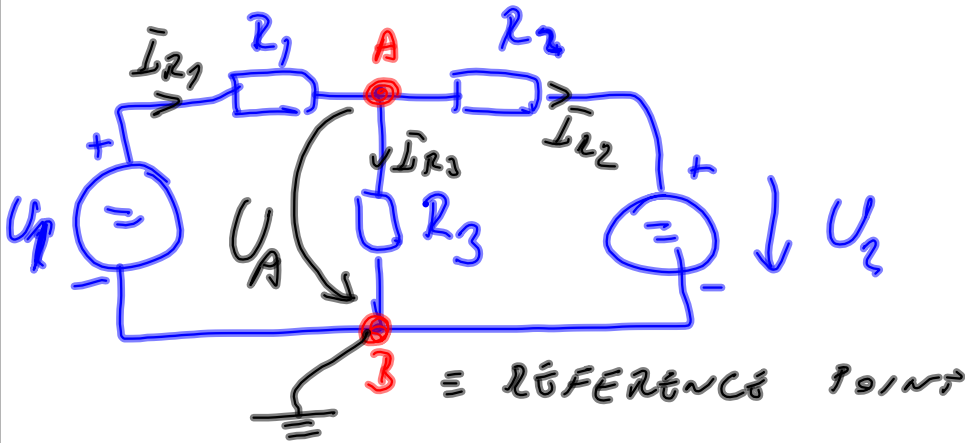

NOJĚ \equiv AT LEAST 3 ELEMENTS ARE CONNECTED

$$I_{R1} = I_{R2} + I_{R3}$$


EQUIVALENT CIRCUIT FOR I_{R1}

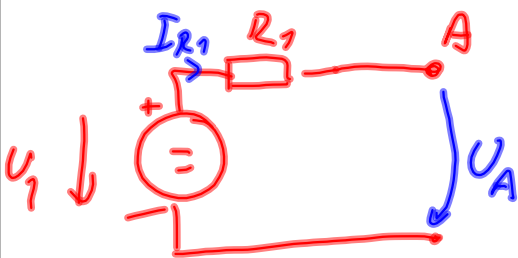

$$I_{R1} \cdot R_1 + U_A - U_1 = 0$$


$$I_{R1} = \frac{U_1 - U_A}{R_1}$$


CIRCUIT FOR \bar{I}_{R_2}

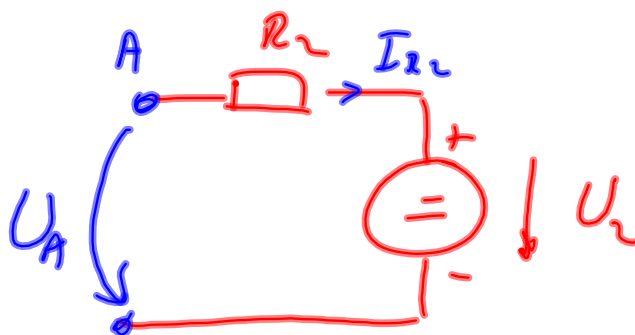


$$R_2 \cdot I_{R_2} + U_2 - U_A = 0$$

$$I_{R_2} = \frac{U_A - U_2}{R_2}$$

 


 

 



For I_{R_3}

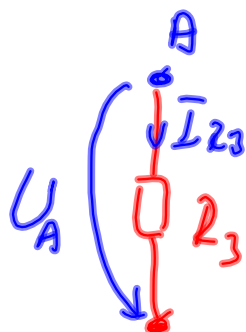

$$I_{R_3} = \frac{U_A}{R_3}$$

$$I_{R_1} = I_{R_2} + I_{R_3}$$

$$\frac{U_1 - U_A}{R_1} = \frac{U_A - U_2}{R_2} + \frac{U_A}{R_3}$$

ONLY

↑ UNKNOWN

U_A

