
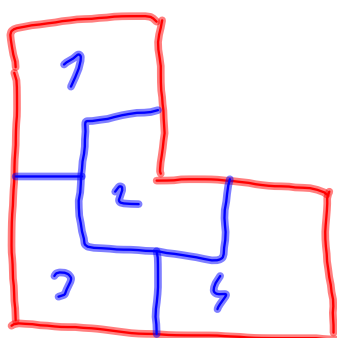


IEL 2016

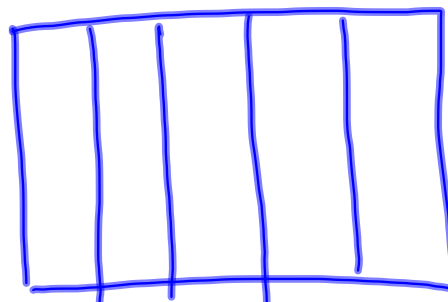


4 PARTS




5 PARTS

R L C CIRCUITS

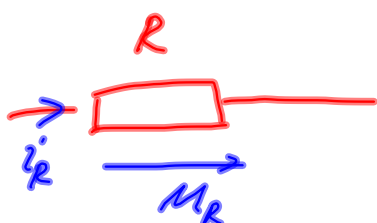

OHM'S LAW


$$i_R = \frac{M_R}{R}$$

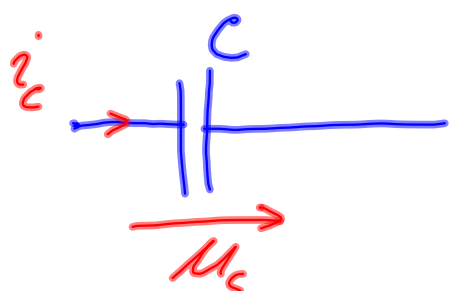

$$u_c' = \frac{1}{C} i_c$$

$$u_c' = \frac{d u_c}{dt}$$


"Ohm's LAW"

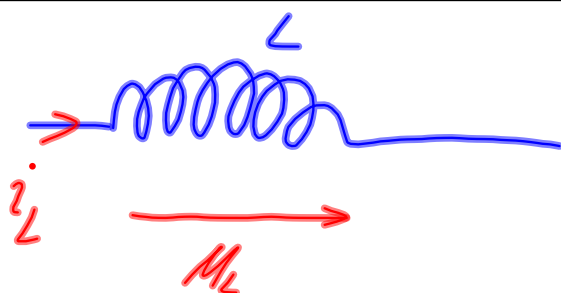

$$i_L' = \frac{1}{L} M_L$$

$$i_L' = \frac{d i_L}{dt}$$

C and L ARE TIME
DEPENDENT

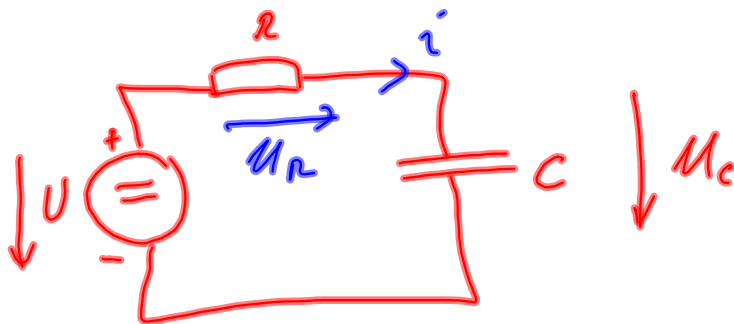

TASK IS TO FIND $U_C = ?$

$U_R = ?$


$i = ?$

AXIOM 1


WHEN CIRCUITS CONSISTS OF CAPACITANCE

THEN WE CONSTRUCT

DIFFERENTIAL EQUATION FOR $U_C' = ?$

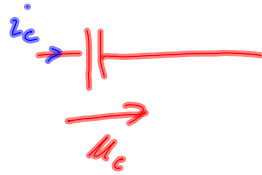

$$u_c' = \frac{1}{C} i_c$$

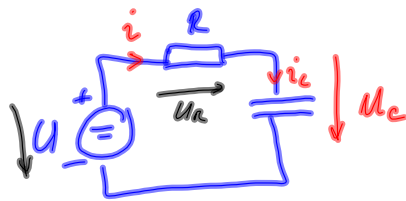

$$i = i_c$$

II. KIRCHHOFF'S LAW

$$\sum U \text{ IN THE CLOSED LOOP} = 0$$

$$u_R + u_c - U = 0$$

$$R \cdot i + u_c - U = 0$$

$$i = \frac{U - u_c}{R}$$

$$u_c' = \frac{1}{C} i \quad i_c = i$$

$$u_c' = \frac{1}{C} \frac{U - u_c}{R} \quad \underline{\underline{OK}}$$


$$\text{LET } R = 1 \Omega \quad C = 1 \text{ F}$$

$$U = 1 \text{ V}$$

INITIAL CONDITION

$$u_c' = 1 - u_c$$

$$u_c(0)$$

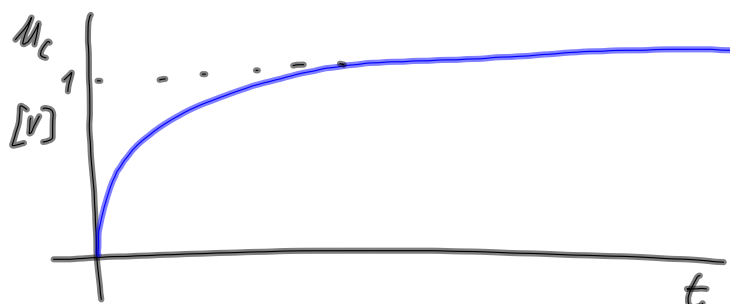

VERY SIMILAR R-L



AXIOM 2

WHEN CIRCUIT CONSISTS OF INDUCTANCES WE WILL CONSTRUCT DIFF. EQUATION IN FORM

$$i_2' = ?$$

OHM'S LAW FOR INDUCTANCE

$$i_2' = \frac{1}{L} M_L$$



II. KIRCHHOFF'S LAW FOR CIRCUIT

$$\sum U = 0 \text{ IN THE LOOP}$$

$$M_R + M_L - U = 0$$

$$R \cdot i_2 + M_L - U = 0$$


$$M_L = U - R \cdot i_2$$

$$i_2' = \frac{1}{L} (U - R \cdot i_2) \quad \text{OK} \checkmark$$


$$L = 1H \quad U = 1V \quad R = 1\Omega$$

$$i_2' = 1 - i_2 \quad \text{INITIAL CONDITION } i_2(0) = 0$$

FOR EXAMPLE

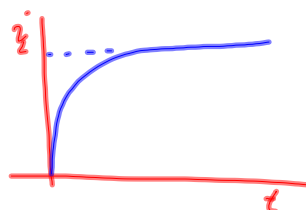

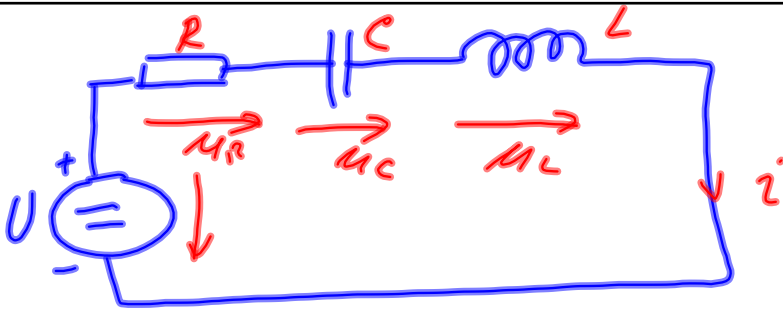$M_L' = 1 - M_L$
ANALYZED FOR CAPACITANCES



||

$$U_C' = ?$$

$$U_C' = \frac{1}{C} i \quad \text{I}$$

ok

$$i' = ?$$

$$i' = \frac{1}{L} U_L$$


$$U_R + U_L + U_C - U = 0$$

$$U_L = U - U_C - R \cdot i$$


$$i' = \frac{1}{L} (U - U_C - R \cdot i) \quad \text{II}$$

R L C ELEMENTS
CONNECTED TO HARMONICAL
VOLTAGE SOURCE


$$u = U_0 \sin \omega t$$

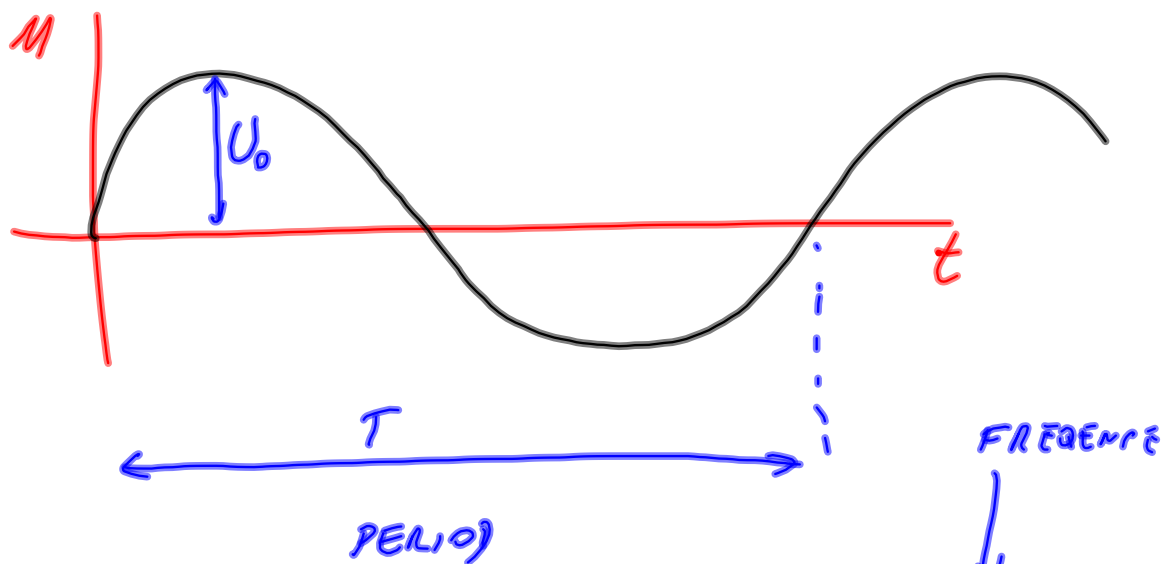


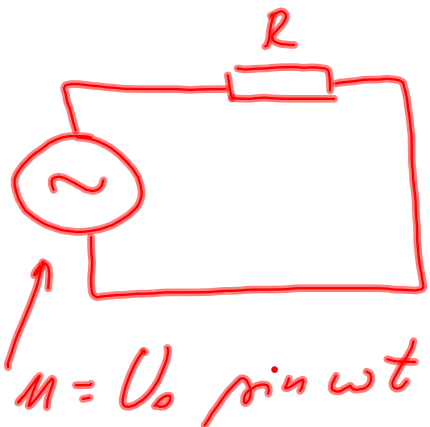
$$\omega = \frac{2\pi}{T} \quad \omega = 2\pi f$$




THE SAME
 \equiv R
 FOR ANY
 FREQUENCY

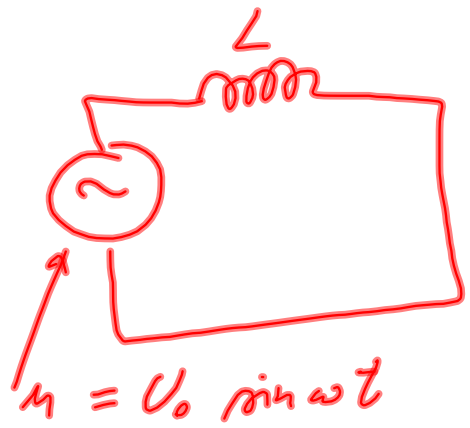


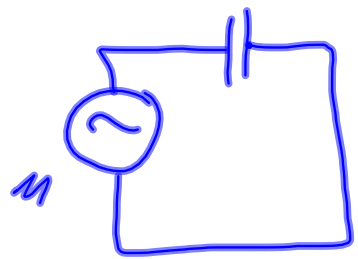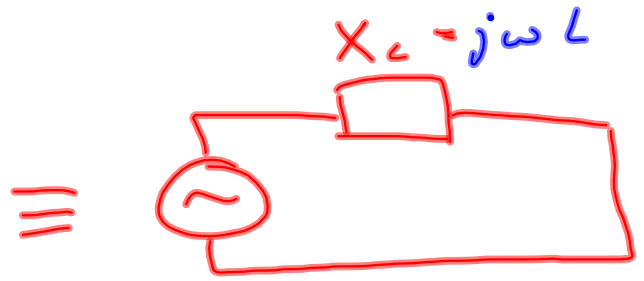
\equiv $X_L = j\omega L$
 ↑ COMPLEX
 VARIABLE




$u = U_0 \sin \omega t$

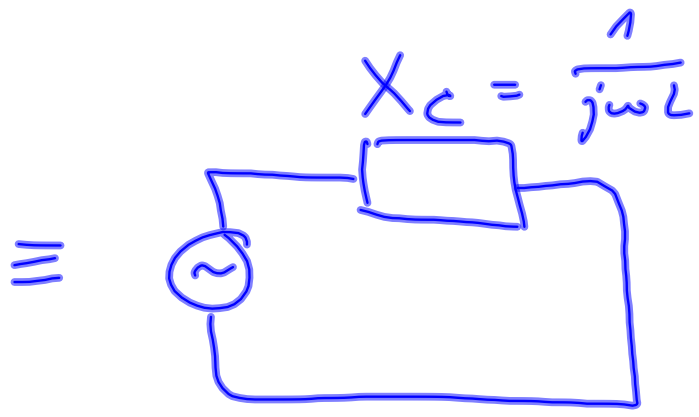

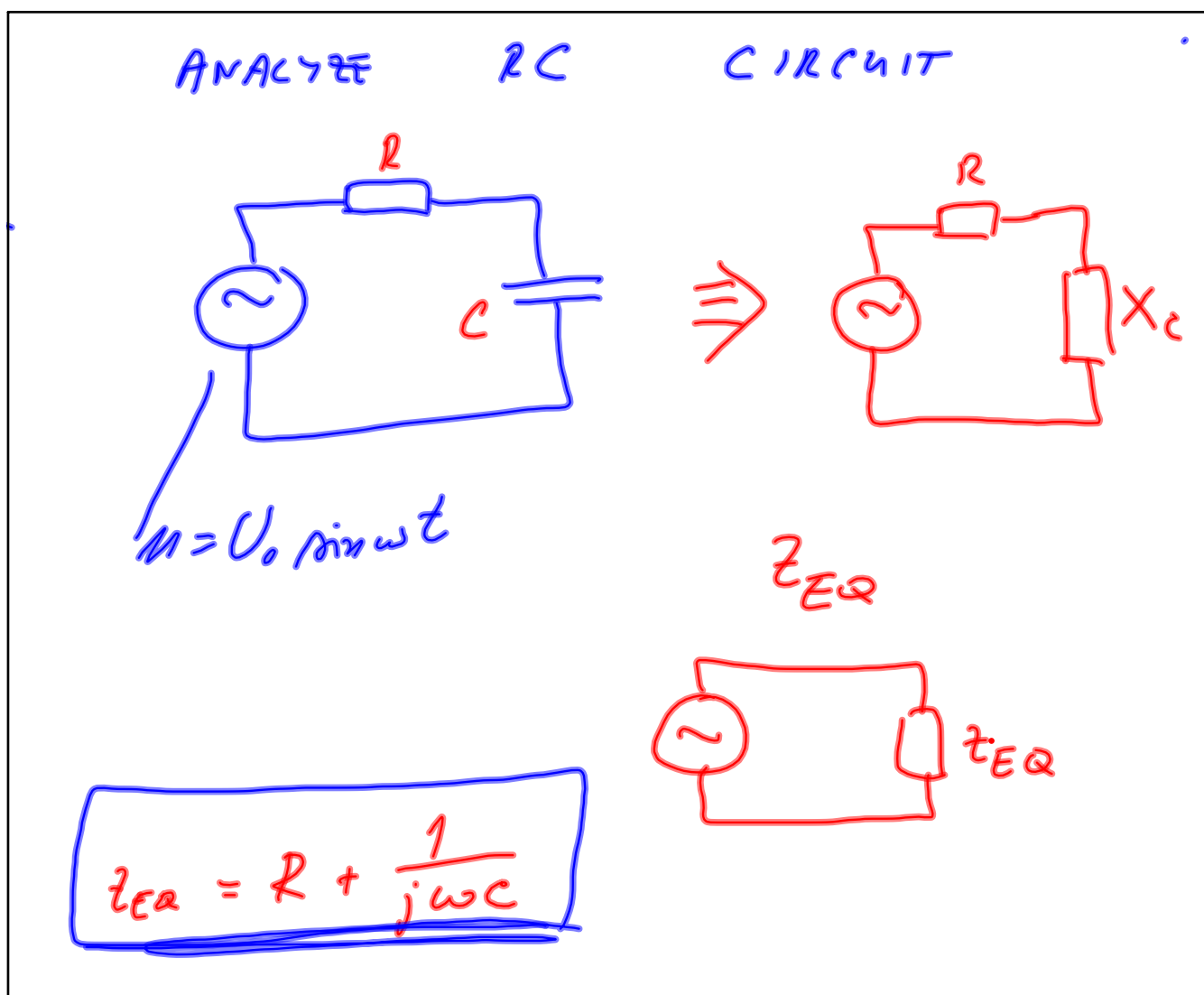


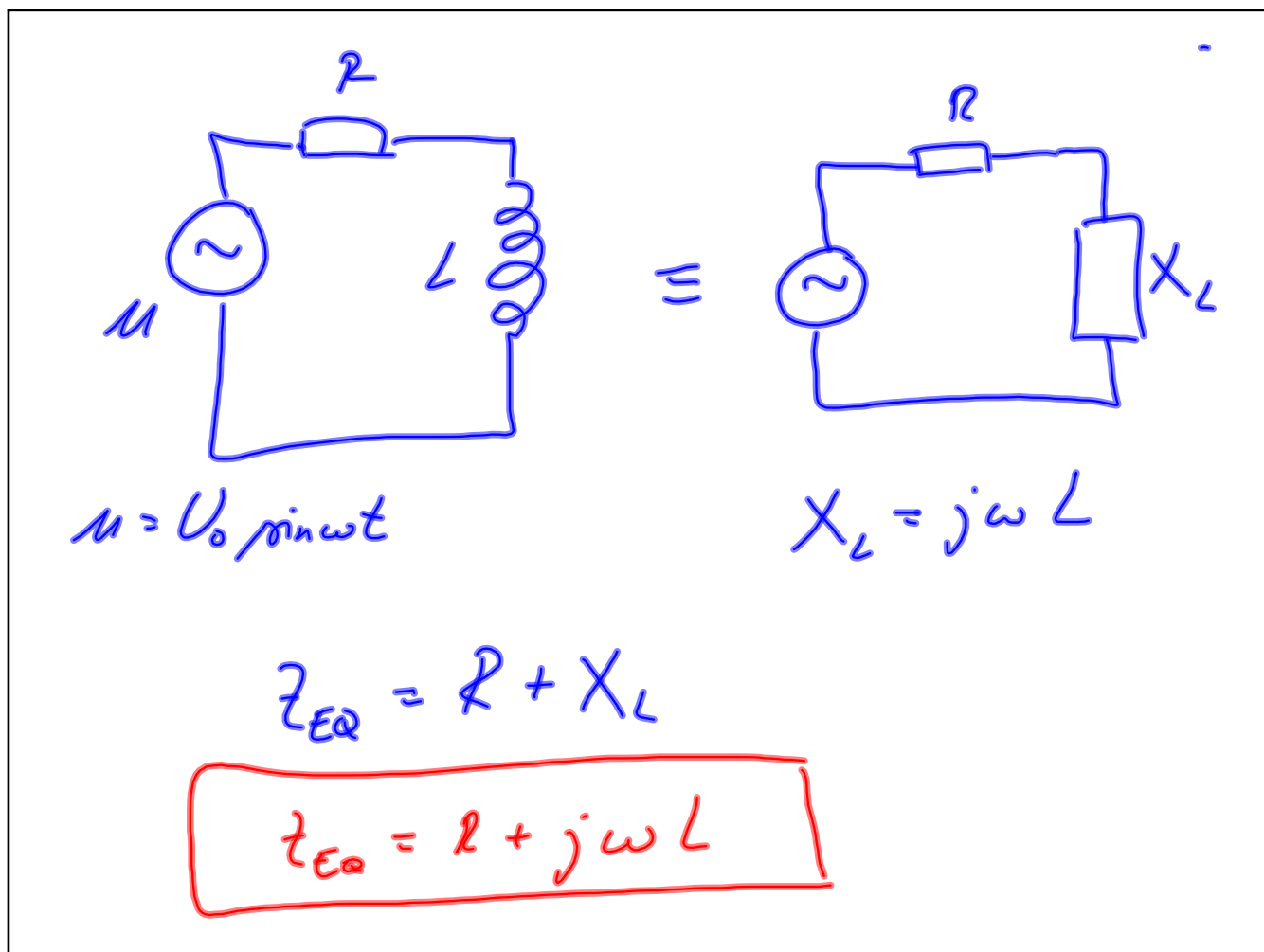


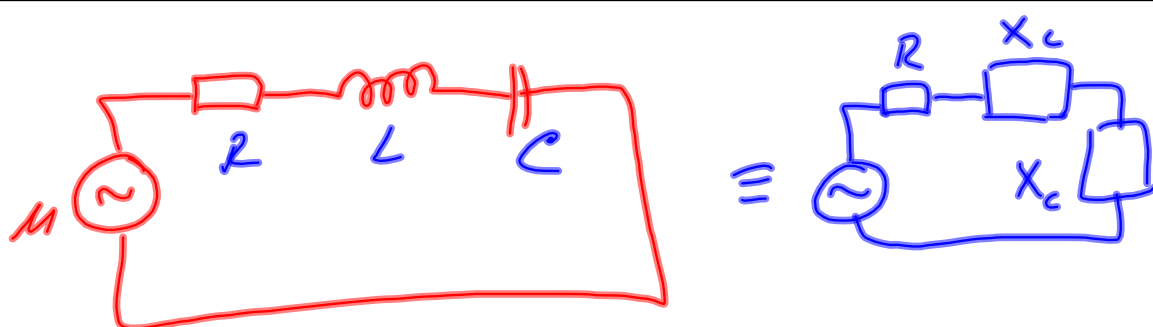




$$u = U_0 \sin \omega t$$

$$z_{EQ} = R + j\omega L + \frac{1}{j\omega C}$$

$$j \equiv$$

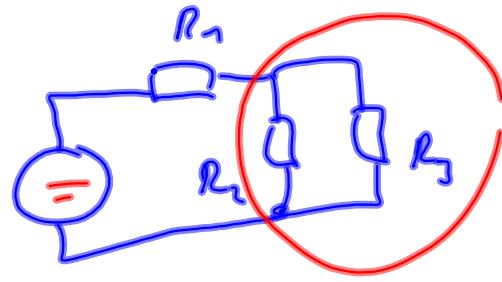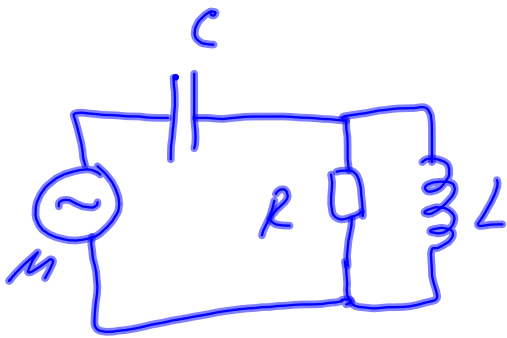


R_{EQ}

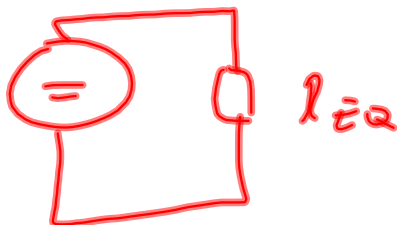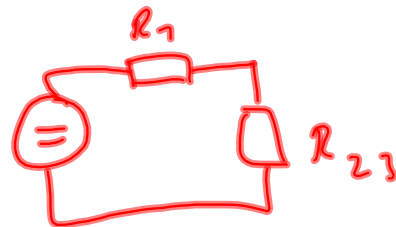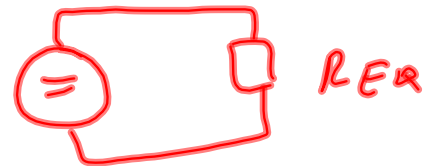

$$R_{13} = \frac{R_1 \cdot R_3}{R_1 + R_3}$$

$$R_{EQ} = R_1 + R_{23}$$

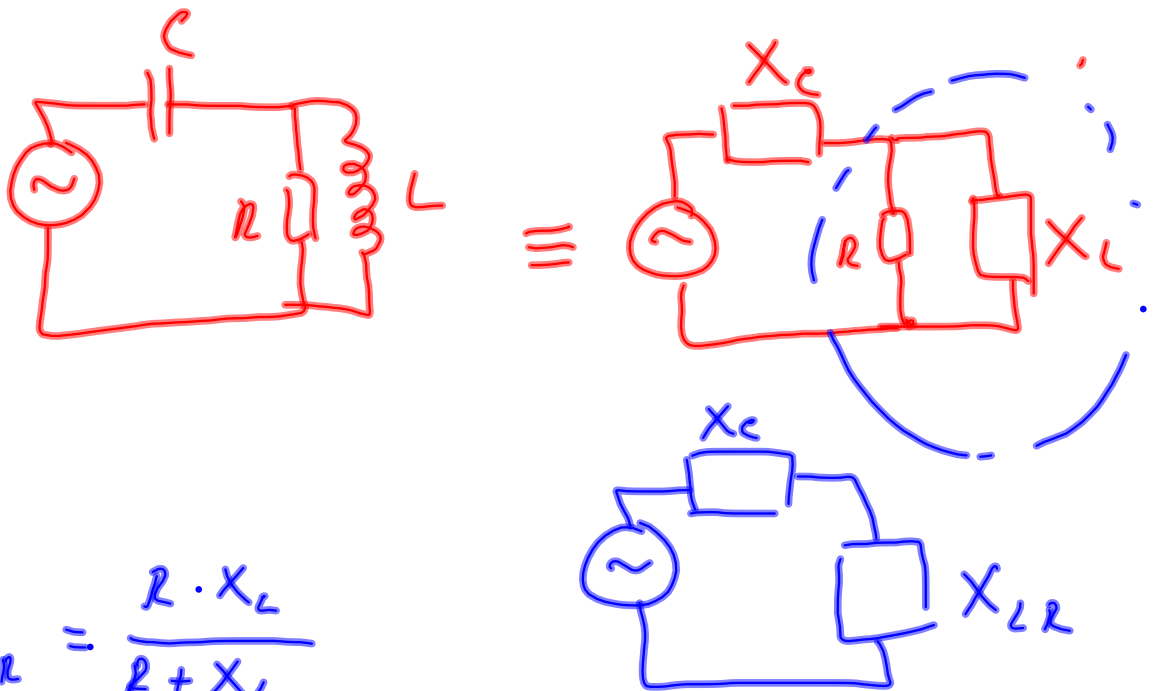

$$X_{LR} = \frac{R \cdot X_L}{R + X_L}$$

$$X_{LR} = \frac{R \cdot j\omega L}{R + j\omega L}$$

$$z_{EQ} = X_C + X_{LR}$$

$$z_{EQ} = \frac{1}{j\omega C} + \frac{R \cdot j\omega L}{R + j\omega L}$$

$$= A + j B$$

↑
REAL PART

—
IMAGINARY PART

SW

ELECTRONIC CIRCUITS
ANALYSIS

TKSL

SYSTEM



DEFINITION OF DIFF. EQUATION

SYSTEM

