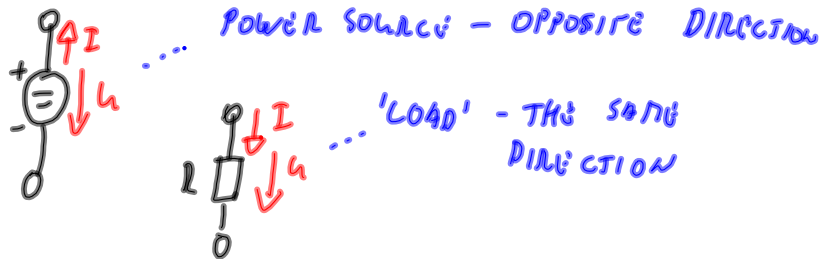



BASIC ELECTRIC CIRCUITS

CURRENT AND VOLTAGE ARROWS




CONNECTION OF THE SOURCES

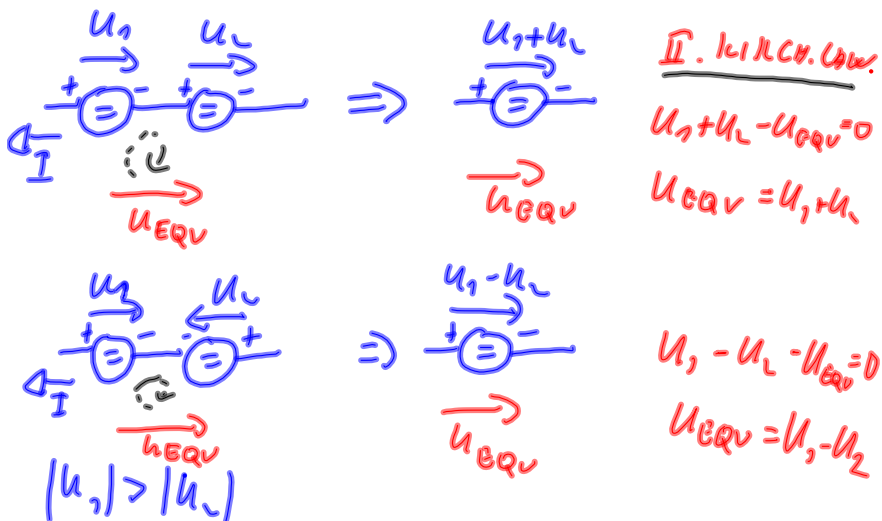1) SERIES - THE SAME CURRENT, SUMMATE VOLTAGES




2) PARALLEL - SUMMATE THE CURRENTS

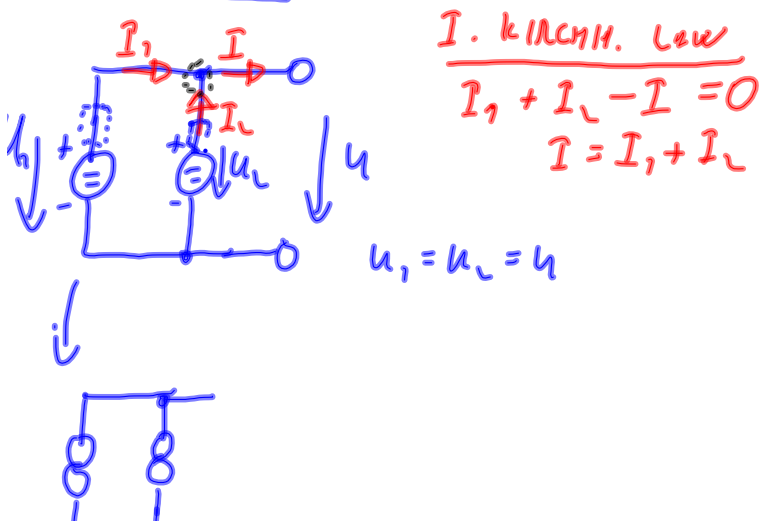

SIMPLE ELECTRIC CIRCUIT


- WITH 1 POWER SUPPLY

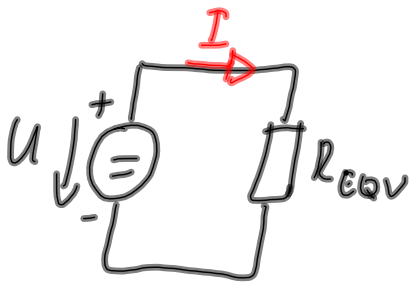

OHM'S LAW

$$I = \frac{U}{R_{eqv}}$$

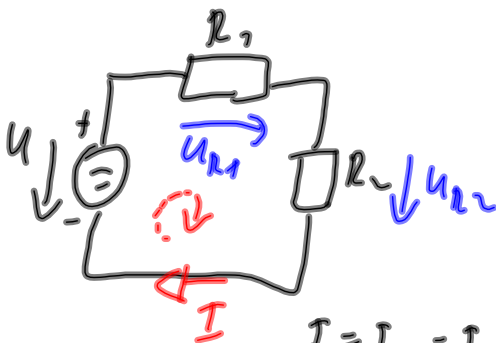1, RESISTORS IN SERIES ($R_{eqv} = R_1 + R_2$)



$$U_{R1} = R_1 \cdot I \quad \dots \quad \text{SAME CURRENT}$$

$$U_{R2} = R_2 \cdot I$$

$$I = \frac{U}{R_{eqv}} = \frac{U_{R1} + U_{R2}}{R_1 + R_2}$$

$$I = I_{R1} = I_{R2} \rightarrow I = \frac{U_{R1}}{R_1} = \frac{U_{R2}}{R_2}$$

II. KIRCH. LAW

$$U_{R1} + U_{R2} - U = 0$$

$$U = U_{R1} + U_{R2}$$

$$\left[\frac{U_{R1}}{U_{R2}} = \frac{R_1}{R_2} \right]$$

R_{eqv} IS LARGER THAN SOME
OF THE RESISTORS CONNECTED IN

SERIES

$$R_{eqv} = R_1 + R_2$$


↓

$$R_{eqv} > R_1$$

$$> R_2$$

⋮

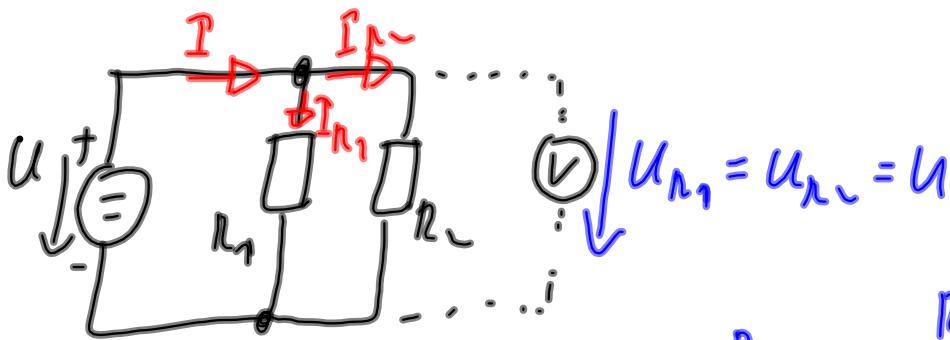2) PARALLEL CONNECTION OF
RESISTORS $\left(\frac{1}{R_{\text{EQV}}} = \frac{1}{R_1} + \frac{1}{R_2}\right)$



I . KIRCH-LAW

$$I - I_1 - I_2 = 0$$

$$R_{\text{EQV}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

R_{EQV} IS SMALLER THAN
 R_1, R_2

$$R_{\text{EQV}} < R_1$$

$$< R_2$$

$$\vdots$$

$$U = I_1 \cdot R_1 = I_2 \cdot R_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$