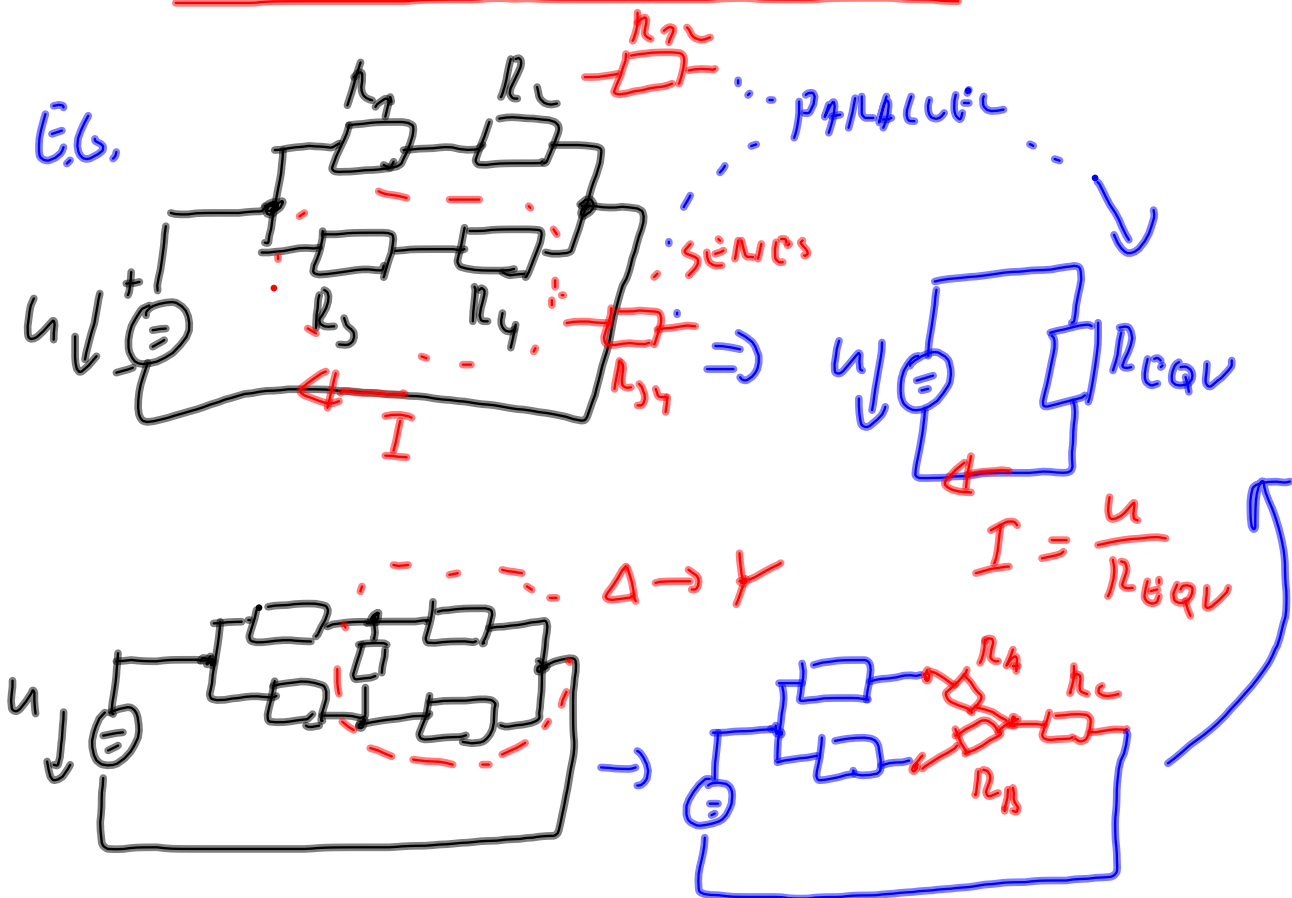


METHODS FOR SOLVING ELECTRICAL CIRCUITS

IEE
6.10.2017

a) METHODS FOR SOLVING THE ELEC. CIRCUITS WITH 1 POWER SUPPLY

→ METHOD OF SIMPLIFICATION



b) METHODS FOR SOLVING THE
EL. CIRCUITS WITH MORE POWER SUPPLIES

→ LOOP CURRENT METHOD


→ NODE VOLTAGE METHOD

→ THEVENIN'S THEOREM

SOLVING OF EL. CIRCUITS USING

SLAE (SYSTEM OF LINEAR ALGEBRAIC EQUATIONS)

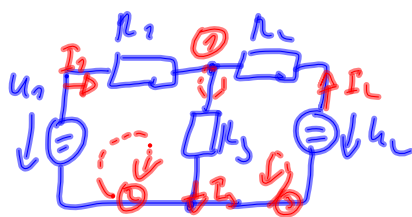Ex SOLVE THE EL. CIRCUIT USING KIRCHHOFF'S LAWS



PARAMETERS:

$$u_1 = 5V$$

$$u_2 = 20V$$

$$R_1 = 20\Omega$$

$$R_2 = 20\Omega$$

$$R_3 = 40\Omega$$

CONSTRUCTION OF SLAE:

$$\textcircled{1} I_1 + I_2 - I_3 = 0 \dots \text{I. KIRCHH. LAW}$$

$$\textcircled{2} R_1 \cdot I_1 + R_2 I_2 - u_1 = 0 \dots \text{II. K. L.}$$

$$\textcircled{3} R_2 I_2 + R_3 I_3 - u_2 = 0 \dots \text{I}_1, \text{I}_2, \text{I}_3 = ?$$

MATRIX-VECTOR NOTATION:

$$\begin{pmatrix} 1 & 1 & -1 \\ R_1 & 0 & R_2 \\ 0 & R_2 & R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ u_1 \\ u_2 \end{pmatrix}$$

→ SOLVING SLAE, E.G. CRAMER'S RULE

SOLVING DETERMINANTS USING

SARRUS RULE

$$D_5 = \begin{vmatrix} \textcircled{1} & \textcircled{2} & \textcircled{3} \\ 1 & 1 & -1 \\ R_1 & 0 & R_2 \\ 0 & R_2 & R_3 \end{vmatrix} = \textcircled{1} (1 \cdot 0 \cdot R_3) + \textcircled{2} (1 \cdot R_3 \cdot 0) + \textcircled{3} (-1 \cdot R_1 \cdot R_2) - (0 \cdot 0 \cdot (-1)) - (R_2 \cdot R_3 \cdot 1) - (R_3 \cdot R_1 \cdot 1)$$

$$D_{I_1} = \begin{vmatrix} 0 & 1 & -1 \\ u_1 & 0 & R_3 \\ u_2 & R_2 & R_3 \end{vmatrix} = R_3 u_2 - u_1 R_2 - R_3 u_1 =$$

$$= 800 - 100 - 200 = \underline{\underline{500}}$$

$$D_{I_2} = \begin{vmatrix} 1 & 0 & -1 \\ R_1 & u_1 & R_3 \\ 0 & u_2 & R_3 \end{vmatrix} = u_1 R_3 - R_1 u_2 - u_2 R_3 =$$

$$= 200 - 400 - 800 =$$

$$= - \underline{\underline{1000}}$$

$$D_{I_3} = \begin{vmatrix} 1 & 1 & 0 \\ R_1 & 0 & u_1 \\ 0 & R_2 & u_2 \end{vmatrix} = -R_2 u_1 - u_2 R_1 =$$

$$= -100 - 400 = - \underline{\underline{500}}$$

$$I_1 = \frac{D_{I_1}}{D_S} = \frac{500}{-2000} = \underline{\underline{-0.25 A}}$$

$$I_2 = \frac{D_{I_2}}{D_S} = \frac{-1000}{-2000} = \underline{\underline{0.5 A}}$$

$$I_3 = \frac{D_{I_3}}{D_C} = \frac{-500}{-2000} = \underline{\underline{0.25 A}}$$

CONTROL OF OUR RESULTS:

→ CHECKING CALCULATION BY SUBSTIT.
THE CALCULATED VALUES TO THE
ORIGINAL SLAE

$$\textcircled{1} I_1 + I_2 - I_3 = 0 \Rightarrow -0,25 + 0,5 - 0,25 = 0 \quad \checkmark$$

$$\textcircled{2} \begin{matrix} u_{R1} & u_{R2} \\ R_1 I_1 + R_3 I_3 - u_1 = 0 \\ -5 + 10 - 5 = 0 \quad \checkmark \end{matrix}$$

$$\textcircled{3} \begin{matrix} u_{R2} & u_{R3} \\ R_2 I_2 + R_3 I_3 - u_2 = 0 \\ 10 + 10 - 20 = 0 \quad \checkmark \end{matrix}$$

→ TEST (CHECK) OUR SOLUTION

IN MATLAB

$$A \vec{x} = \vec{b}$$

$$\underbrace{A^{-1} A}_{E} \vec{x} = A^{-1} \vec{b}$$
$$\vec{x} = A^{-1} \vec{b}$$

$$\vec{x} = A \setminus \vec{b}$$

MULTIPLY THE
SYSTEM WITH
INVERSE MATRIX A^{-1}


$$A^{-1} A = A A^{-1} = E \begin{pmatrix} 1 & & 0 \\ & \ddots & \\ 0 & & 1 \end{pmatrix}$$

↑
IDENTITY
MATRIX

GAUSS ELIMINATION METHOD

LOOP CURRENT METHOD

(EX) PARAMETERS: U_1, U_2, R_1, R_2, R_3

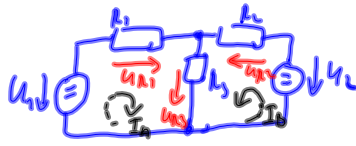

IN EVERY LOOP HOLDS:
 $\sum U = 0$ (K.V.L.)

IN THE DIRECTION OF LOOP (I_A):

$$U_{R1} + U_{R3} - U_1 = 0$$

$$R_1 \cdot I_A + R_3(I_A + I_B) = U_1$$

OHM'S LAW:

$$U_{R1} = R_1 \cdot I_A$$

$$U_{R3} = R_3 \cdot (I_A + I_B)$$

$$U_{R2} = R_2 \cdot I_B$$

IN THE DIRECTION OF LOOP (I_B):

$$U_{R2} + U_{R3} - U_2 = 0$$

$$R_2 I_B + R_3(I_A + I_B) = U_2$$


2 EQUATIONS FOR 2 UNKNOWN (I_A, I_B)

→ SOLVE SLAB

$$\Rightarrow \begin{aligned} I_A &= \dots \\ I_B &= \dots \end{aligned}$$

COMPUTATION OF THE CURRENTS IN

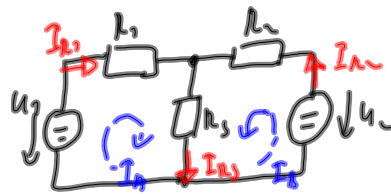OUR EL. CIRCUIT: I_{R1}, I_{R2}, I_{R3} ?



WE KNOW I_A

WE LOOK AT THE ORIENTATION (DIRECTION)

OF I_A, I_B, I_{R1}, I_{R2}

AND COMPUTE:

$$\begin{aligned} I_{R1} &= I_A, \quad I_{R2} = I_B \\ I_{R3} &= I_A + I_B \end{aligned}$$

FINALLY WE CAN COMPUTE VOLTAGE

$$U_x = R \cdot I$$