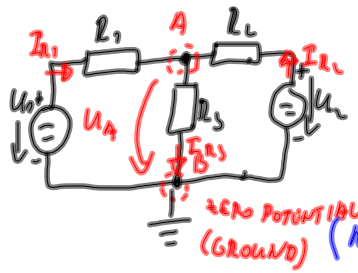


NODE VOLTAGE METHOD

IEE
20.10.2017



NODE = THE PLACE IN
EL. CIRCUIT WHERE
AT LEAST 3 WIRES
(COMPONENTS)
ARE CONNECTED


SET ONE NODE AS "REFERENCE"
(DIFFERENTIAL NODE)

SUM OF THE CURRENTS IN THE NODE

$$\sum I = 0 \quad (\text{I. K. L.})$$

$$I_{R1} + I_{R2} - I_{R3} = 0$$

ALTERNATIVE EL. CIRCUIT FOR I_{R1}

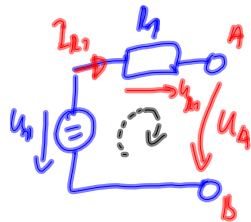


$(\sum u = 0) \dots \text{I. K. L.}$

$$R_1 \cdot I_{R1} + U_A - U_0 = 0$$

$$I_{R1} = \frac{U_0 - U_A}{R_1} \quad \checkmark$$


ALTERNATIVE EL. CIRCUIT FOR I_{R2}

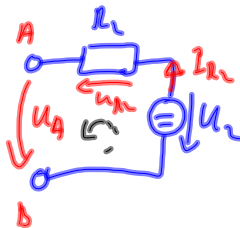

$$R_2 \cdot I_{R2} + U_B - U_1 = 0$$

$$I_{R2} = \frac{U_1 - U_B}{R_2} \quad \checkmark$$

ALTERNATIVE EL. CIRCUIT FOR I_{R3}

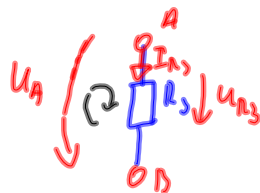

$$R_3 I_{R3} - U_A = 0$$

$$I_{R3} = \frac{U_A}{R_3} = \frac{U_{R3}}{R_3} \quad \checkmark$$

NOTE: 'REVERSE' LOOP (⊖)

$$U_A - R_3 I_{R3} = 0 \rightarrow I_{R3} = \frac{-U_A}{-R_3}$$

SUBSTITUTE $\underline{I_{R1}}$, $\underline{I_{R2}}$, $\underline{I_{R3}}$ INTO


$$\begin{aligned} & \underline{I_{R1}} + \underline{I_{R2}} - \underline{I_{R3}} = 0 \\ & \frac{U_1 - U_A}{R_1} + \frac{U_2 - U_A}{R_2} - \frac{U_A}{R_3} = 0 \end{aligned}$$

$$\Rightarrow U_A = \dots$$

OF COURSE WE KNOW CURRENTS $(\underline{I_{R1}}, \underline{I_{R2}}, \underline{I_{R3}})$


AND VOLTAGES $(\underline{U_{R1}}, \underline{U_{R2}}, \underline{U_{R3}})$

THEVENIN'S THEOREM

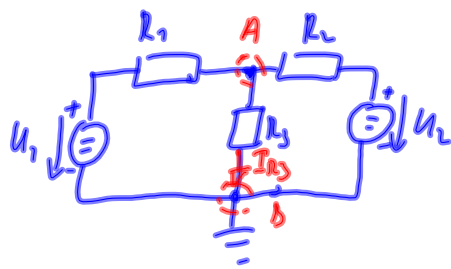

$$I_{R3} = ?$$

⇒ EQUIVALENT GL. CIRCUIT

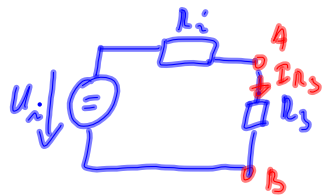


$$I_{R3} = \frac{U_i}{R_i + R_3}$$


R_{EQV}

$$U_i, R_i = ?$$

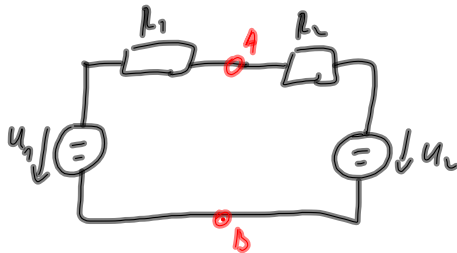$R_i = ?$? REORAW THE GL. CIRCUIT WITHOUT R_3




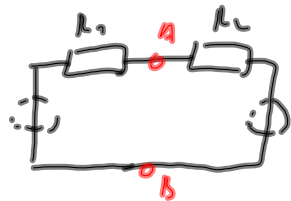↳ REPLACE VOLTAGE SOURCES BY A "SHORT CIRCUIT"



→ COMPUTE RESISTANCE BETWEEN TERMINALS A, B

$$R_{EQV} \equiv R_i (R_{AB})$$

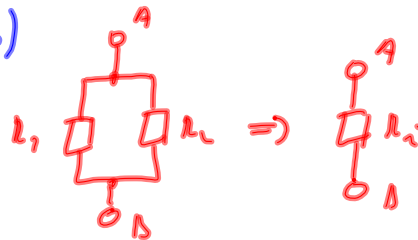


$$R_i = \frac{R_1 \cdot R_2}{R_1 + R_2} \quad \text{-- PARALLEL COMBINATION } R_1, R_2$$

$U_i = \dots \rightarrow$ REDRAW THE EL. CIRCUIT WITHOUT R_3

AND SOLVE THE VOLTAGE:

U_i AS "OPEN CIRCUIT" A, B

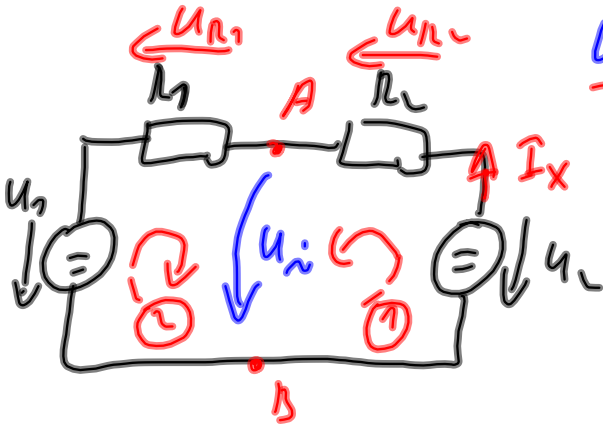

compute I_x (II.K.L.)

$$\textcircled{1} R_1 I_x + R_2 I_x + u_1 - u_2 = 0$$


$$I_x = \frac{u_2 - u_1}{R_1 + R_2} \equiv u \text{ in } R_{\text{equiv}}$$

II.K.L.

$$\textcircled{2} -R_2 I_x + u_i - u_2 = 0$$

$$u_i = u_2 + R_2 I_x \quad \checkmark$$


\rightarrow LAST STEP

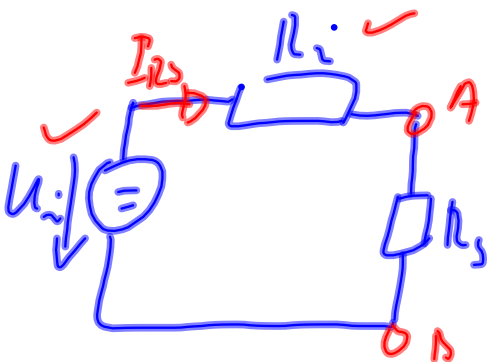


$$I_{R_s} = \frac{u_i}{R_i + R_s} \quad \checkmark$$

$$u_{R_s} = R_s I_{R_s} \quad \checkmark$$


OHN'S LAWS

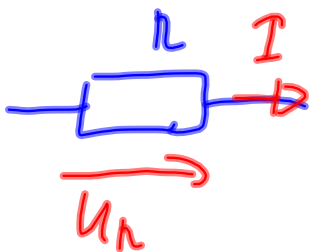

$$I = \frac{U_R}{R}$$

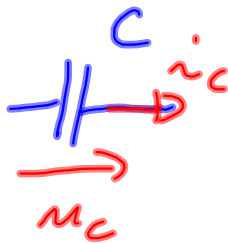

$$i_C = \frac{u_C}{C}$$

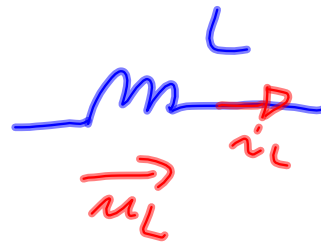


$$i_L = \frac{u_L}{L}$$

$$i_C = \frac{du_C}{dt}$$

$$i_L = \frac{du_L}{dt}$$

TRANSIENT STATE IN RLC ELECT. CIR.

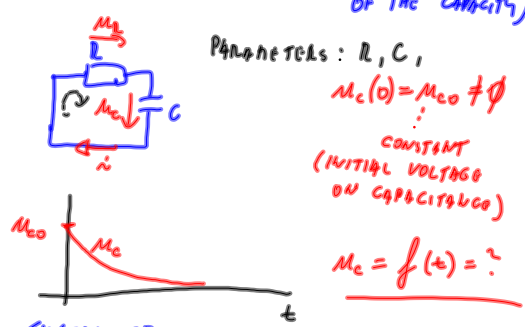1) EXAMPLE - RC CIRCUIT (DISCHARGING OF THE CAPACITY)



- SYSTEM OF EQUATIONS:
- 1) $u_R = R \cdot i$... OHM'S LAW
 - 2) $u_R + u_c = 0$... I. K. L.
 - 3) $u_c' = \frac{\dot{i}}{C}$, $u_c(0) = u_{c0}$

SET UP SOME EQUATION WITH UNKNOWN u_c' , u_c

→ SUBSTITUTE 1) INTO 2)

$$\underbrace{R \cdot i}_{u_R} + u_c = 0 \rightarrow i = \frac{-u_c}{R}$$

→ SUBSTITUTE i INTO 3) EQ.

$$u_c' = -\frac{u_c}{R \cdot C}$$

→ FIND ANALYTIC SOLUTION OF THE 1st ORDER ORDINARY

(*) DIFF. EQ.

$$\boxed{u_c' + \frac{1}{RC} \cdot u_c = 0}, u_c(0) = u_{c0}$$

↑
HOMOGENOUS

→ GENERAL SOLUTION:

$$u_c(t) = k(t) e^{\lambda t}$$

→ CHARACTERISTIC EQUATION

$$\lambda + \frac{1}{RC} = 0 \quad (u_c' = \lambda, u_c = 1, u_c'' = \lambda^2, u_c''' = \lambda^3)$$

$$\lambda = -\frac{1}{RC} \dots \tau \dots \text{TIME CONSTANT OF RC CIRCUIT}$$

→ SUBSTITUTE λ INTO GENERAL SOLUTION

$$u_c(t) = k(t) e^{-\frac{t}{RC}}$$