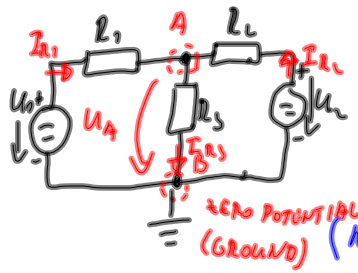


NODE VOLTAGE METHOD

IEE
20.10.2017



NODE = THE PLACE IN EL. CIRCUIT WHERE AT LEAST 3 WIRES (COMPONENTS) ARE CONNECTED


SET ONE NODE AS "REFERENCE" (REFERENTIAL NODE)

SUM OF THE CURRENTS IN THE NODE

$$\sum I = 0 \quad (\text{I. K. L.})$$

$$I_{R1} + I_{R4} - I_{R2} = 0$$

ALTERNATIVE EL. CIRCUIT FOR I_{R2}

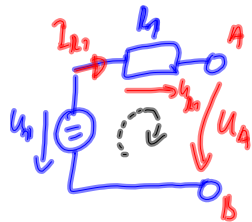


($\sum u = 0$) ... I. K. L.

$$R1 \cdot I_{R1} + U_A - U_0 = 0$$

$$I_{R1} = \frac{U_0 - U_A}{R1} \quad \checkmark$$


ALTERNATIVE EL. CIRCUIT FOR I_{R2}

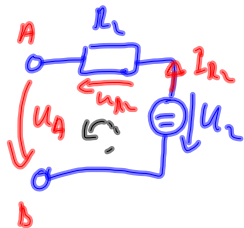

$$R4 \cdot I_{R2} + U_A - U_0 = 0$$

$$I_{R2} = \frac{U_0 - U_A}{R4} \quad \checkmark$$

ALTERNATIVE EL. CIRCUIT FOR I_{R3}

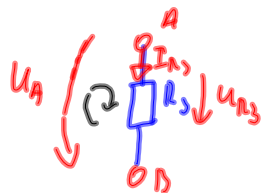

$$R3 \cdot I_{R3} - U_A = 0$$

$$I_{R3} = \frac{U_A}{R3} = \frac{U_{R3}}{R3} \quad \checkmark$$

NOTE: 'REVERSE' LOOP (⊖)

$$U_A - R3 \cdot I_{R3} = 0 \rightarrow I_{R3} = \frac{-U_A}{-R3}$$

SUBSTITUTE I_{R1} , I_{R2} , I_{R3} INTO

$$I_{R1} + I_{R2} - I_{R3} = 0$$


$$\frac{U_1 - U_A}{R_1} + \frac{U_2 - U_A}{R_2} - \frac{U_A}{R_3} = 0$$

$$\Rightarrow U_A = \dots$$


OF COURSE WE KNOW CURRENTS (I_{R1}, I_{R2}, I_{R3})

AND VOLTAGES (U_{R1}, U_{R2}, U_{R3})


THEVENIN'S THEOREM

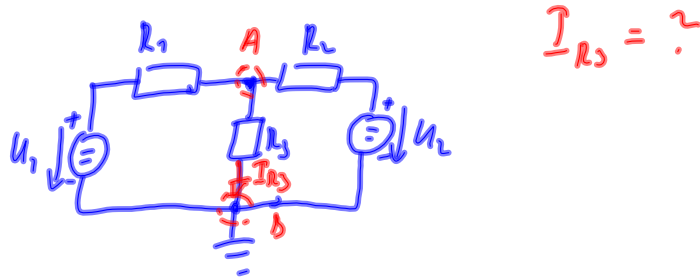


⇒ EQUIVALENT GL. CIRCUIT

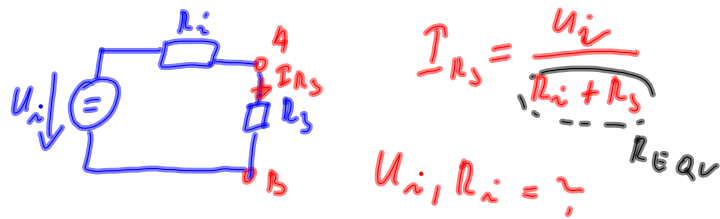

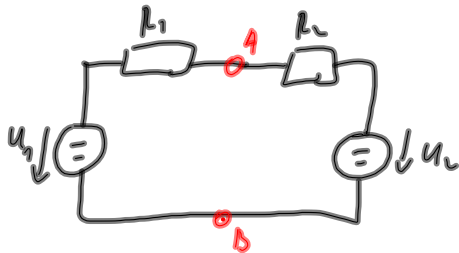$R_i = ?$? REORAW THE GL. CIRCUIT WITHOUT R_3




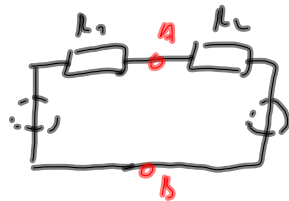↳ REPLACE VOLTAGE SOURCES BY A "SHORT CIRCUIT"



→ COMPUTE RESISTANCE BETWEEN TERMINALS A, B

$R_{EQV} \equiv R_i (R_{AB})$

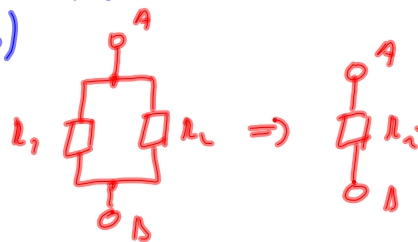


$R_i = \frac{R_1 \cdot R_2}{R_1 + R_2}$ -- PARALLEL COMBINATION R_1, R_2

$U_i = \dots \rightarrow$ REDRAW THE EL. CIRCUIT
WITHOUT R_3

AND SOLVE THE VOLTAGE:

U_i AS "OPEN CIRCUIT"
A,B

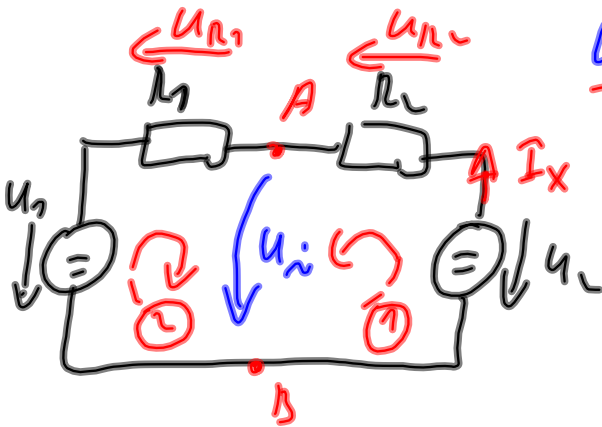

compute I_x (I.K.L.)

$$\textcircled{1} R_1 I_x + R_2 I_x + U_1 - U_2 = 0$$


$$I_x = \frac{U_2 - U_1}{R_1 + R_2} \equiv U \parallel R_{\text{equiv}}$$

I.K.L.

$$\textcircled{2} -R_2 I_x + U_i - U_1 = 0$$

$$U_i = U_1 + R_2 I_x \quad \checkmark$$


\rightarrow LAST STEP

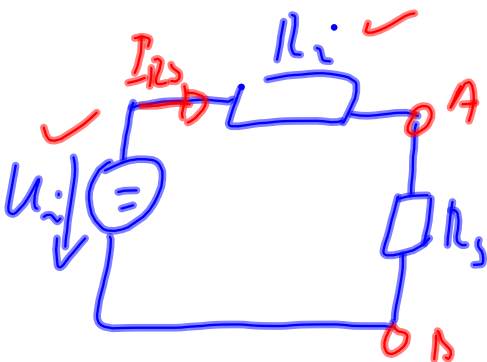


$$I_{R3} = \frac{U_i}{R_i + R_3} \quad \checkmark$$

$$U_{R3} = R_3 I_{R3} \quad \checkmark$$

OHM'S LAW

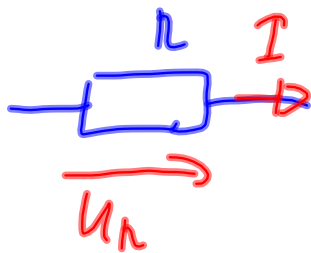


$$I = \frac{U_R}{R}$$

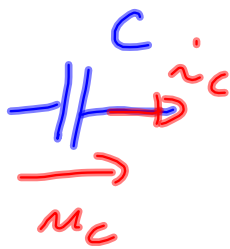

$$i_C = \frac{du_C}{dt}$$

$$i_C = \frac{dQ_C}{dt}$$

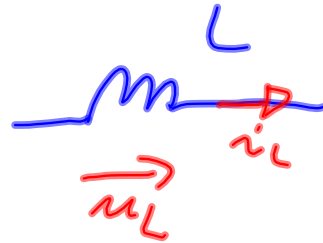

$$i_L = \frac{du_L}{dt}$$


$$i_L = \frac{d\Phi_L}{dt}$$



EL. COMPONENT CAPACITOR - STORES ^{EL.} ENERGY IN AN EL. FIELD

TRANSIENT STATE IN RLC ELECT. CIR.

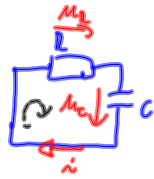1) EXAMPLE - RC CIRCUIT (DISCHARGING OF THE CAPACITY)



Parameters: $R, C,$

$u_C(0) = u_{C0} \neq 0$
 CONSTANT (INITIAL VOLTAGE ON CAPACITANCE)



$u_C = f(t) = ?$

SYSTEM OF EQUATIONS:

1) $u_R = R \cdot i$... OHM'S LAW

2) $u_R + u_C = 0$... I. K. L.

3) $u_C' = \frac{\dot{q}}{C}$, $u_C(0) = u_{C0}$

SET UP SOME EQUATION WITH UNKNOWN u_C', u_C

→ SUBSTITUTE 1) INTO 2)

$R \cdot i + u_C = 0 \rightarrow i = \frac{-u_C}{R}$

→ SUBSTITUTE i INTO 3) EQ.

$u_C' = -\frac{u_C}{R \cdot C}$

→ FIND ANALYTIC SOLUTION OF THE 1st ORDER ORDINARY DIFF. EQ.

$(*) \left[u_C' + \frac{1}{RC} \cdot u_C = 0 \right], u_C(0) = u_{C0}$

HOMOGENOUS

→ GENERAL SOLUTION:

$u_C(t) = K(t) e^{\lambda t}$

→ CHARACTERISTIC EQUATION

$\lambda + \frac{1}{RC} = 0$

$(u_C' = \lambda, u_C = 1, u_C'' = \lambda^2, u_C''' = \lambda^3)$

$\lambda = -\frac{1}{RC}$

... τ ... THE CONSTANT OF RC CIRCUIT

→ SUBSTITUTE λ INTO GENERAL SOLUTION

$u_C(t) = K(t) e^{-\frac{t}{RC}}$

- SUBSTITUTE u_c AND u_c' INTO (*)

$$u_c' = k(t) e^{-\frac{t}{RC}} - \frac{k(t)}{RC} e^{-\frac{t}{RC}}$$

$$k(t) e^{-\frac{t}{RC}} - \frac{k(t)}{RC} e^{-\frac{t}{RC}} + \frac{k(t)}{RC} e^{-\frac{t}{RC}} = 0$$

$$k(t) e^{-\frac{t}{RC}} = 0$$

INTegrate

$$k(t) = 0 \quad | \int$$

$$k(t) = \underline{\underline{A}} \quad \dots \quad \text{INTEGRATION CONSTANT}$$

GENERAL SOLUTION

$$u_c(t) = \underline{\underline{A}} e^{-\frac{t}{RC}}$$

→ SUBSTITUTE INITIAL VALUE

$$u_c(0) = u_{c0}$$

$$u_{c0} = \underline{\underline{A}} \cdot \left(e^{-\frac{0}{RC}} \right) = 1$$

$$\underline{\underline{A}} = u_{c0}$$

PARTICULAR SOLUTION

$$u_c(t) = u_{c0} e^{-\frac{t}{RC}}$$

TEST OF THE SOLUTION:

$$t=0: u_c = u_{c0} e^{-\frac{0}{RC}} \Rightarrow u_c(0) = u_{c0}$$


$$t \rightarrow \infty: u_c = u_{c0} e^{-\frac{\infty}{RC}} \Rightarrow u_c(\infty) = 0$$

→ SUBSTITUTE u_c AND u_c' INTO (*)

$$u_c' = -\frac{u_{c0}}{RC} e^{-\frac{t}{RC}}$$

$$-\frac{u_{c0}}{RC} e^{-\frac{t}{RC}} + \frac{1}{RC} \left(u_{c0} e^{-\frac{t}{RC}} \right) = 0$$

$$0 = 0 \quad \checkmark$$

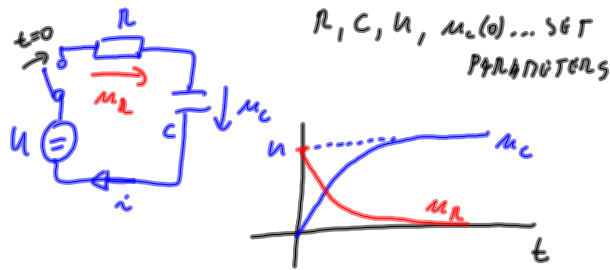CHARGING OF CAPACITOR

I. k. L.

$$i \cdot R + u_C = U$$

$$(*) \quad RC u_C' + u_C = U \quad \leftarrow \text{NOW-HOMOGENEOUS} + u_C(0) = u_{C0}$$

→ GENERAL SOLUTION

→ CHARACTERISTIC EQ ...

→ SUBSTITUTE u_C AND u_C' INTO (**)

$$RC \cdot k'(t) \cdot e^{-\frac{t}{RC}} = U$$

$$k'(t) = \frac{U}{RC} e^{\frac{t}{RC}} \quad | \int$$

$$k(t) = \frac{U}{RC} \cdot RC e^{\frac{t}{RC}} + \varrho$$

$$k(t) = U e^{\frac{t}{RC}} + \varrho$$

NOTE:

$$e^{\frac{t}{RC}} = RC e^{\frac{t}{RC}}$$

$$(RC e^{\frac{t}{RC}})' = e^{\frac{t}{RC}}$$

INTEGRATION CONSTANT

→ SUBSTITUTE $k(t)$ INTO GENERAL SOLN

$$u_C = (U e^{\frac{t}{RC}} + \varrho) \cdot e^{-\frac{t}{RC}} = U + \varrho e^{-\frac{t}{RC}}$$

→ PARTICULAR SOLUTION: SUBSTITUTE

INITIAL VALUE $u_C(0) = u_{C0}$

$$u_{C0} = U + \varrho \cdot e^{\overset{0}{-\frac{t}{RC}}} = ?$$

$$\varrho = u_{C0} - U$$

$$u_C = U + (u_{C0} - U) e^{-\frac{t}{RC}}$$