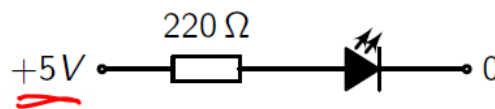


Bipolar transistors – diode recap



Just a reminder about the graphical solution of the diode:




$$U = I \cdot R$$


$$I = \frac{U}{R}$$

$$I = \frac{5V}{220\Omega}$$


$$=$$

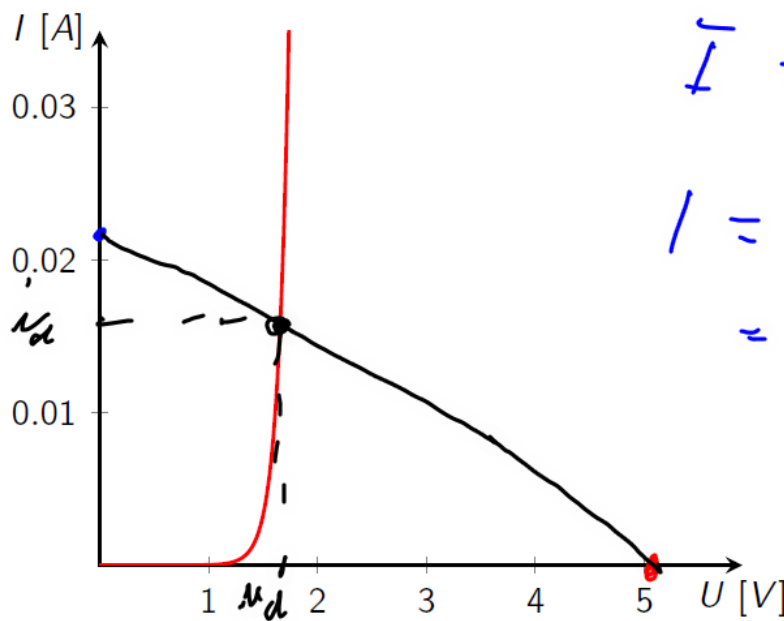


NPN transistor – input part

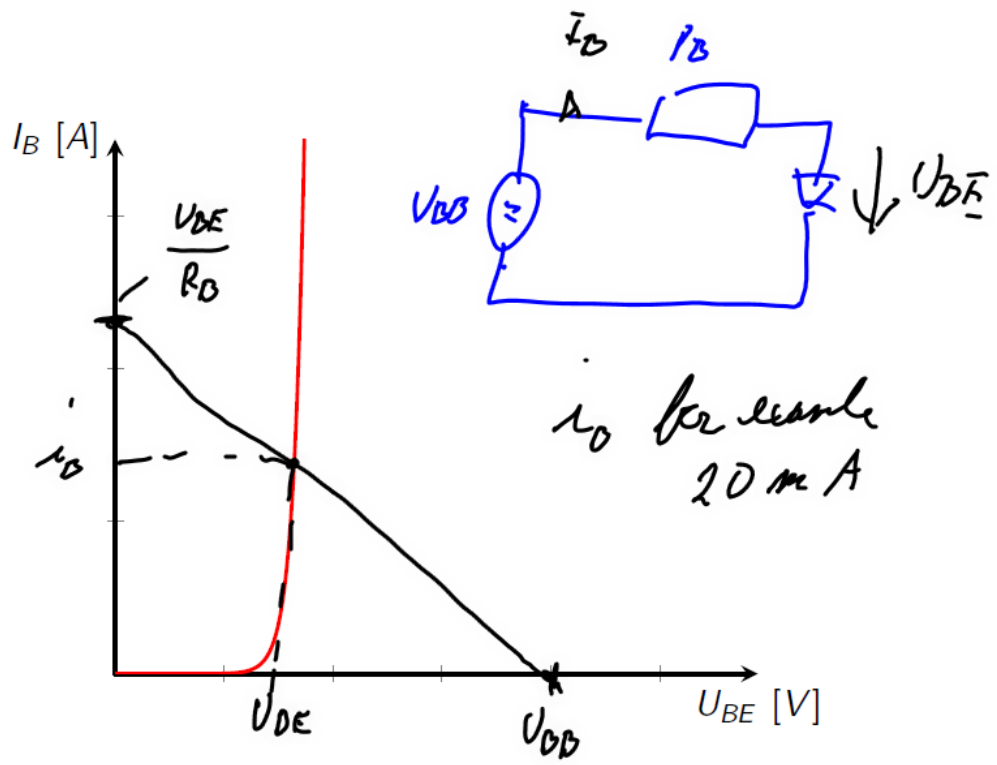

| NPN transistor – output part

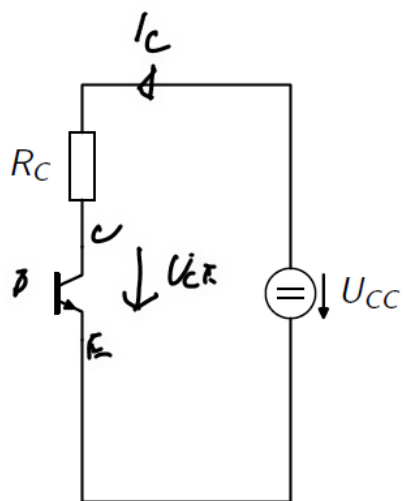


NPN transistor – output part

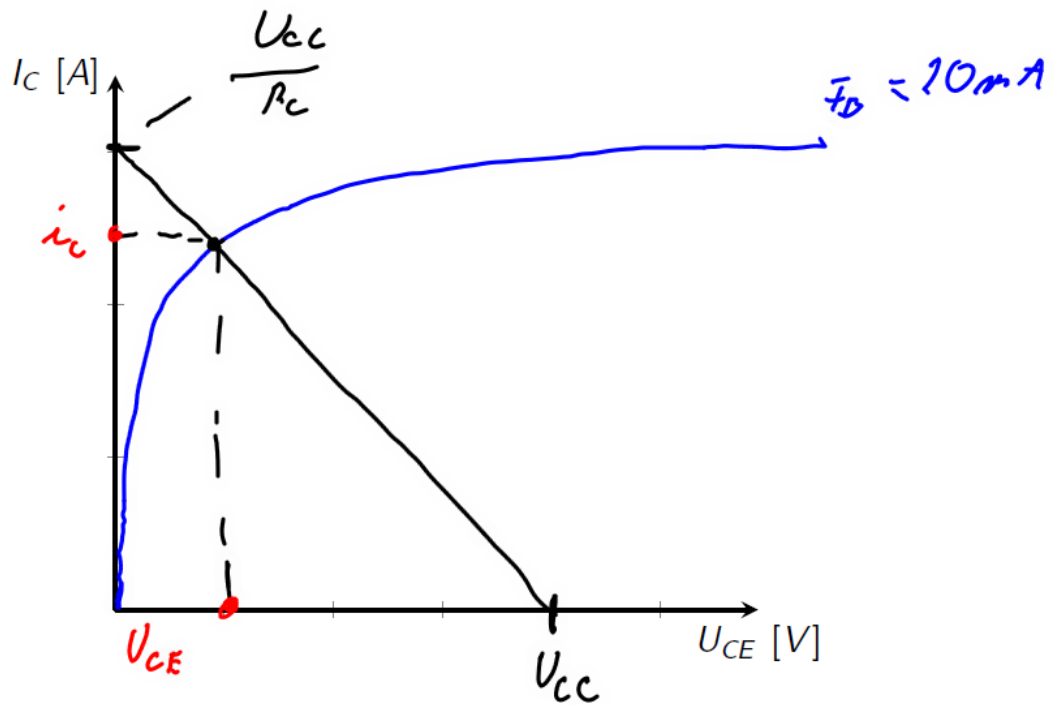

| NPN transistor – working point




Slightly different circuit

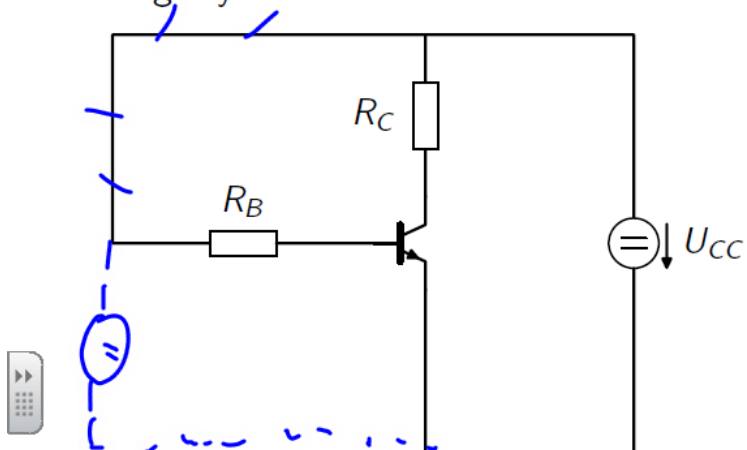

NPN transistor – working point




Slightly different circuit

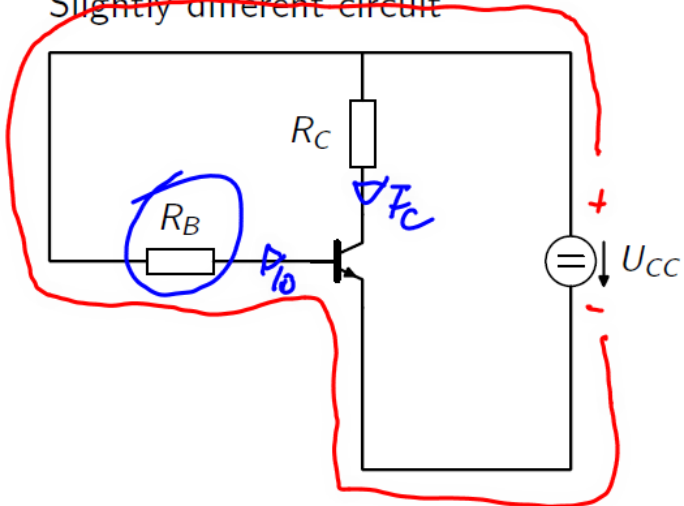

R_B CONTROLS
 I_B , I_C CONTROL
 I_E



NPN transistor – working part

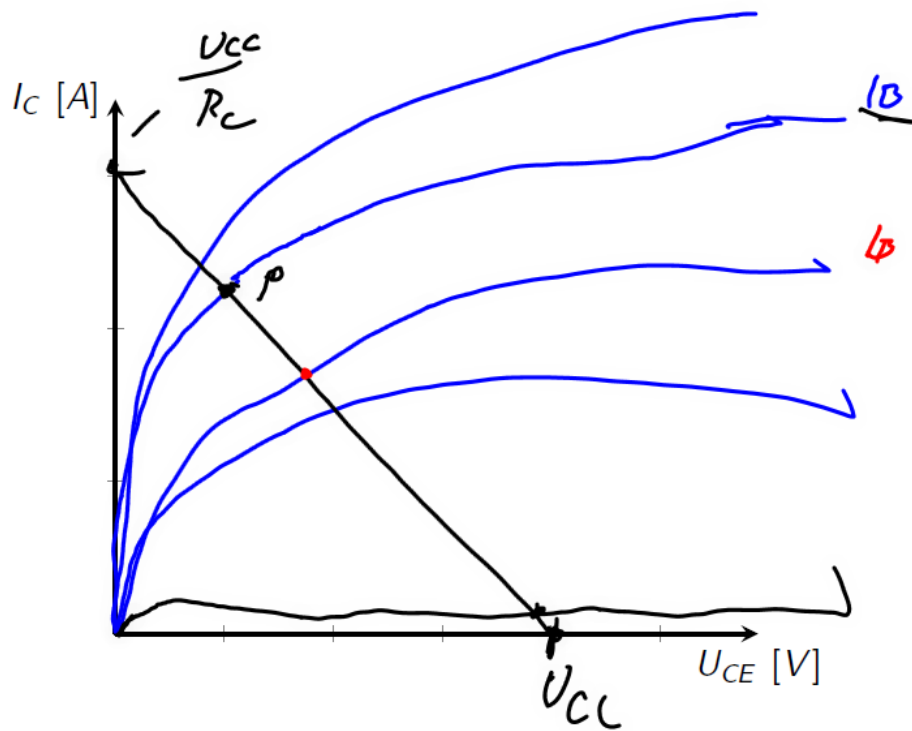


NPN transistor – gain



CHANGE IN OUT VOLTAGE

CHANGE IN INPUT ~~VOLTAGE~~
VOLTAGE

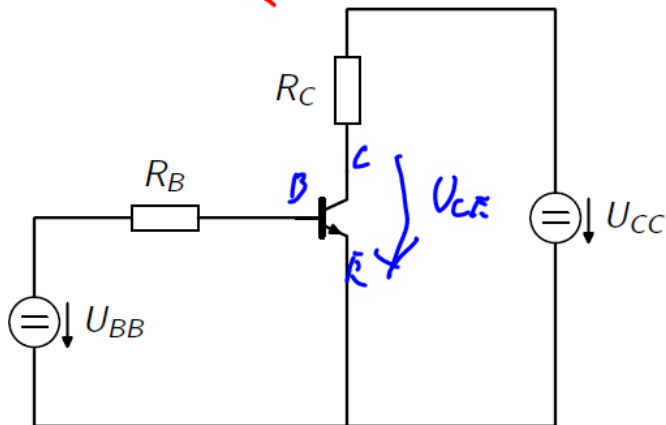
Transistor gain $A = \frac{\Delta U_{CE}}{\Delta U_{BB}}$




NPN transistor – gain (input part)



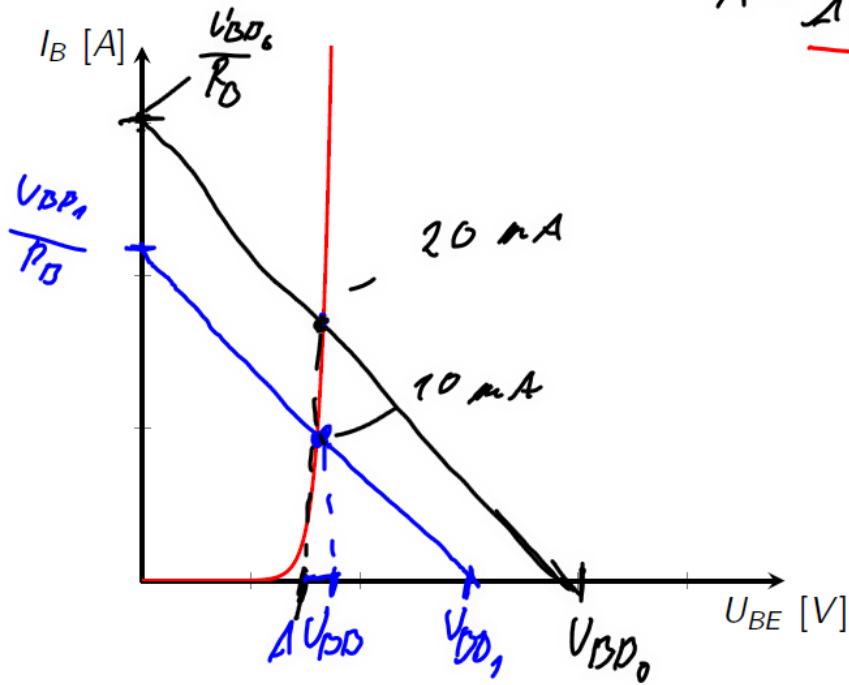
$$A = \frac{\Delta U_{CE}}{\Delta U_{BD}}$$




NPN transistor – output part

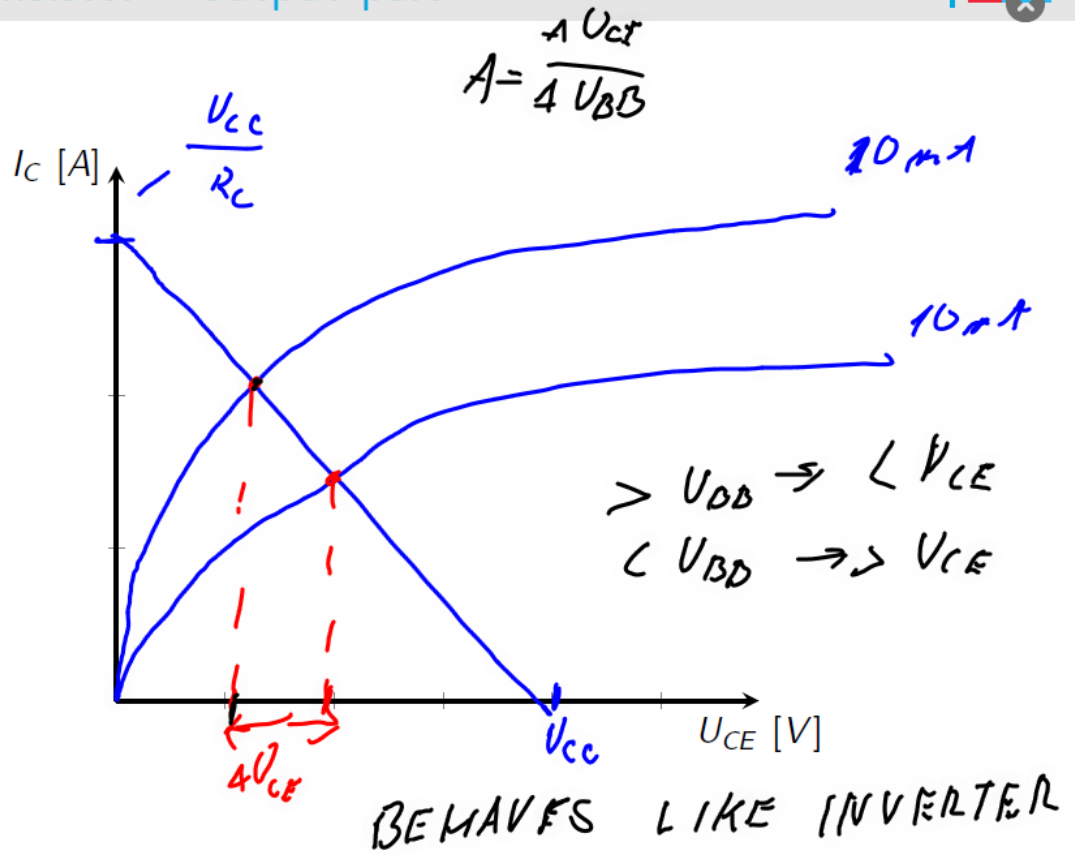


Two transistor amplifier

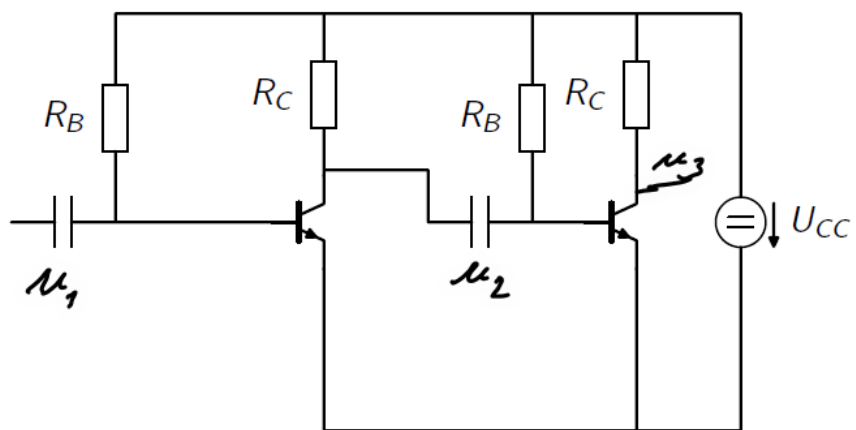

| Two transistor amplifier | T FIT

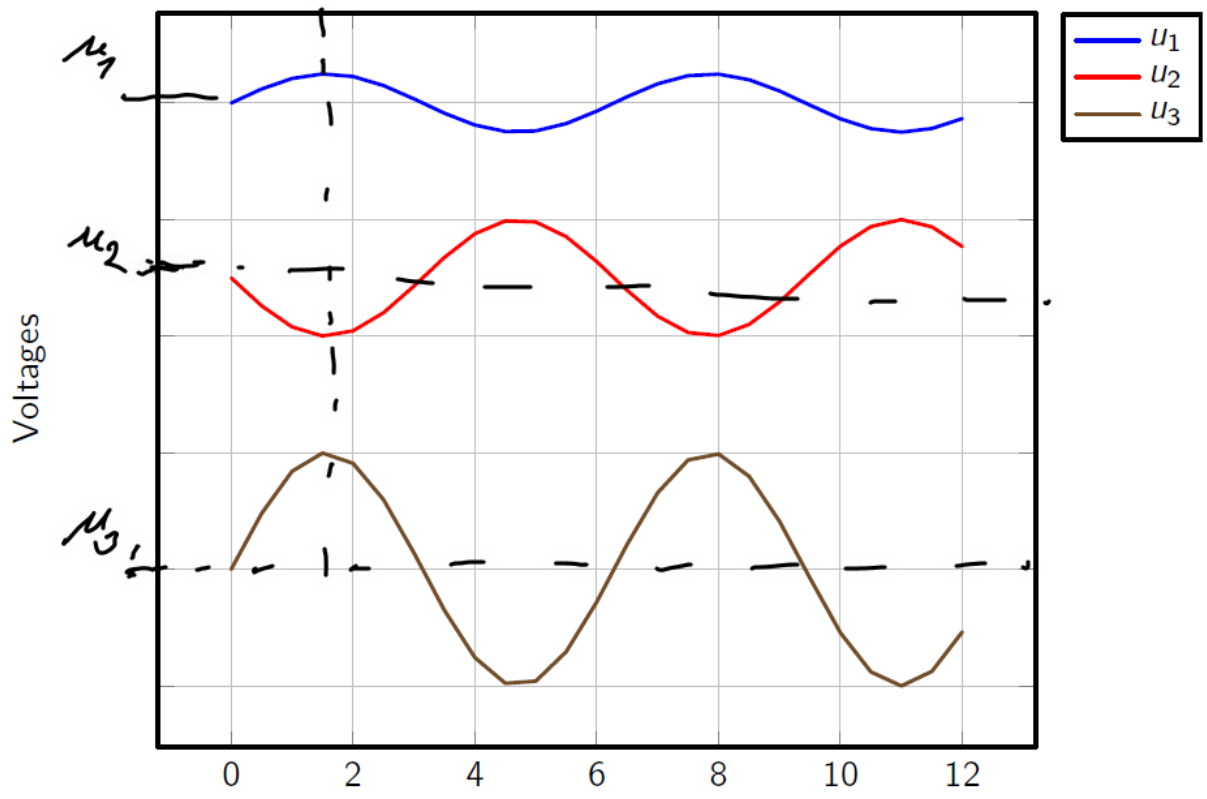


Two transistor amplifier | T FIT

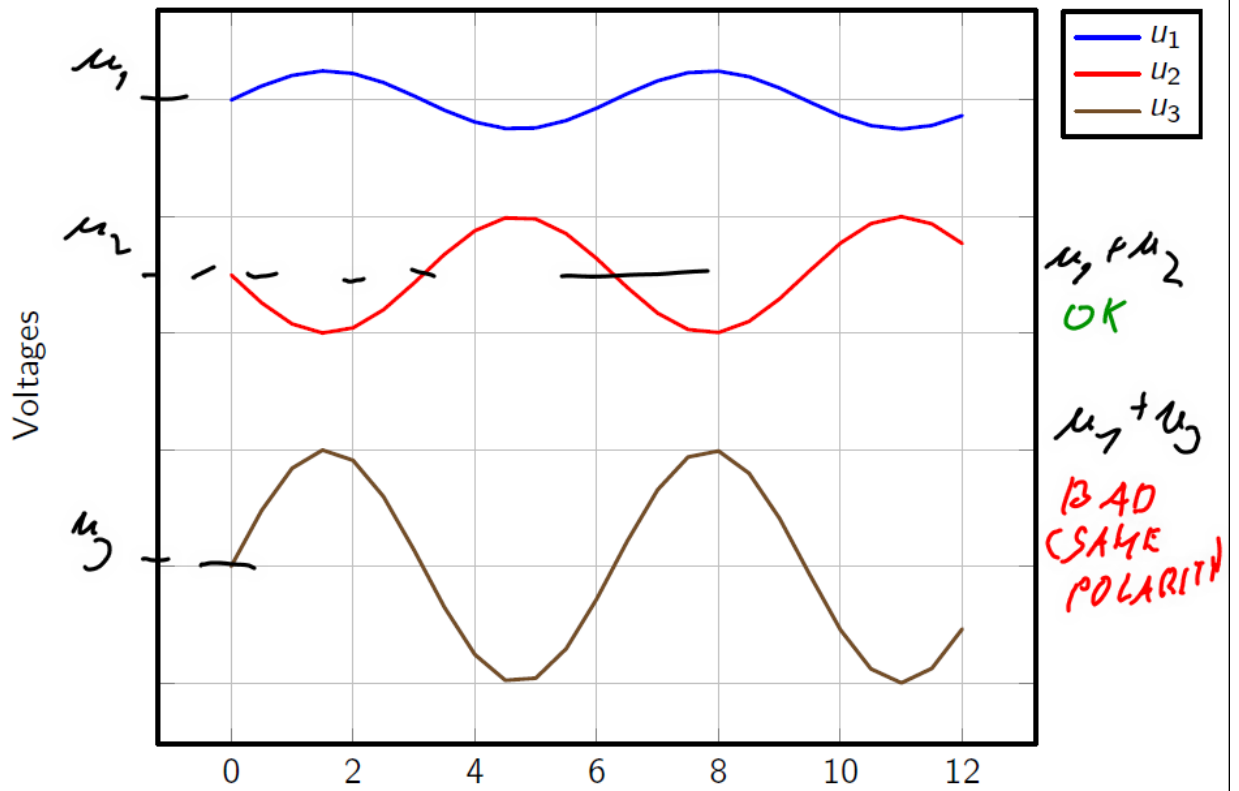


Feedback



POSITIVE → INSTABILITY

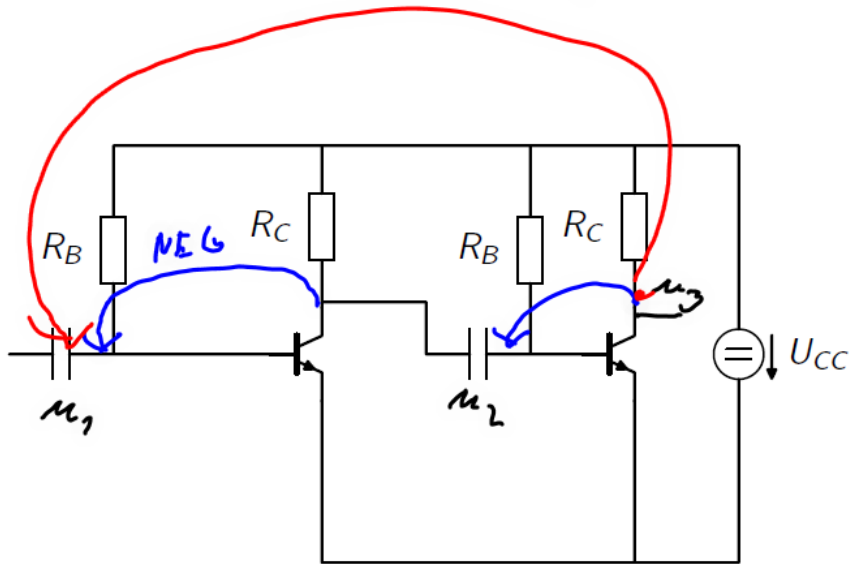


Feedback

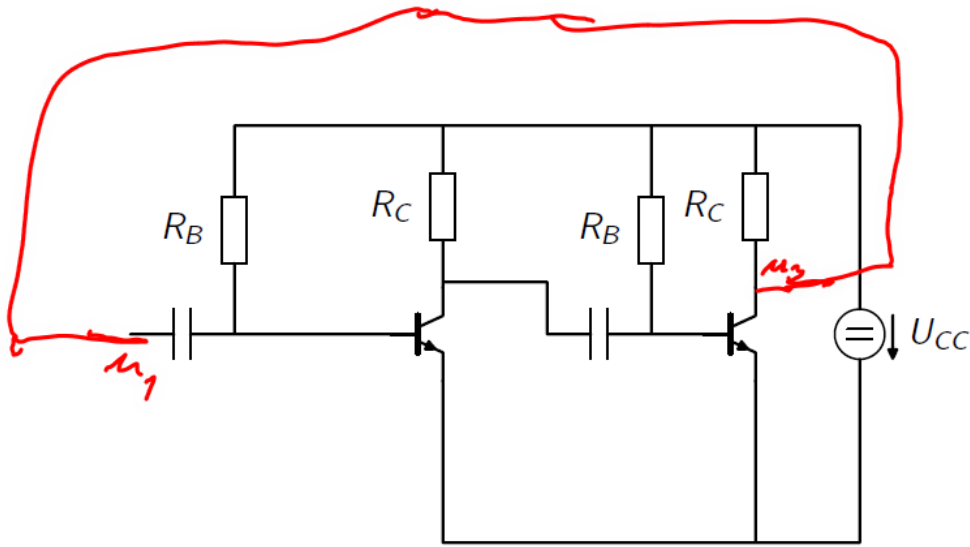

100% FEEDBACK
OSCILLATES



| Multivibrator – two stable states

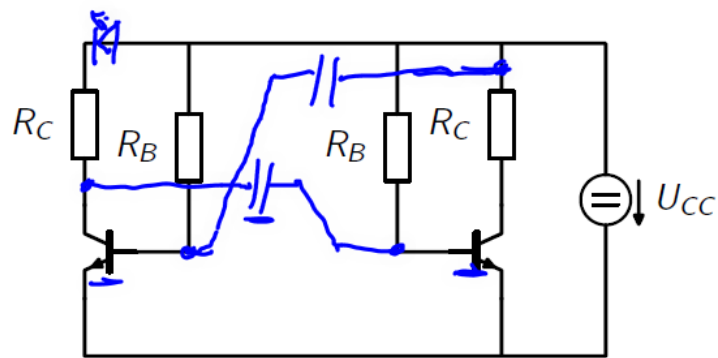

<https://www.youtube.com/watch?v=LgNAnIW1z5Q>