

IELe — bipolar transistors

Petr Veigend

[pveigend AT fit.vutbr.cz](mailto:pveigend@fit.vutbr.cz)

Vysoké učení technické v Brně,

Fakulta informačních technologií, Božetěchova 2, 61266 Brno




(Version: November 23, 2017)

Remember diode


- boxed PN junction, two electrodes (anode – P, cathode – N)
- symbol: anode  cathode
- diode is non linear, possible graphical solution
- we can combine diodes together to form more advanced components – bipolar transistors

Types of bipolar transistors – PNP

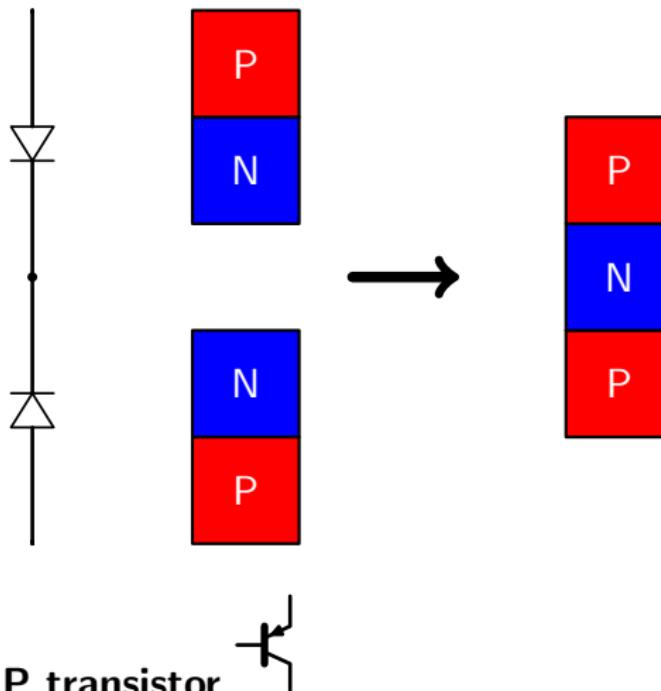



Result — **PNP transistor**

Types of bipolar transistors – NPN

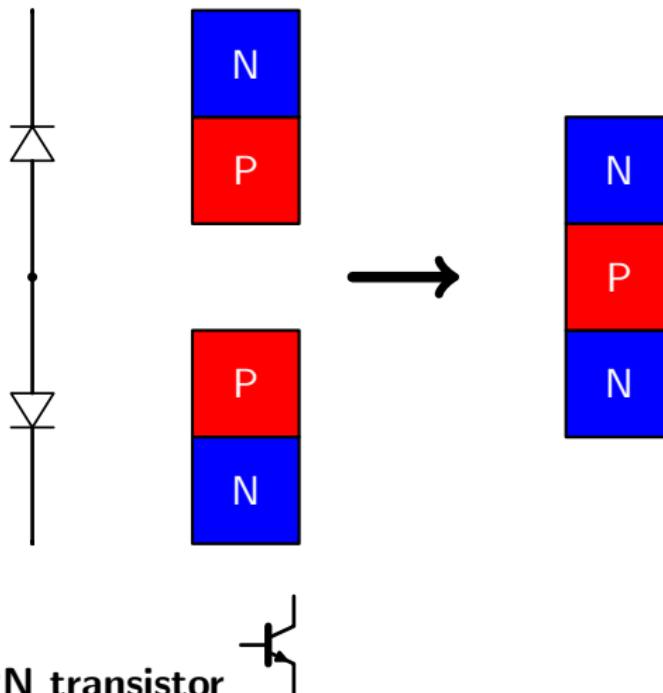


Result — **NPN transistor**


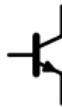


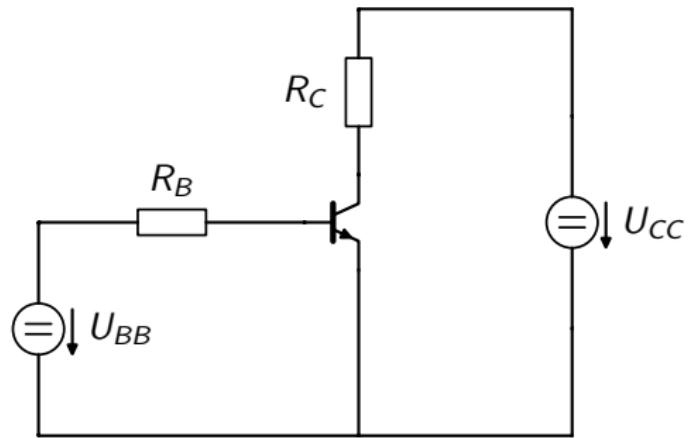



NPN transistor – input part

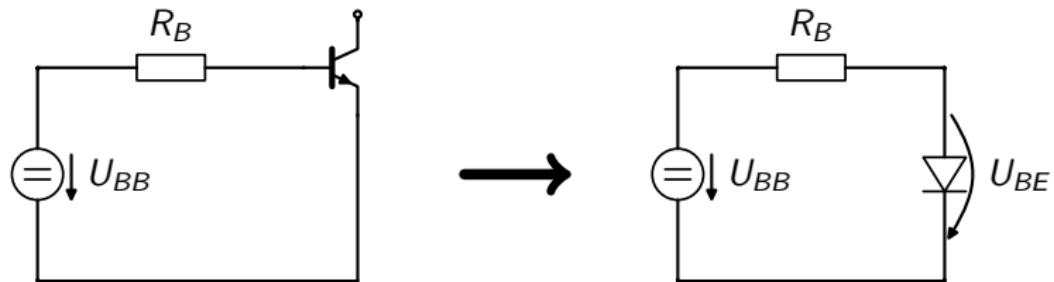


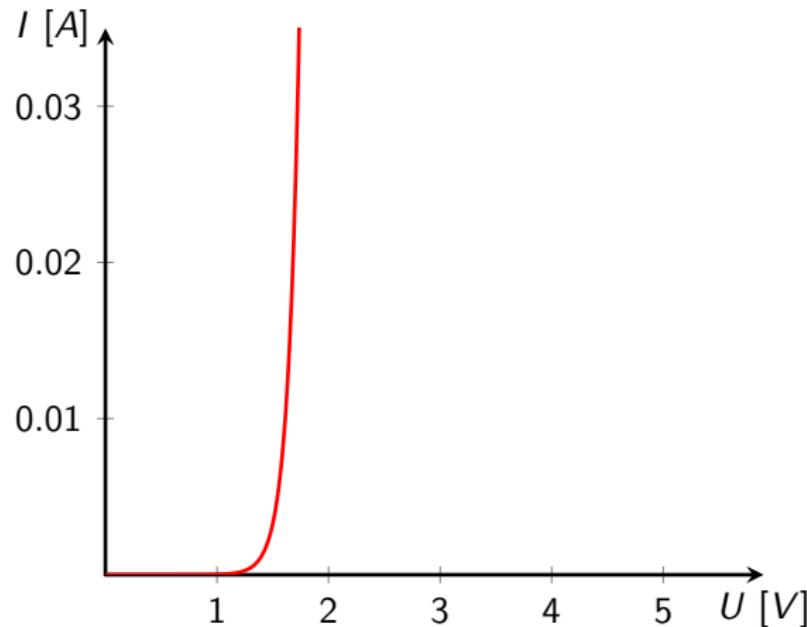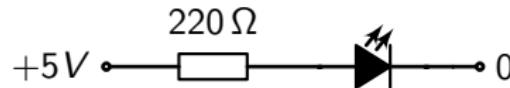Just a reminder about the graphical solution of the diode:




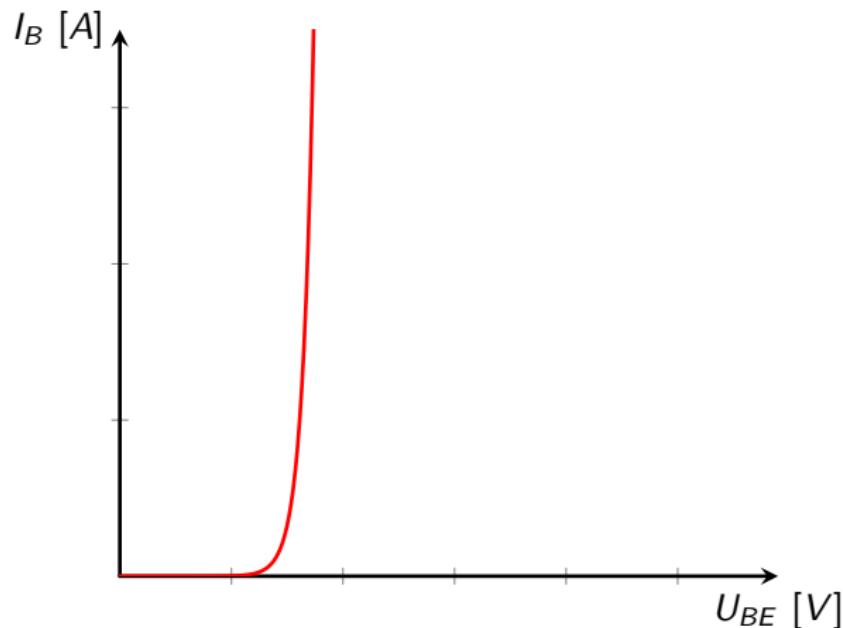


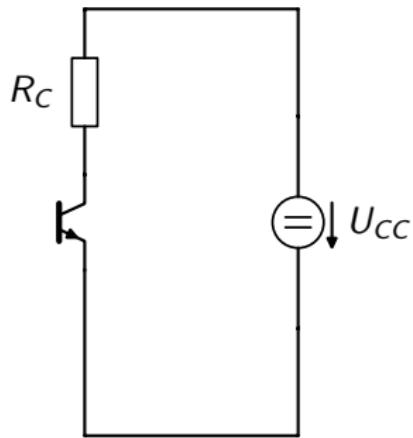

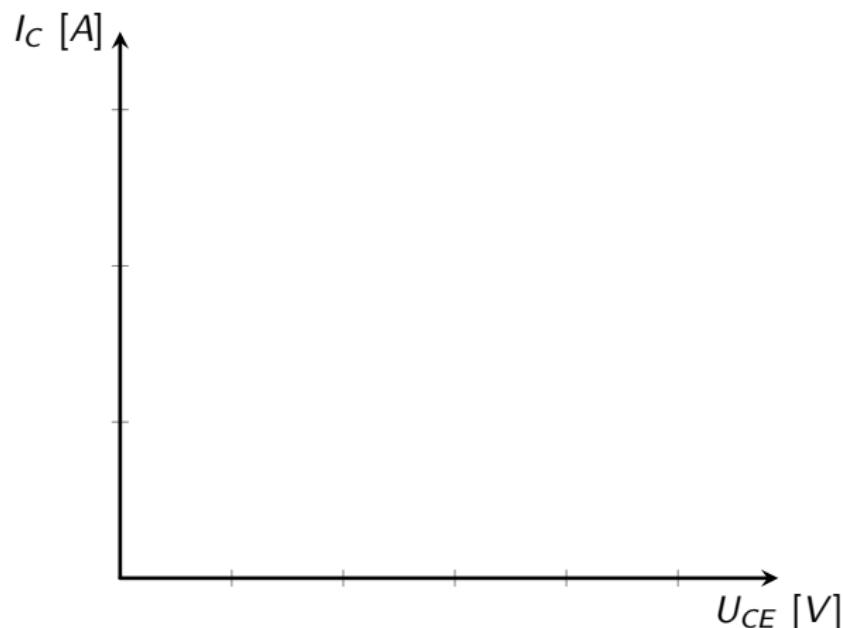



Slightly different circuit

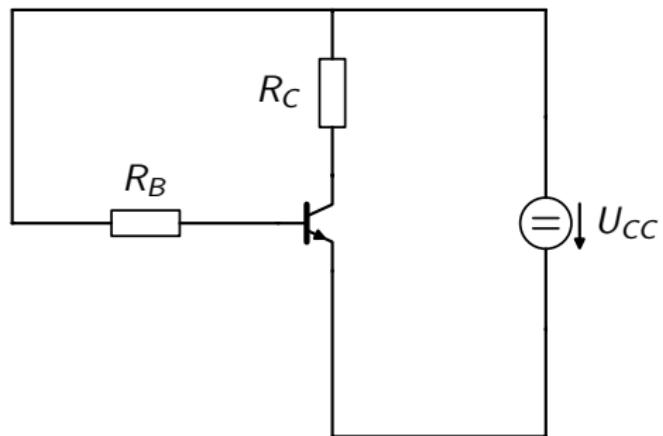


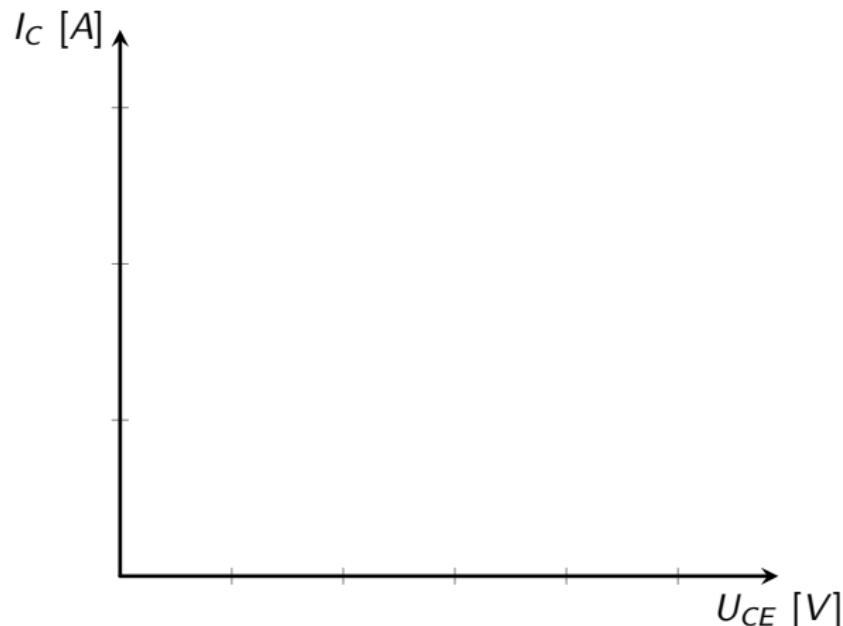

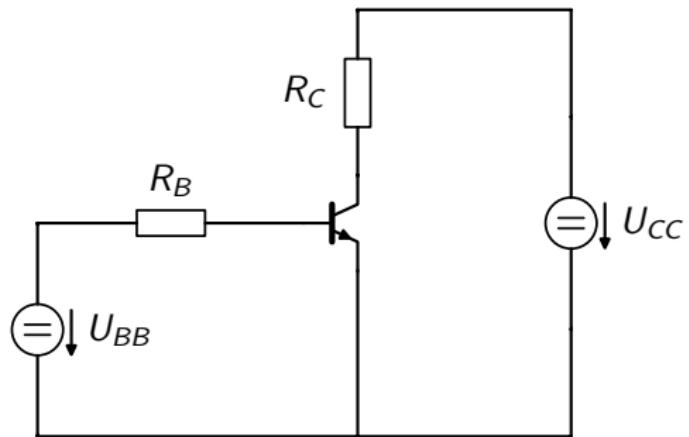
Transistor gain $A = \frac{\Delta U_{CE}}{\Delta U_{BB}}$



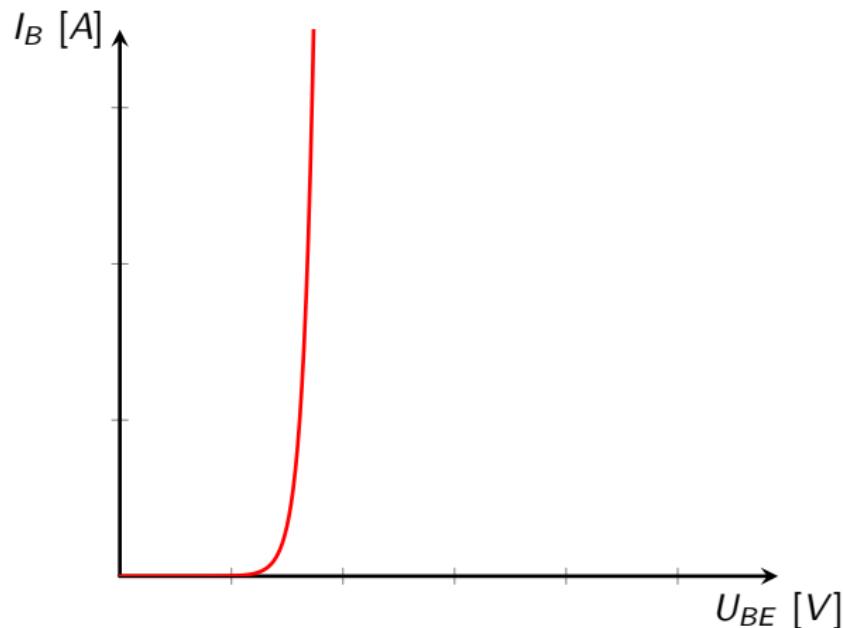


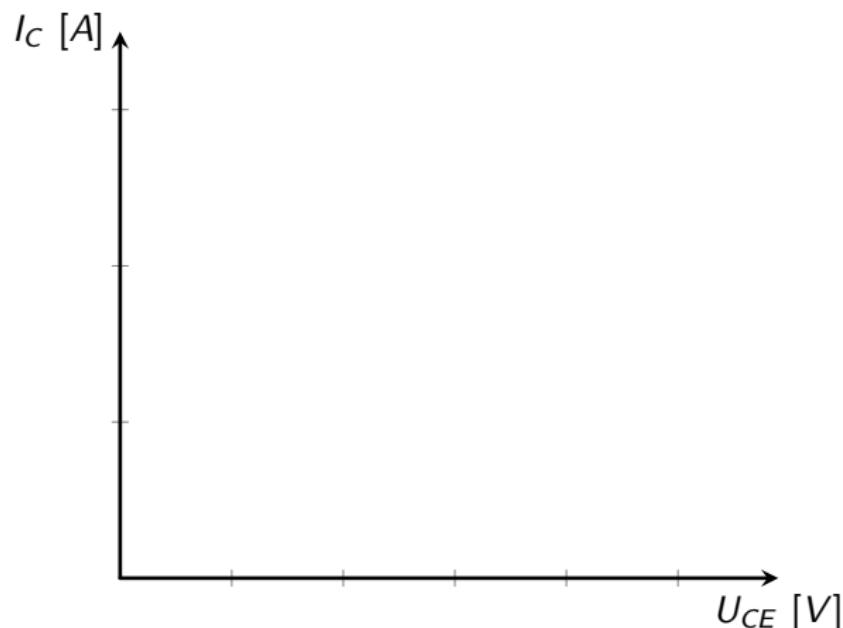



Two transistor amplifier

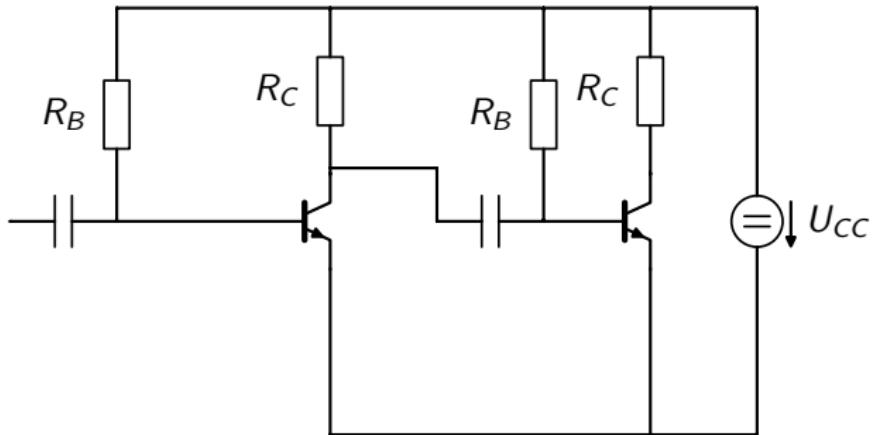

Two transistor amplifier

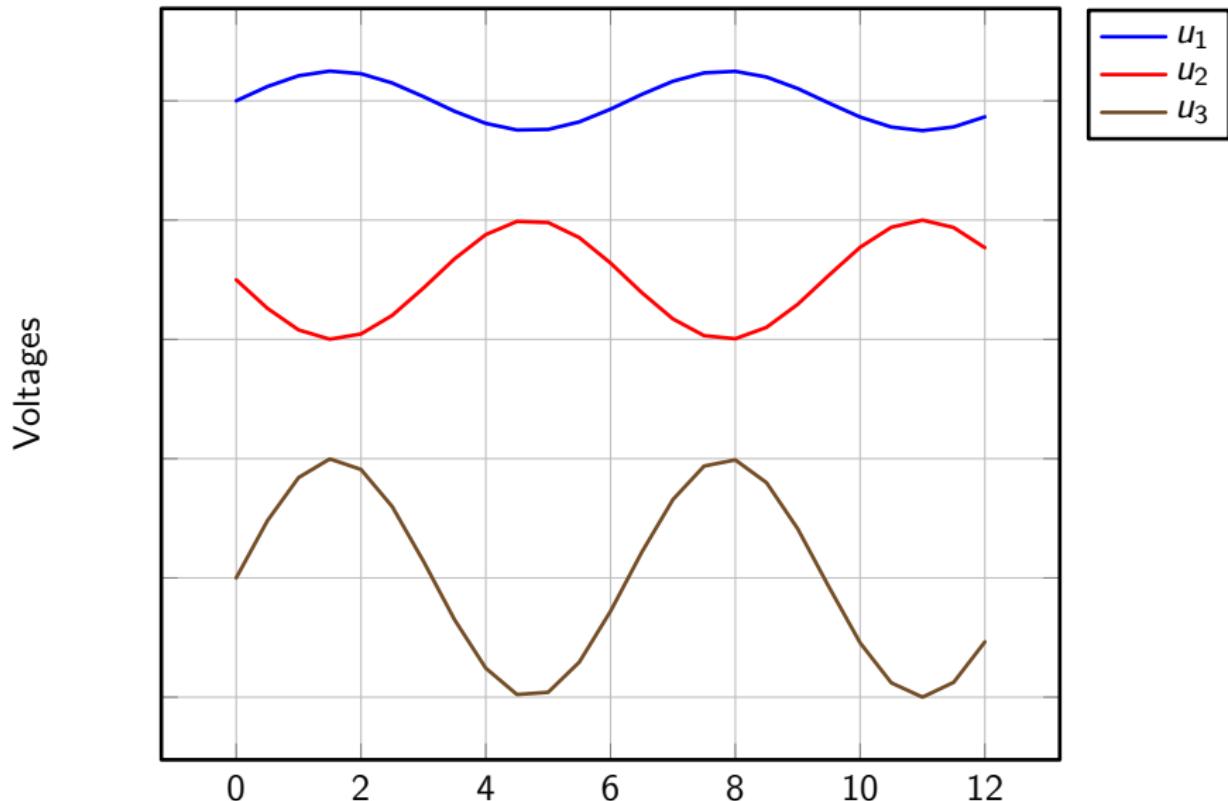

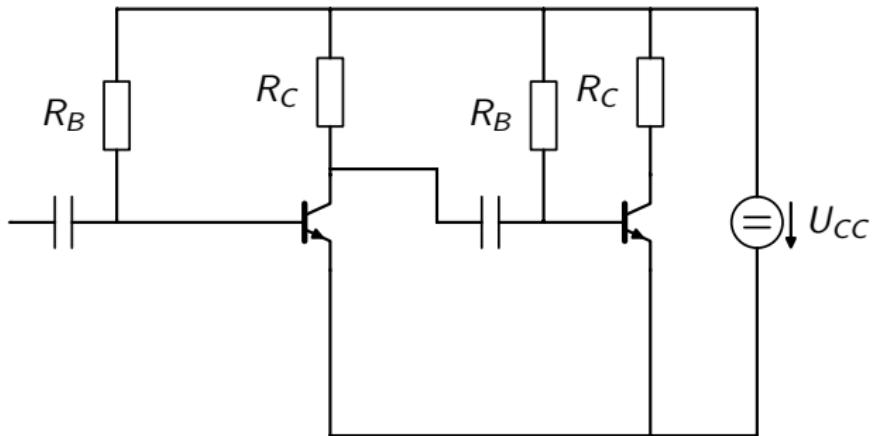

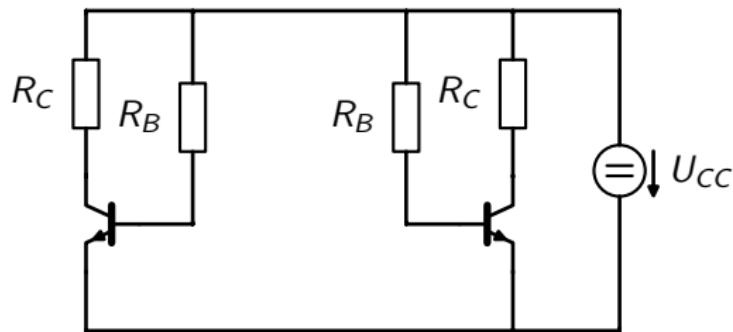

Conclusion:

- bipolar transistor
- solution of the bipolar transistor
- gain of the bipolar transistor
- multi vibrators