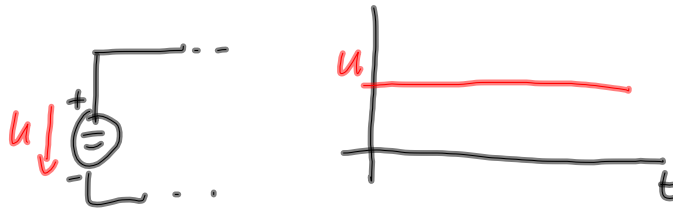



RLC CIRCUITS WITH AC POWER SUPPLY

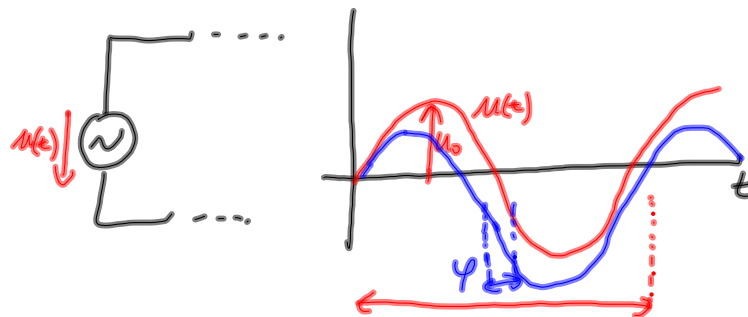1.12.2017
8.12.2017

- DC POWER SUPPLY → CONSTANT VOLTAGE
(DIRECT CURRENT)



- AC POWER SUPPLY → HARMONIC SIGNAL
(ALTERNATING CURRENT)



$$u(t) = U_0 \sin(\omega t + \varphi) \quad \text{PHASE SHIFT}$$

U_0 ... PEAK VOLTAGE [V]

ω ... ANGULAR VELOCITY [$\frac{\text{rad}}{\text{s}}$]

$\omega = 2\pi f \rightarrow f$... FREQUENCY [Hz]


$f = \frac{1}{T} \rightarrow T = \frac{1}{f}$... PERIOD OF THE SIGNAL [s]

→ STEADY-STATE ANALYSIS




(AMPLITUDE AND PHASE)

1) RESISTOR IN AC CIRCUIT

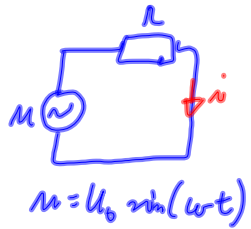


$i = ?$ CURRENT IS IN THE PHASE WITH POWER VOLTAGE ($\varphi = 0^\circ$)
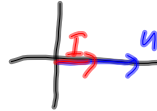
$$i = \frac{I_0 \sin(\omega t)}{I_0 = \frac{u_0}{R}} \quad i = \frac{u}{R}$$



2) CAPACITOR IN AC CIRCUIT

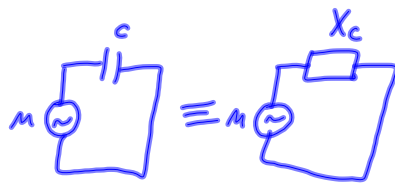


$X_C \dots$ CAPACITIVE REACTANCE [Ω]

$$X_C = \frac{1}{\omega C}$$


$Z_C \dots$ IMPEDANCE [Ω]

$$Z_C = \frac{1}{j\omega C} X_C$$
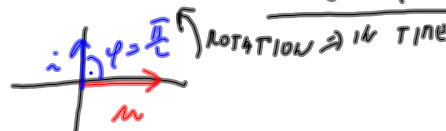
$$i = \frac{u}{Z_C} = \frac{u}{\frac{1}{j\omega C}} = j\omega C \cdot u = \omega C u_0 \sin(\omega t + \frac{\pi}{2})$$



3) INDUCTOR IN AC CIRCUIT

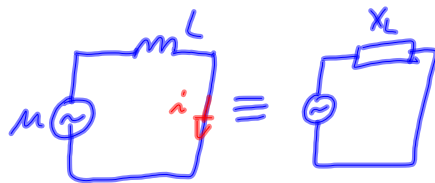


$X_L \dots$ INDUCTIVE REACTANCE [Ω]

$$X_L = \omega L$$

$$Z_L = j X_L$$

IMPEDANCE

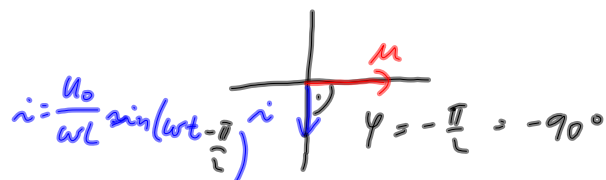
$$i = \frac{u}{jX_L} = \frac{u}{j\omega L} \cdot \frac{-j\omega L}{-j\omega L} = \frac{-j\omega L u}{-j^2 \omega^2 L^2} = \frac{-j u}{\omega L} = -\frac{j u}{\omega L}$$



4) RLC IN SERIES


$$u, R, C, L, \omega, U_0$$

$$u = U_0 \sin(\omega t)$$

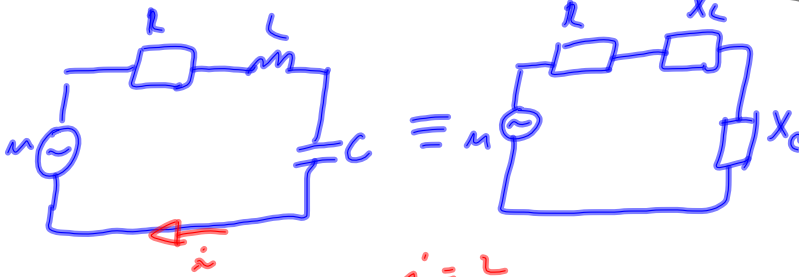

$$i = I_0 \sin(\omega t + \varphi)$$

→ METHOD OF SIMPLIFICATION

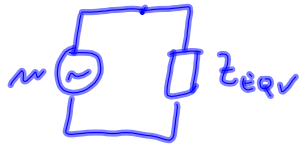

Z_{eqv} ... IMPEDANCE: (Ω)

$$Z_{eqv} = R + jX$$

RESISTANCE (REAL PART) REACTANCE (IMAGINARY PART)

$$Z_{eqv} = R + (X_L + X_C) j$$

$$Z_{eqv} = R + j\omega L - \frac{j}{\omega C} \dots \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$Z_{eqv} = R + j(\omega L - \frac{1}{\omega C})$$

Re Im

COMPUTING AMPLITUDES AND PHASE SHIFTS

$$I_0 = \frac{U_0}{Z_{eqv}} \dots \text{OHM'S LAW} \quad I_0 = A + Bj$$

$$|I_0| = \sqrt{A^2 + B^2}$$

$$U_R = I_0 \cdot R$$

$$\varphi = \arctan\left(\frac{B}{A}\right)$$

$$U_C = I_0 \cdot Z_C = \frac{j}{\omega C}$$

NOTE: BE CAREFUL OF

→ CAN BE $|u_c| = |u_L|$

YES, WHEN $|X_C| = |X_L| \Rightarrow \text{Im}(Z_{\text{total}}) = 0$

$$\omega_{\text{res}} L - \frac{1}{\omega_{\text{res}} C} = 0 \quad \left| \begin{array}{l} \text{RESONANCE} \\ \text{EFFECT} \end{array} \right.$$

$$\omega_{\text{res}}^2 LC - 1 = 0$$

$$\omega_{\text{res}} = \sqrt{\frac{1}{LC}}$$

$$2\pi f_{\text{res}} = \sqrt{\frac{1}{LC}}$$

$$f_{\text{res}} = \frac{1}{2\pi\sqrt{LC}} \quad \dots \quad \begin{array}{l} \text{RESONANCE} \\ \text{FREQUENCY} \end{array}$$

→ $f = f_{\text{res}} \dots (X = 0) \dots$ ^{REACTANCE} RESISTIVE CHARACTER
 U_0 IS ON RESISTOR R

$f < f_{\text{res}} \dots X < 0 \dots$ CAPACITIVE CHARACTER



$f > f_{\text{res}} \dots X > 0 \dots$ INDUCTIVE CHARACTER

→ PRACTICAL USAGE: EG. FILTERS

LOW PASS FILTERS
 (CAPACITOR
 OUTPUT VOLTAGE)

HIGH PASS
 (INDUCTOR
 OUT. VOLT.)


DON'T AFFIRMED OF OTHER COMBINATIONS

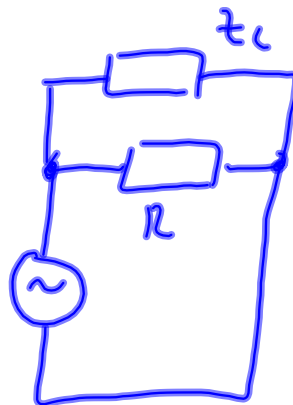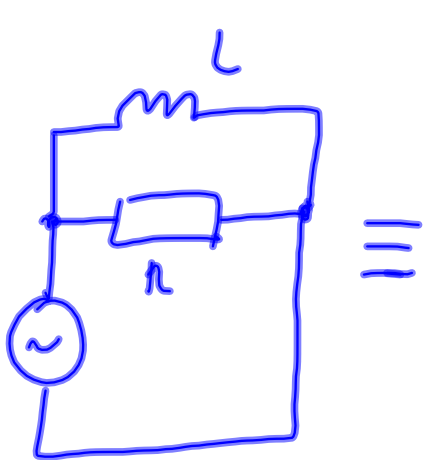

PARALLEL
COMBINATION

$$z_{eqv} = \frac{R \cdot z_L}{R + z_L} = \frac{R \cdot j\omega L}{R + j\omega L}$$

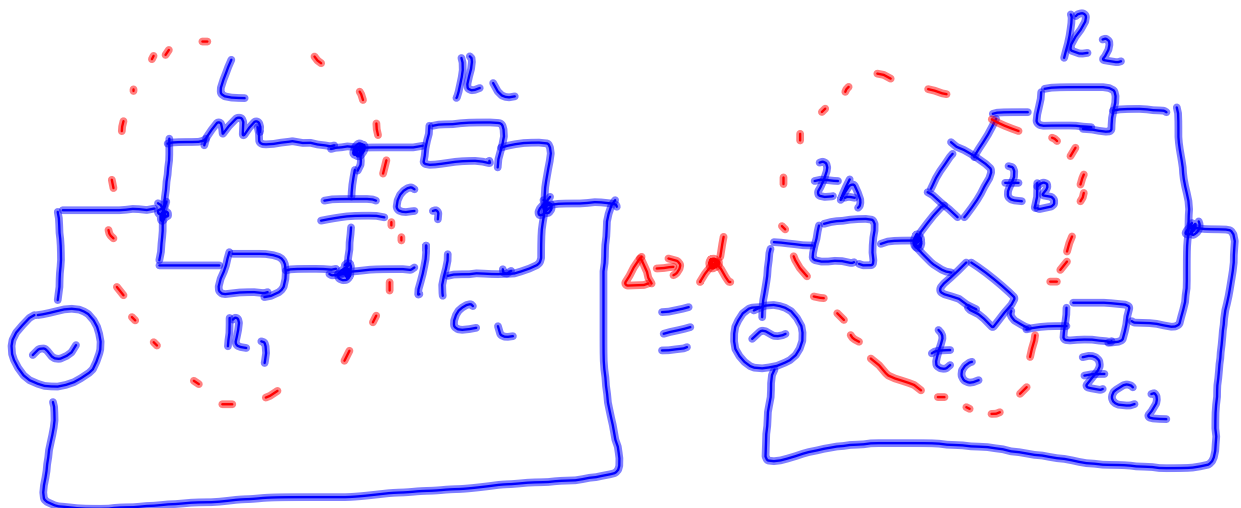
$$z_{eqv} = \frac{A}{Re} + j \frac{B}{Im} \in \mathbb{C}$$



$$z_A = \frac{z_L \cdot R_1}{z_L + R_1 + z_{C_1}} \in \mathbb{C}$$

⋮

→ OR CIRCUITS WITH MORE POWER SUPPLIES

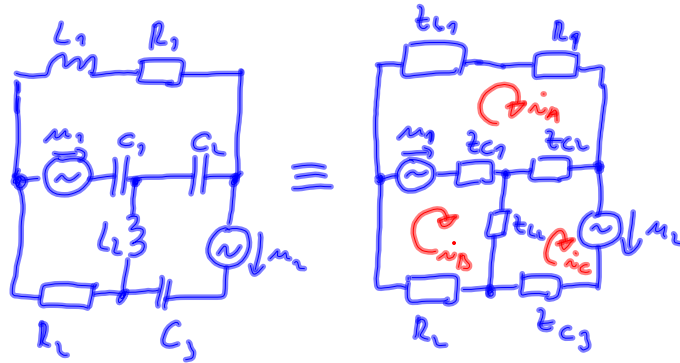

$$\tilde{i}_A: (z_{L1} + R_1) I_A + z_{C2}(I_A - I_C) + z_{C1}(I_A - I_B) - u_1 = \phi$$

$$\tilde{i}_B: z_{C1}(I_B - I_A) + z_{L2}(I_B - I_C) + R_2 I_B + u_1 = \phi$$

$$\tilde{i}_C: z_{C3} I_C + z_{L2}(I_C - I_B) + z_{C2}(I_C - I_A) + u_2 = \phi$$

$$\begin{pmatrix} z_{L1} + R_1 + z_{C2} + z_{C1} & -z_{C1} & -z_{C2} \\ -z_{C1} & z_{C1} + z_{L2} + R_2 & -z_{L2} \\ -z_{C2} & -z_{L2} & z_{C3} + z_{L2} + z_{C2} \end{pmatrix}$$

A

NOTE: MATRIX A IS SYMMETRIC

$$A = A^T$$


SOLVE SYSTEM (SLAE)

$$A \vec{x} = \vec{b} \quad \dots \text{CRAMER'S RULE, MATRIX INVERSE MATRIX} \dots$$



$$\vec{x} = \begin{pmatrix} I_A \\ I_B \\ I_C \end{pmatrix}, \quad \vec{b} = \begin{pmatrix} u_1 \\ -u_1 \\ -u_2 \end{pmatrix}$$

$A, \vec{x}, \vec{b} \in \mathbb{C} \dots$ COMPLEX NUMBERS


THEVENIN'S THEOREM

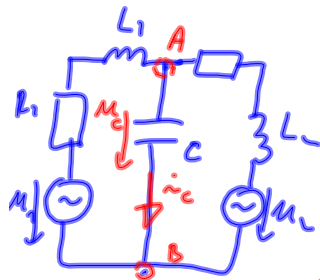

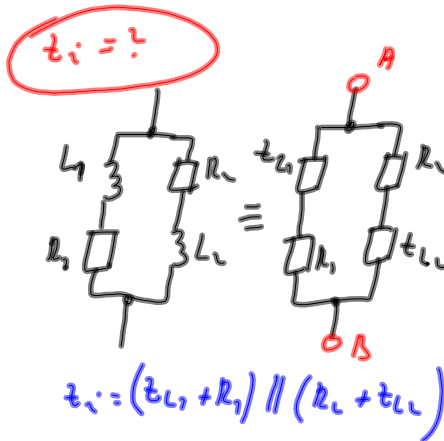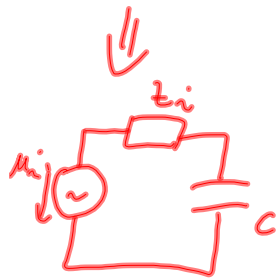$I_c, U_c = ?$
 $(\varphi_{I_c}, \varphi_{U_c})$



$U_i = ?$

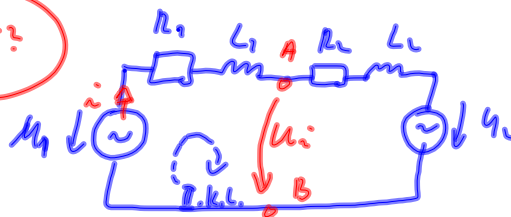

KIRCHHOFF'S LAW

METHOD OF SIMPLIFICATION

$U_{R1} + U_{L1} + U_i - U_2 = 0$
 $U_i = U_2 - U_{R1} - U_{L1}$

$U_i = U_2 - R_1 I - j\omega L_1 I$



$z_{oqv} = R_1 + R_2 + j\omega(L_1 + L_2)$

$U_{12} = U_1 - U_2 \in \mathbb{R}$

$I = \frac{U_{12}}{z_{oqv}} \in \mathbb{C}$

$I_c = \frac{U_i}{z_i + z_c} \in \mathbb{C}$

$U_c = I_c \cdot z_c \in \mathbb{C}$

compute AMPLITUDES $|I_c|, |U_c|$