# VNVe 2019/2020 - Final project

Author's name

April 22, 2020

Solve all examples and send your final solution (pdf file) and all source codes (LaTex, MATLAB, C, C++, etc.) to e-mail address satek@fit.vutbr.cz until May 17, 2020. Everything will be packed in one zip file 'surname.zip'.

### **1** Problem - Derivation reduction

Solve linear differential equation of the  $4^{th}$  order

$$y'''' + a_3 y''' + a_2 y'' + a_1 y' + a_0 y = b_4 z'''' + b_3 z''' + b_2 z'' + b_1 z' + b_0 z$$
(1)

with zero initial conditions, constant forcing function z = 1 and constants

$$a_3 = 12, a_2 = 24, a_1 = 2, a_0 = 3,$$
  
 $b_4 = 1, b_3 = 13, b_2 = 8, b_1 = 13, b_0 = 1$ 

Use Method of Derivative Order Reduction with Auxiliary Variable (MDOR-wAV) and the Method of Successive Integration (MSI).

- 1. Write the system of first order differential equations for the both methods (MDORwAV and MSI), use symbolic operator p and 1/p for operation of derivation and integration, respectively.
- 2. Draw (e.g. in Dia software) the scheme with inverting blocks (inverting integrators and summators).
- 3. Show the stability of the system (use Routh-Hurwitz stability criterion).
- 4. Implement both schemes (MDORwAV and MSI) in MATLAB-Simulink. Plot the graphs of the solutions  $y_{MDORwAV}$  and  $y_{MSI}$ . Plot the absolute error  $|y_{MDORwAV} - y_{MSI}|$  in the separate figure.

## 2 Problem - Discharging of Capacitance

Let's find a solution of the voltage on capacitance  $u_C(t)$  and the current i(t) in RC circuit Fig. 1. Parameters of the RC circuit are  $R = 10\Omega$ ,  $C = 10^{-2}$ F,  $u_C(0) = 10$ V.



Figure 1: RC Circuit

- 1. Set ordinary differential equation (initial value problem) for voltage on capacitance  $u_C(t)$  in the RC circuit Fig. 1.
- 2. Find analytic solution of  $u_C(t)$ .
- 3. Find numerical solution of  $u_C(t)$ : use the Euler method, the Runge-Kutta of 2nd and 4th order. Implement it using your own code (e.g. MATLAB, C, C++, Java, etc. it is on your choice, what you prefer). Compare your numerical solutions with the Taylor series based numerical solution (in TKSL software).
- 4. Compare analytic solution with numerical solutions plot figures with absolute error between numerical solutions and analytical solution.
- 5. Prepare a block scheme of this problem and solve it numerically in MATLAB-Simulink. Compare the numerical solution from Simulink with the previous numerical solutions.
- 6. Change the parameter of capacitance in the RC circuit Fig. 1 to the new value  $C = 10^{-6}$ F and compare the total number of integration

steps used in different numerical methods (Euler method, Runge-Kutta methods and Taylor series based method - TKSL). Which numerical method allow you to make a larger integration step size? NOTE: Use smaller time of simulation.

### **3** Problem - Charging of Capacitance

Let's find a solution of the voltage on capacitance  $u_C(t)$  and the current i(t) in RC circuit in Fig. 2. Parameters of the RC circuit are  $R = 10\Omega$ ,  $C = 10^{-2}$ F, U = 10V,  $u_C(0) = 1$ V.



Figure 2: RC Circuit with Supply Voltage U

- 1. Set ordinary differential equation (initial value problem) for voltage on capacitance  $u_C(t)$  in the RC circuit Fig. 1.
- 2. Find analytic solution of  $u_C(t)$ .
- 3. Find numerical solution of  $u_C(t)$ : use the Euler method, the Runge-Kutta of 2nd and 4th order. Implement it using your own code (e.g. MATLAB, C, C++, Java, etc. it is on your choice, what you prefer). Compare your numerical solutions with the Taylor series based numerical solution (in TKSL software).
- 4. Compare analytic solution with numerical solutions plot figures with absolute error between numerical solutions and analytical solution.

- 5. Prepare a block scheme of this problem and solve it numerically in MATLAB-Simulink. Compare the numerical solution from Simulink with the previous numerical solutions.
- 6. Change the parameter of capacitance in the RC circuit Fig. 2 to the new value  $C = 10^{-6}$ F and compare the total number of integration steps used in different numerical methods (Euler method, Runge-Kutta methods and Taylor series based method TKSL). Which numerical method allow you to make a larger integration step size? NOTE: Use smaller time of simulation.

## 4 Problem - RLC circuit

Let's find a solution of the voltage on capacitance  $u_C(t)$  and the current i(t) in RLC circuit Fig. 3. Parameters of the RLC circuit are  $R = 200\Omega$ ,  $L = 10^{-2}$ H,  $C = 10^{-6}$ F,  $u_C(0) = 0$ V, i(0) = 0A and input voltage  $u(t) = U \sin(\omega t)$ V, where U = 1V and  $\omega = 1000$  rad/s.



Figure 3: RLC Circuit with AC Supply Voltage U

- 1. Set ordinary differential equation (initial value problem) for voltage on capacitance  $u_C(t)$  in the RLC circuit Fig. 3.
- 2. Find analytic solution of  $u_C(t)$  and i(t).
- 3. Find numerical solution of  $u_C(t)$ : use the Euler method, the Runge-Kutta of 2nd and 4th order. Implement it using your own code (e.g. MATLAB, C, C++, Java, etc. it is on your choice, what you prefer). Compare your numerical solutions with the Taylor series based numerical solution (in TKSL software).

- 4. Compare analytic solution with numerical solutions plot figures with absolute error between numerical solutions and analytical solution.
- 5. Prepare a block scheme of this problem and solve it numerically in MATLAB-Simulink. Compare the numerical solution from Simulink with the previous numerical solutions. NOTE: Use auxiliary differential equations to generate the input voltage the function  $u(t) = \sin(1000t)$ .